 



FIGURES FOR
CHAPTER 11
LATCHES AND FLIP-FLOPS

This chapter in the book includes:




- Objectives
- Study Guide
- 11.1 Introduction
- 11.2 Set-Reset Latch
- 11.3 Gated D Latch
- 11.4 Edge-Triggered D Flip-Flop
- 11.5 S-R Flip-Flop
- 11.6 J-K Flip-Flop
- 11.7 T Flip-Flop
- 11.8 Flip-Flops with Additional Inputs
- 11.9 Summary
- Problems
- Programmed Exercise

 
Click the mouse to move to the next page.
Use the ESC key to exit this chapter.




Study Guide, No. 1

 


Study Guide, No. 3c

 


Study Guide, No. 4d

 


Study Guide, No. 7b

 

Study Guide, No. 8b

 


(a) Inverter with feedback

 


(b) Oscillation at inverter output

Figure 11-1

 


(a)

 


(b)

Figure 11-2

 


(a)

 


(b)

Figure 11-3

 


(a)

 


(b)

Figure 11-4

 

(a)

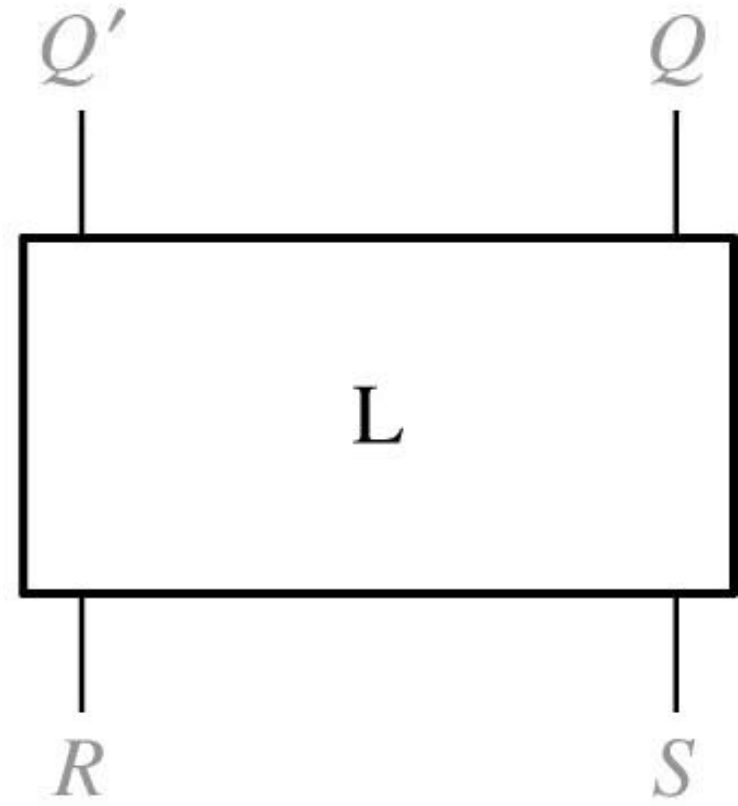

(b)

Figure 11-5: S-R Latch

 


Figure 11-6: Improper S-R Latch Operation

 


Figure 11-7: Timing Diagram for S-R Latch

		$S(t)$	
		00	01
$R(t) Q(t)$	00	0	1
	01	1	1
	11	0	X
	10	0	X

$$Q(t + \epsilon) = S(t) + R'(t) Q(t)$$

Figure 11-8: Map for $Q(t + E)$



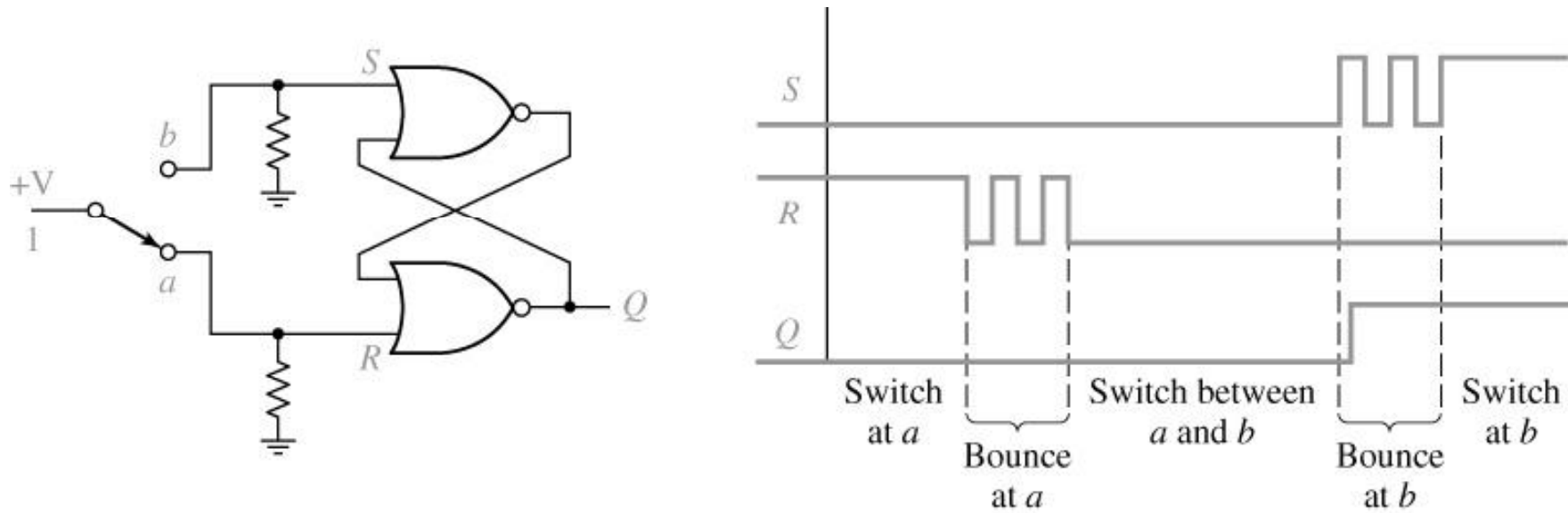


Figure 11-9: Switch Debouncing with an S-R Latch

 

(a)

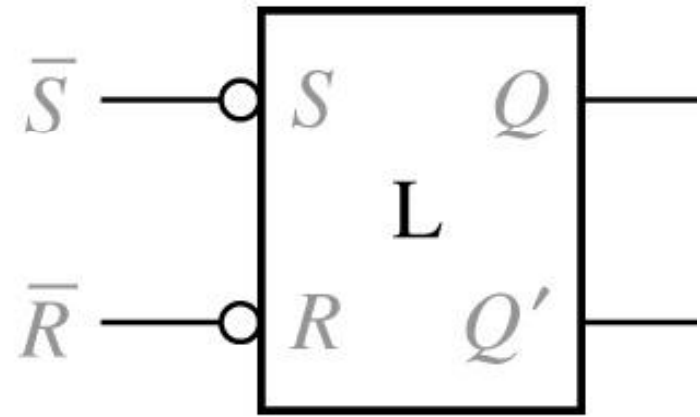

(b)

Figure 11-10: \bar{S} - \bar{R} Latch

 
 


Figure 11-11: Gated D Latch


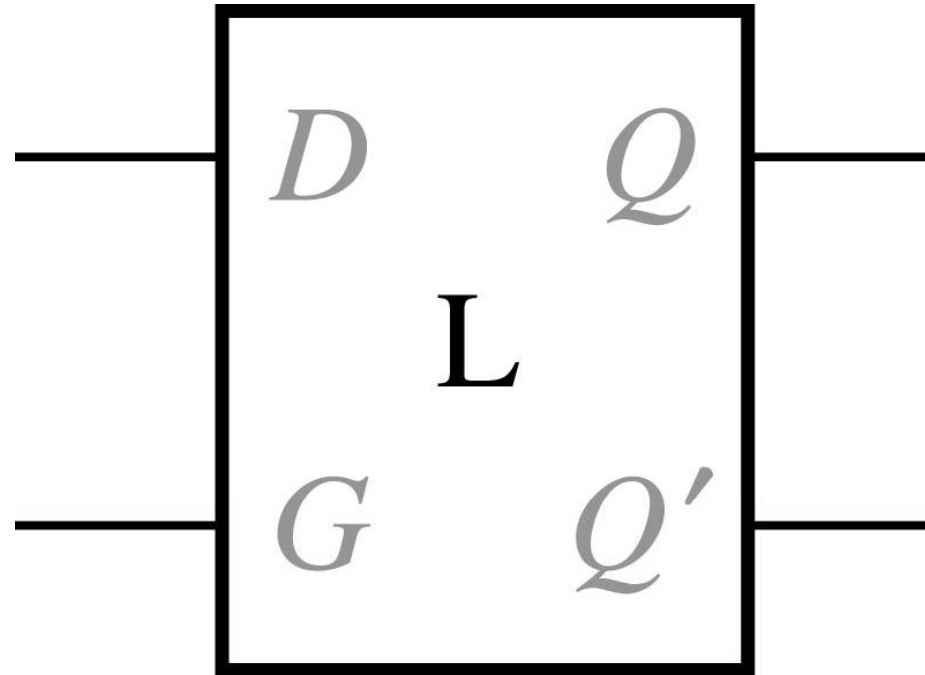


Figure 11-12 (left): Symbol and Truth Table for Gated Latch


		<i>GD</i>			
		00	01	11	10
<i>Q</i>	0	0	0	1	0
	1	1	1	1	0

$$Q^+ = G'Q + GD$$

Figure 11-12 (right): Symbol and Truth Table for Gated Latch

 

(a) Rising-edge trigger

 

(b) Falling-edge trigger

Figure 11-13a and b: D Flip-Flops



 


Figure 11-14: Timing for D Flip-Flop (Falling Edge Trigger)

 

 (a) Construction from two gated D latches



(b) Time analysis

Figure 11-15: D Flip-Flop (Rising Edge Trigger)



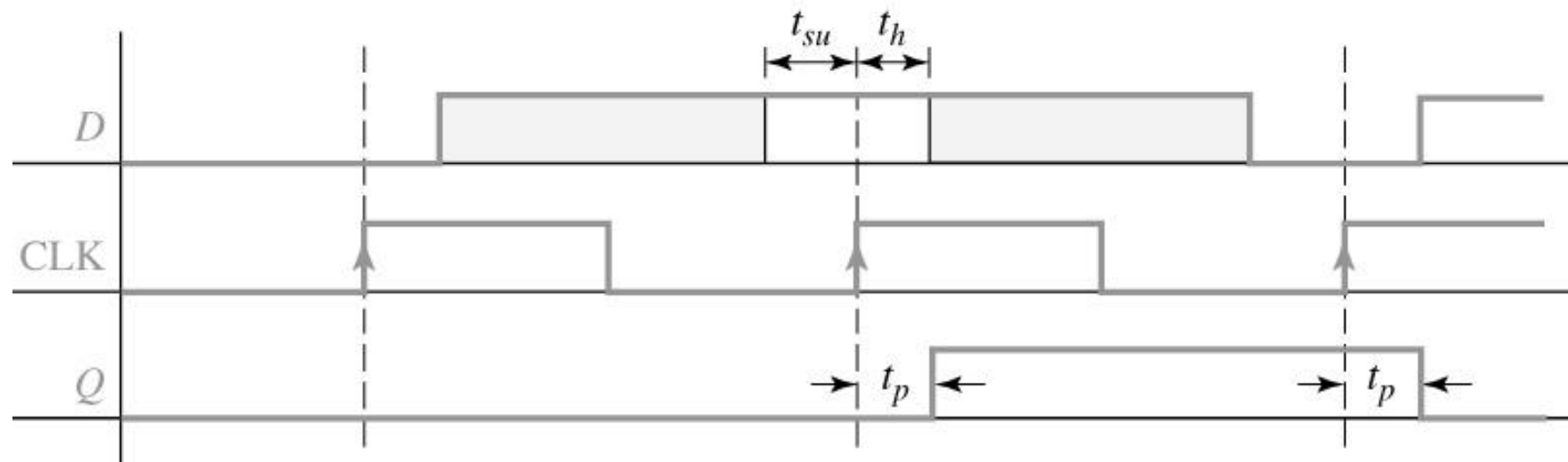



Figure 11-16: Setup and Hold Times for an Edge-Triggered D Flip-Flop

 


(a) Simple flip-flop circuit

 

(b) Setup time not satisfied

 

(c) Setup time satisfied

 

(d) Minimum clock period

Figure 11-17: Determination of Minimum Clock Period



 


Figure 11-18: S-R Flip-Flop

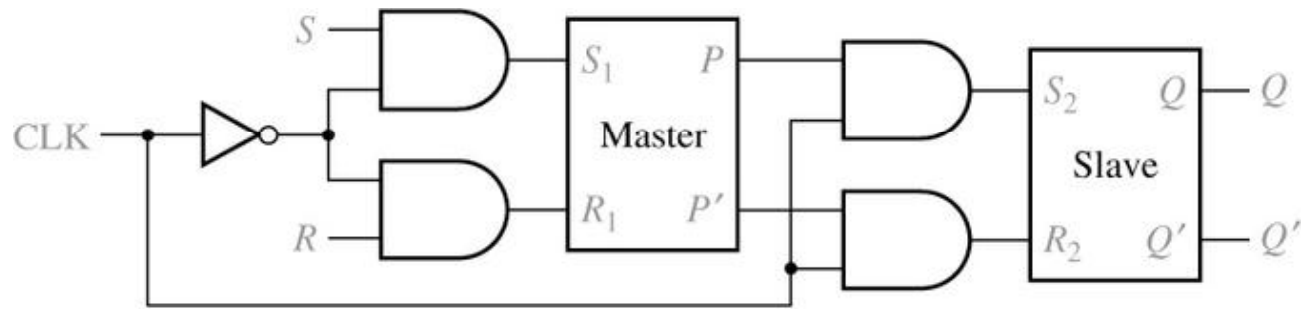


(a) Implementation with two latches

 


(b) Timing analysis

Figure 11-19: S-R Flip-Flop Implementation and Timing

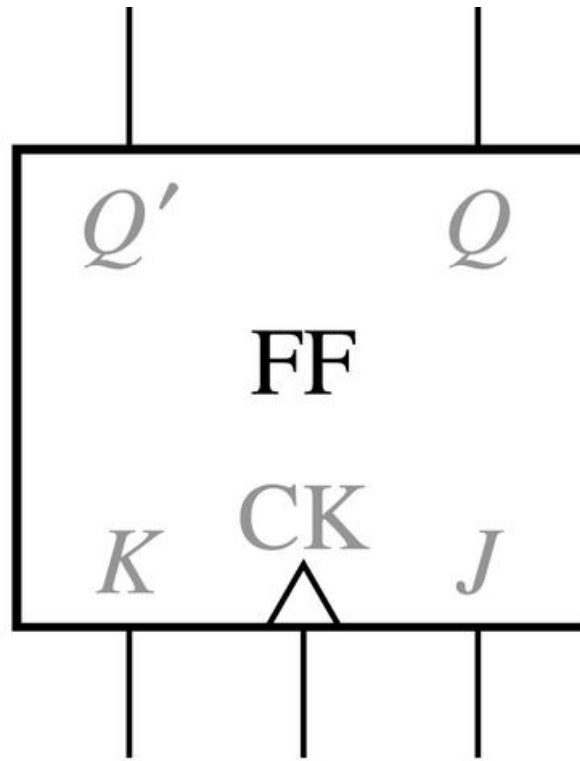


(a) J-K flip-flop

**Figure 11-20a: J-K Flip-Flop
(Q Changes on the Rising Edge)**

 


(c) J-K flip-flop timing

**Figure 11-20c: J-K Flip-Flop
(Q Changes on the Rising Edge)**

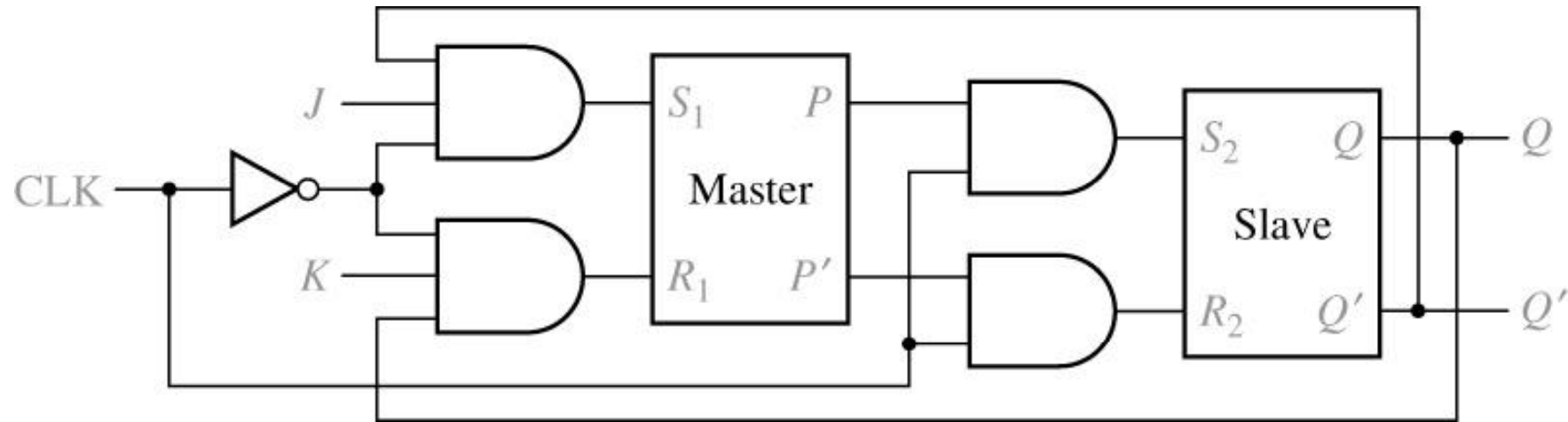

**Figure 11-21: Master-Slave J-K Flip-Flop
(Q Changes on Rising Edge)**

 

(a)

Figure 11-22a: T Flip-Flop



 


Figure 11-23: Timing Diagram for T Flip-Flop (Falling-Edge Trigger)

 


(a) Conversion of J-K to T

 

(b) Conversion of D to T

Figure 11-24: Implementation of T Flip-Flops

 

(a)

Figure 11-25: D Flip-Flop with Clear and Preset

 


Figure 11-26: Timing Diagram for D Flip-Flop with Asynchronous Clear and Preset



 



Figure 11-27: D Flip-Flop with Clock Enable

 


Problem 11.1

 


Problem 11.2b

 


Problem 11.2c

 


Problem 11.3

 


Problem 11.5

 



Problem 11.7

 


Problem 11.8

 


Problem 11.9a

  


Problem 11.9b

 

Problem 11.11

 


(a)

 


(b)


Problem 11.12

 


Problem 11.13

 


Problem 11.14

 



Problem 11.16

 


Problem 11.17

 


Problem 11.18

  


Problem 11.19

 


Problem 11.20

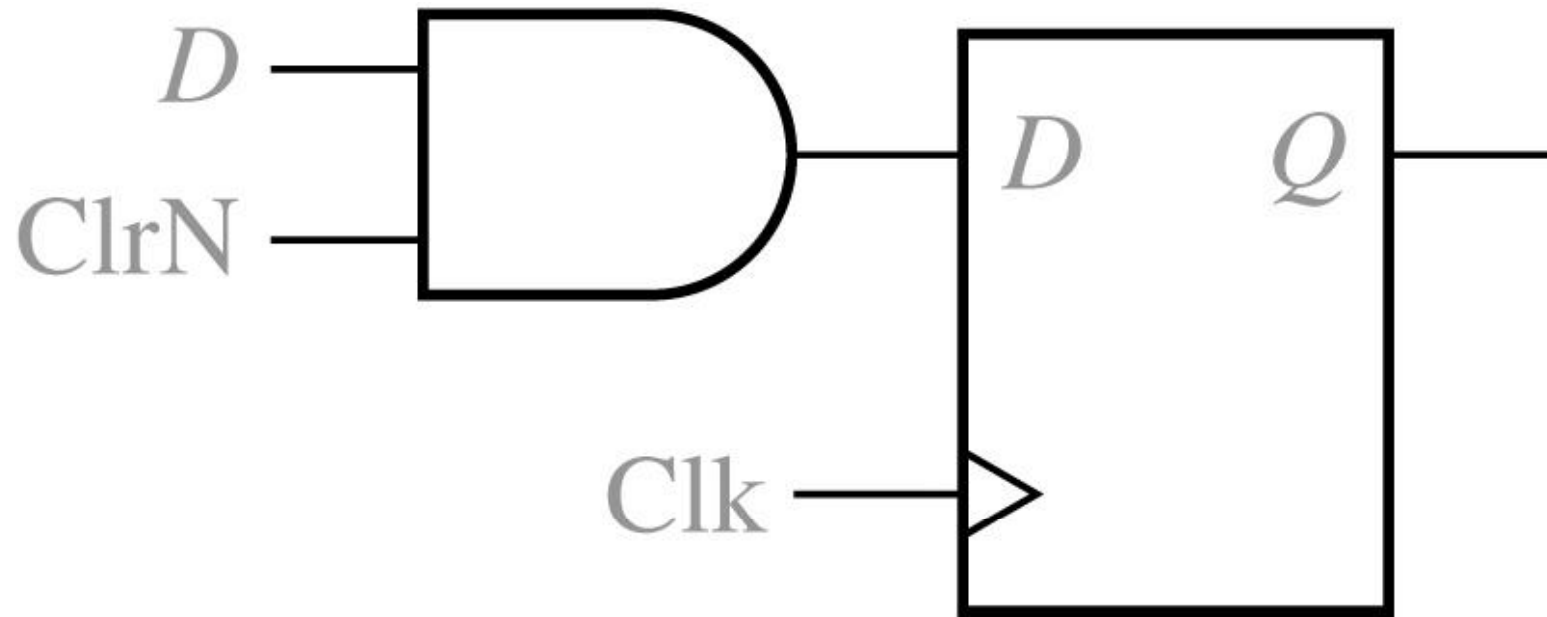


Problem 11-21 (part 1)

 


Problem 11-21 (part 2)

 

Programmed Exercise 11.24 (diagram)

 

 Programmed Exercise 11.24 (Answer 5 of 6)



Programmed Exercise 11.24 (Answer 6 of 6)