 



FIGURES FOR
CHAPTER 8

**COMBINATIONAL CIRCUIT DESIGN
AND SIMULATION USING GATES**





This chapter in the book includes:


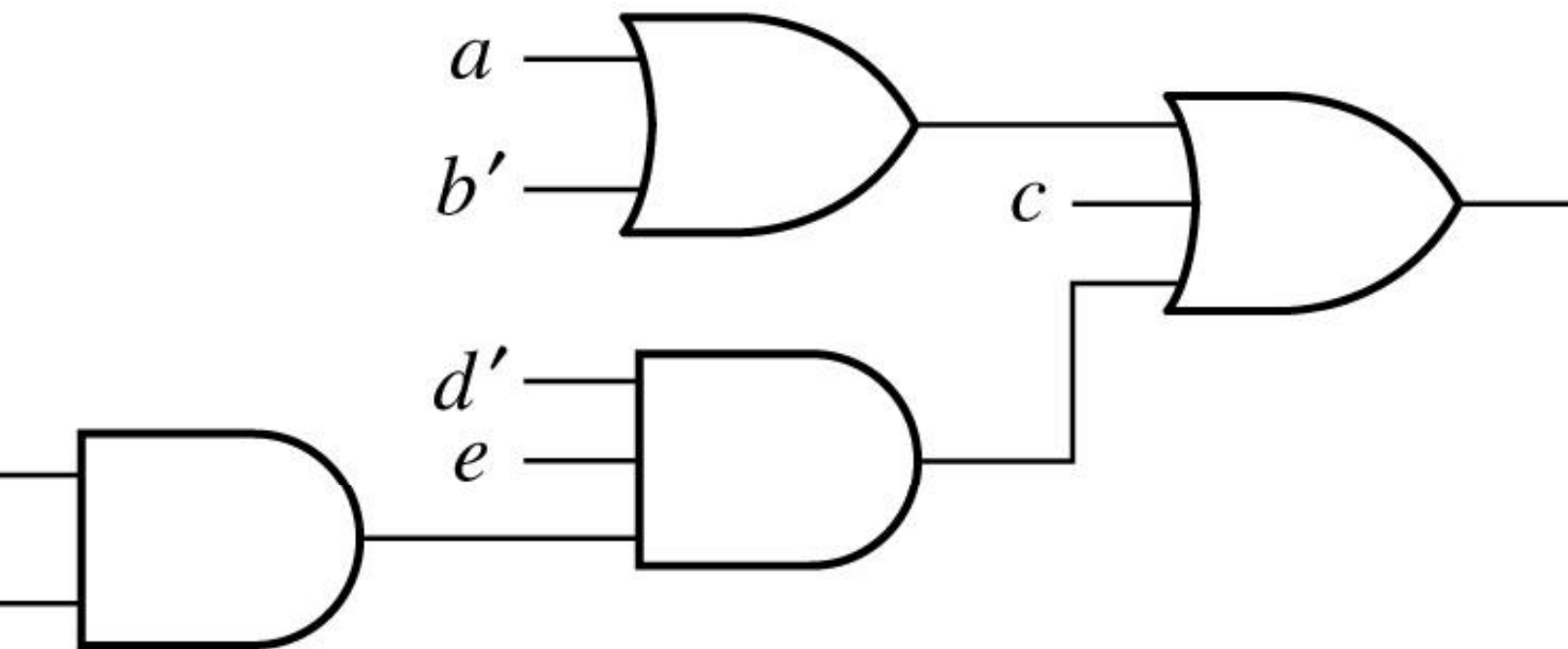
- Objectives
- Study Guide
- 8.1 Review of Combinational Circuit Design
- 8.2 Design Circuits with Limited Gate Fan-In
- 8.3 Gate Delays and Timing Diagrams
- 8.4 Hazards in Combinational Logic
- 8.5 Simulation and Testing of Logic Circuits
- Problems
- Design Problems




Study Guide, No. 3

  


Study Guide, No. 5a

  

Study Guide, No. 6a

 

Study Guide, No. 7b

 

$$f' = a'b'c'd + ab'cd + abc' + a'bc + a'cd'$$



 



Figure 8-1

 

$$= \Sigma m(0, 2, 3, 4, 5)$$

 

$$f_2 = \Sigma m(0, 2, 3, 4, 7)$$

 

$$f_3 = \Sigma m(1, 2, 6, 7)$$

Figure 8-2

 


Figure 8-3: Realization of Figure 8-2

 


Figure 8-4: Propagation Delay in an Inverter

 
 


Figure 8-5: Timing Diagram for AND-NOR Circuit



 



Figure 8-6: Timing Diagram for Circuit with Delay

 

Static 1-hazard

 

(b) Static 0-hazard

 

(c) Dynamic hazards



 



Figure 8-7: Types of Hazards

 

(a) Circuit with a static 1-hazard

 


(b) Timing chart

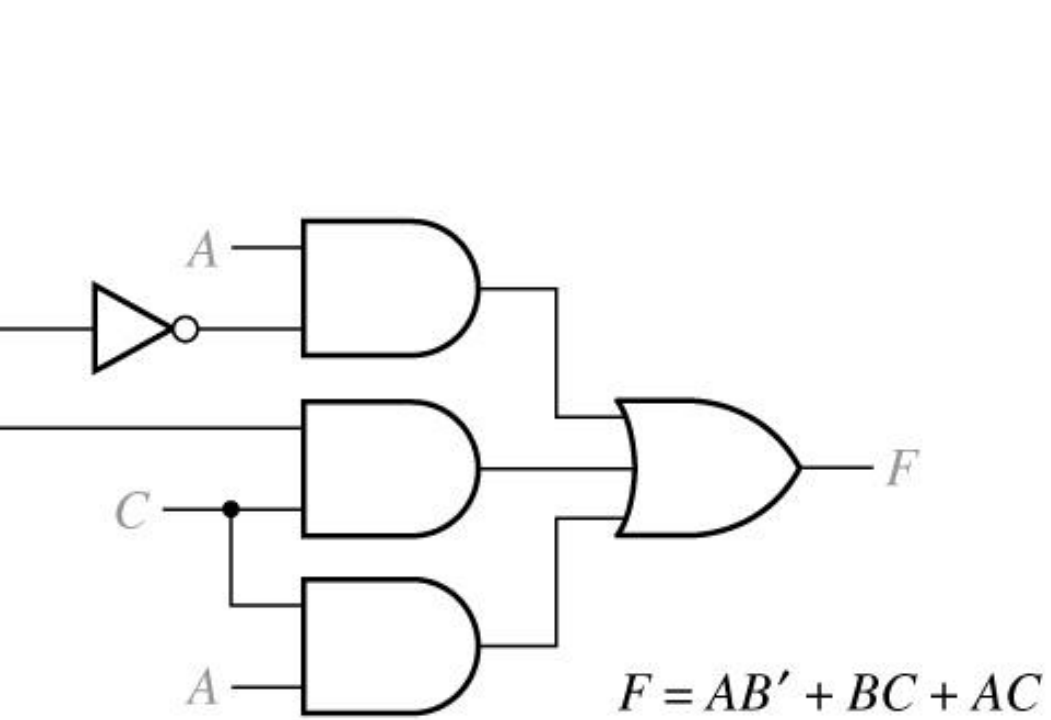


		A	
		0	1
BC	00	0	1
	01	0	1
	11	1	1
	10	0	0


Figure 8-9: Circuit with Hazard Removed

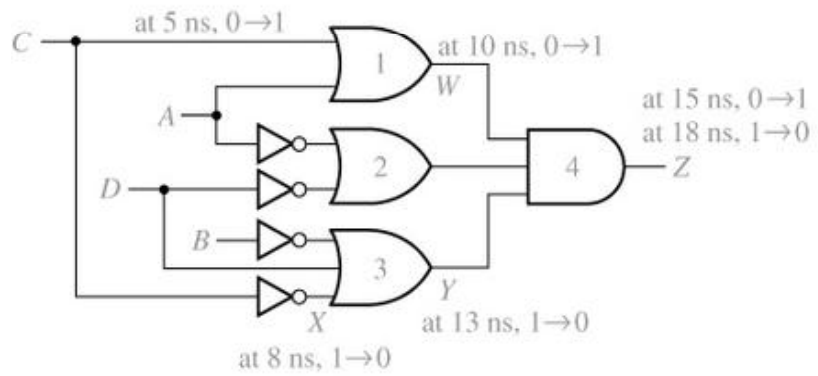

(a) Circuit with a static 0-hazard

 

(b) Karnaugh map for circuit of (a)

 

(c) Timing diagram illustrating 0-hazard of (a)



 


Figure 8-11: Karnaugh Map Removing Hazards

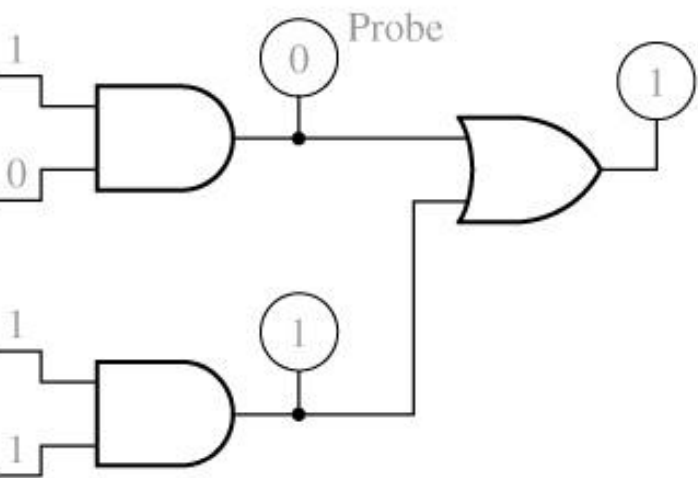

Simulation screen showing switches

 

(b) Simulation screen with missing gate input

Figure 8-12



 
 



Figure 8-13: Logic Circuit with Incorrect Output

 


Problem 8.1

 



Problem 8.3

 


Problem 8.4

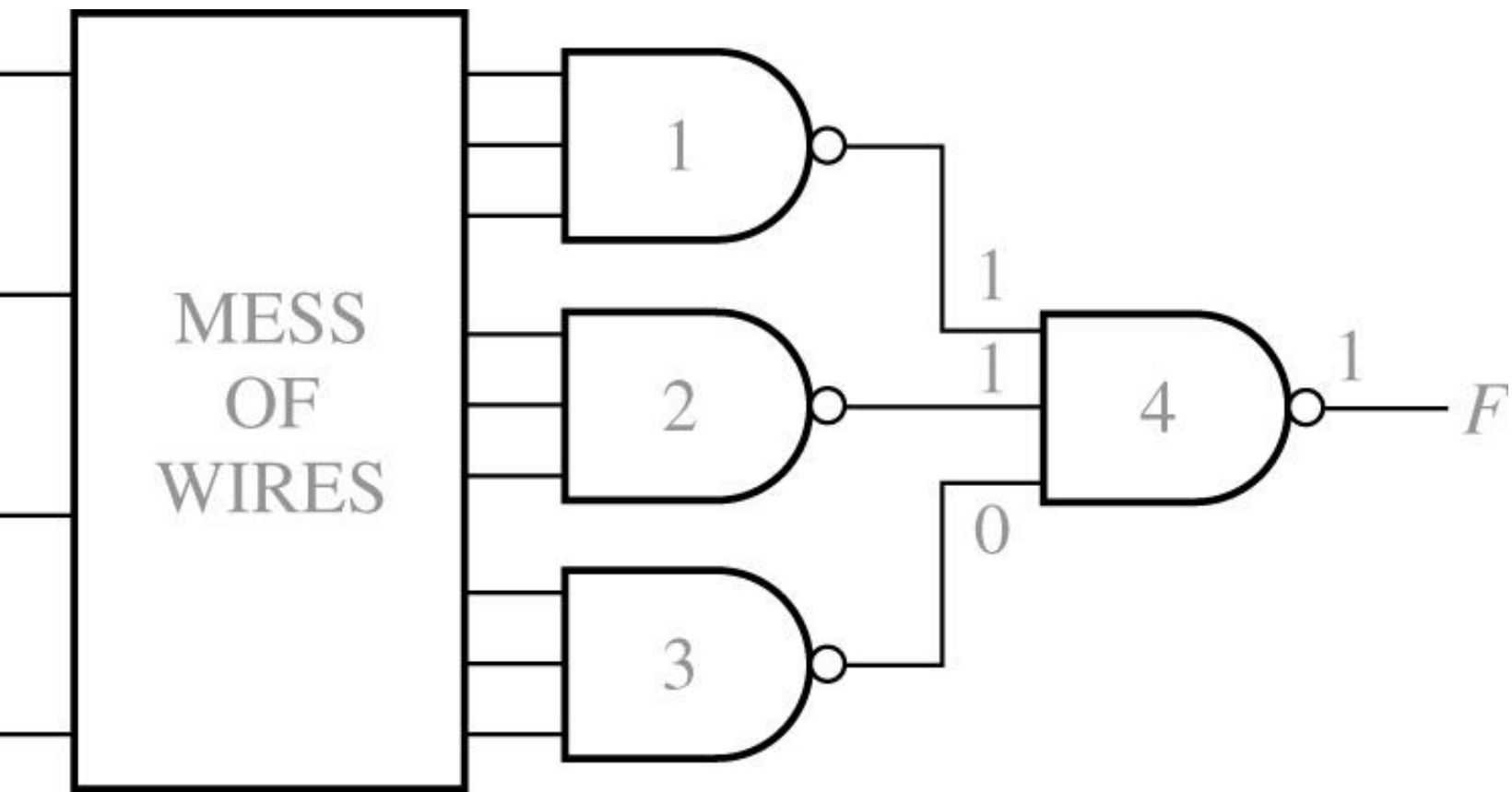


Problem 8.5

  

Problem 8.6

 

Problem 8.8

 

Problem 8-9



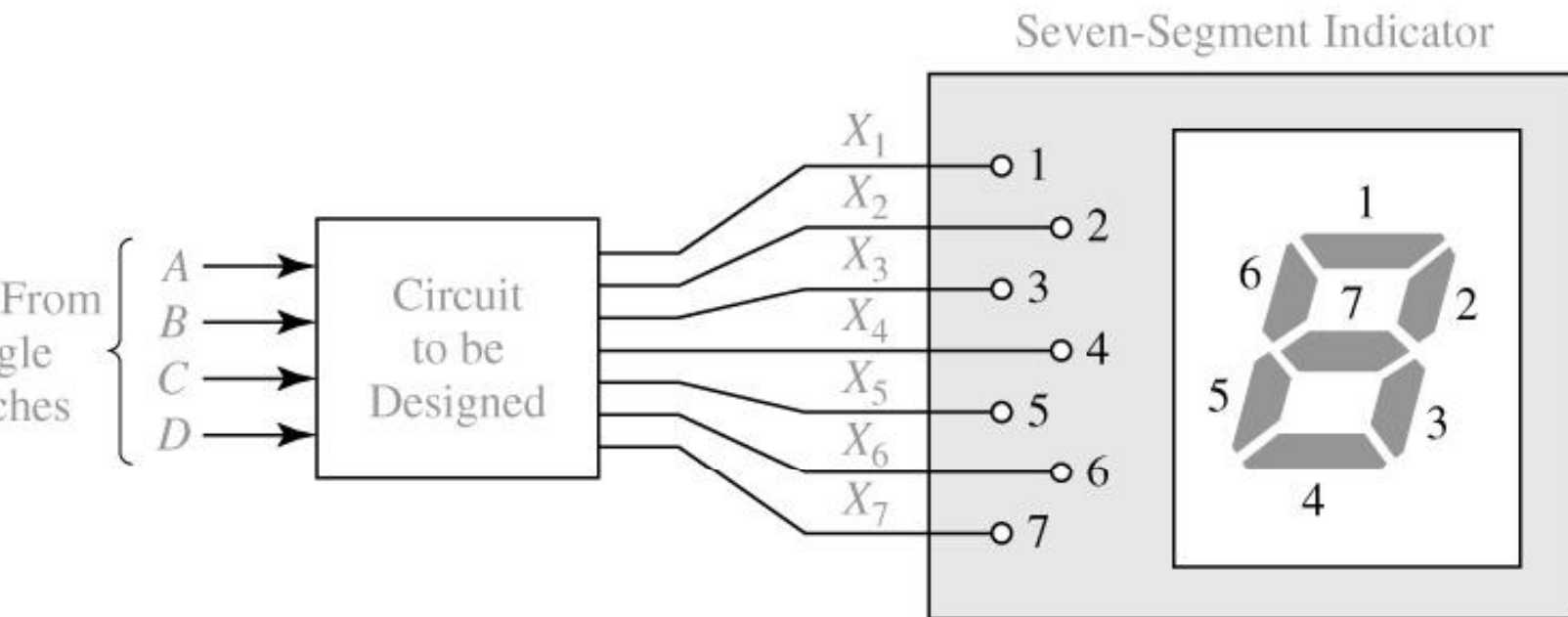



Figure 8.14: Circuit Driving Seven-Segment Module

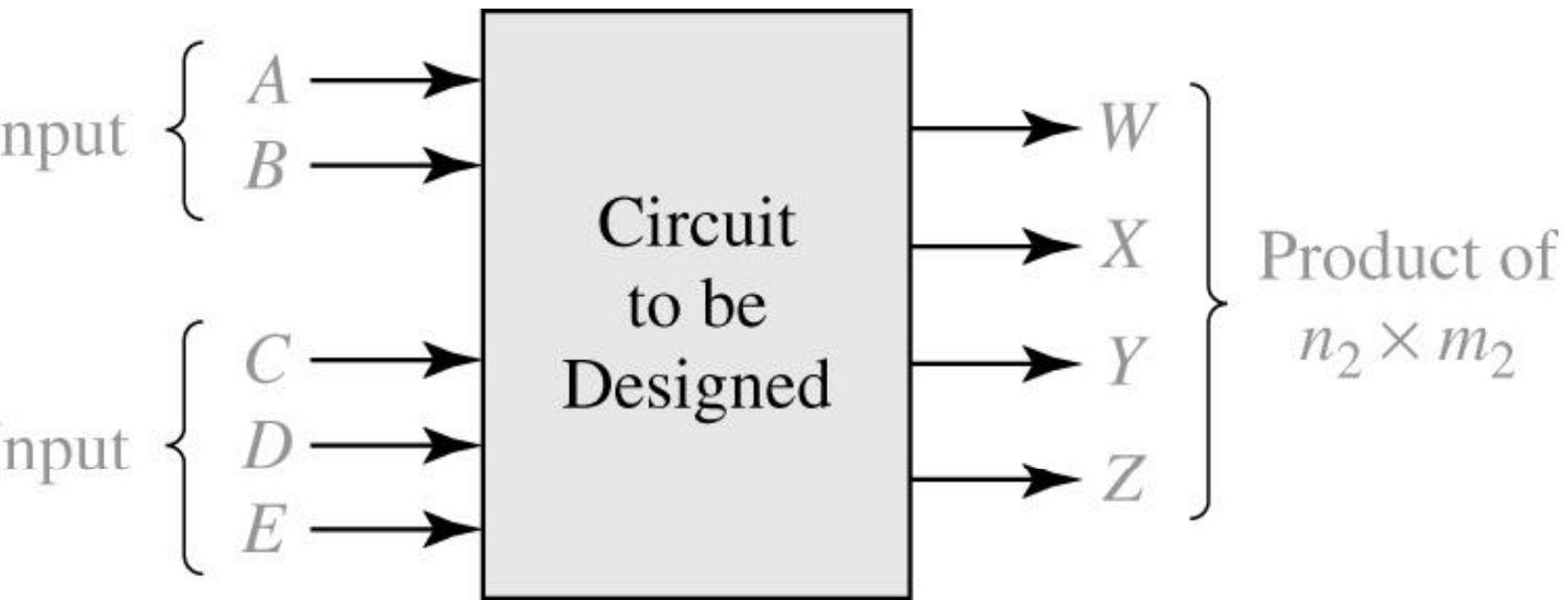

Design Problem 8.C

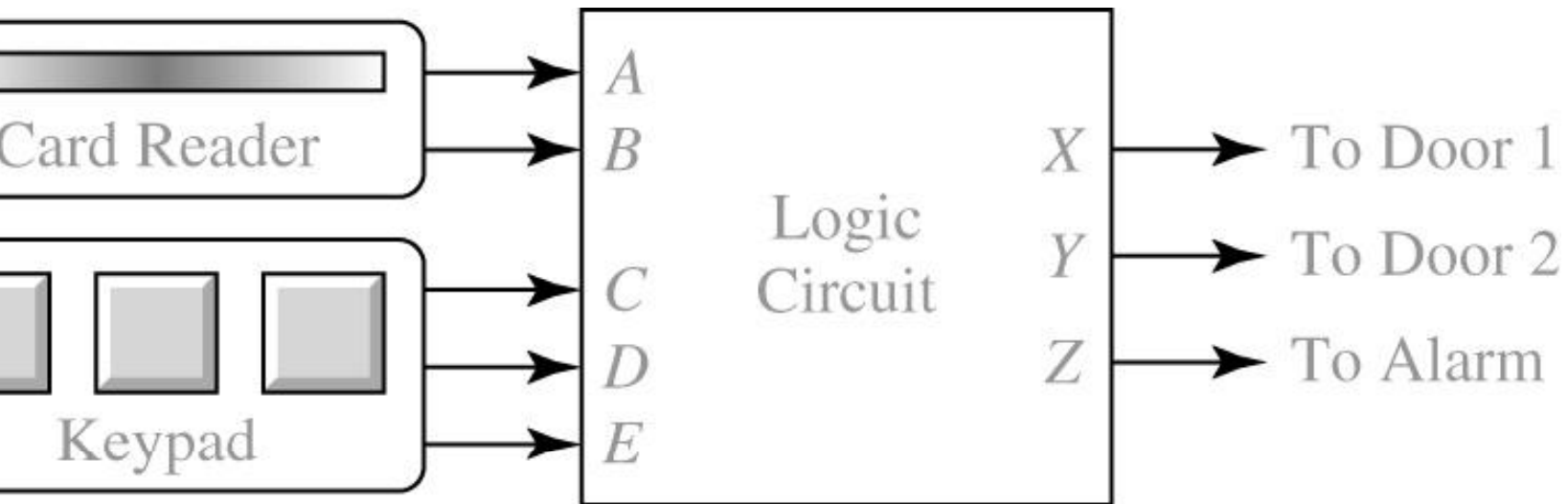

Design Problem 8.N

 

Design Problem 8.S