

# Chap 11: Flip-Flops

Combinational: Output is a function of **present inputs** only


Sequential : Output is function both **present and previous inputs**

Circuit “**remembers**” previous history

→ Flip Flop (F/F): with clock input (on clock **edge**)


→ Latches : with no clock input (on clock **level**)

 F/F: a memory device with 1 output,  
or 2 complementary outputs








# Timing in combinational circuits

*That's what we learn up to now.*

 

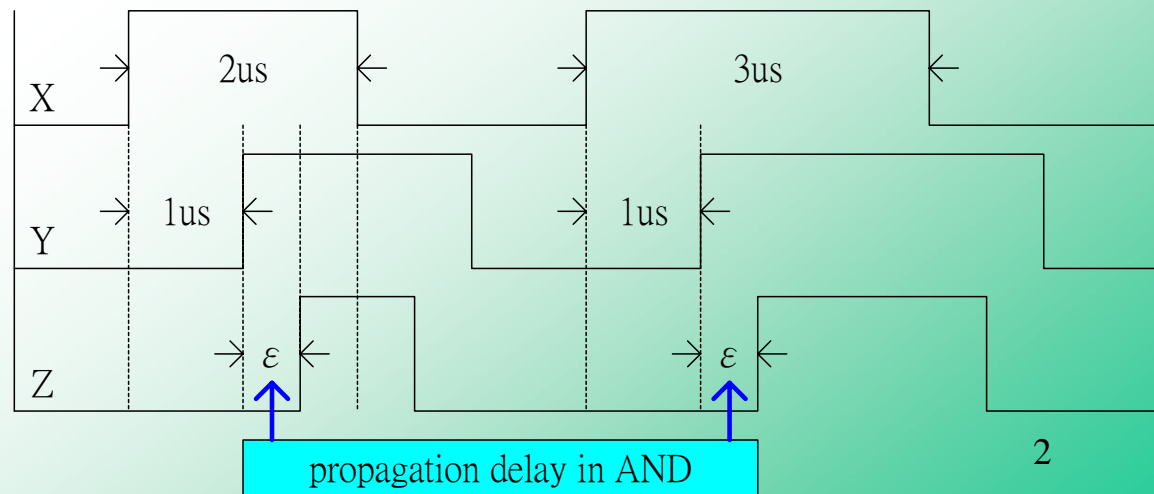    
$\epsilon_1, \epsilon_2$  may be very small but still exist.




How your construct a switching circuit with memory? By *feedback*

## Timing in feedback Network

*One inversion*






 


*Two inversions*


 


*To control the stable states*

# Set-Reset Latch (SR latch)

      

# Timing Diagram

 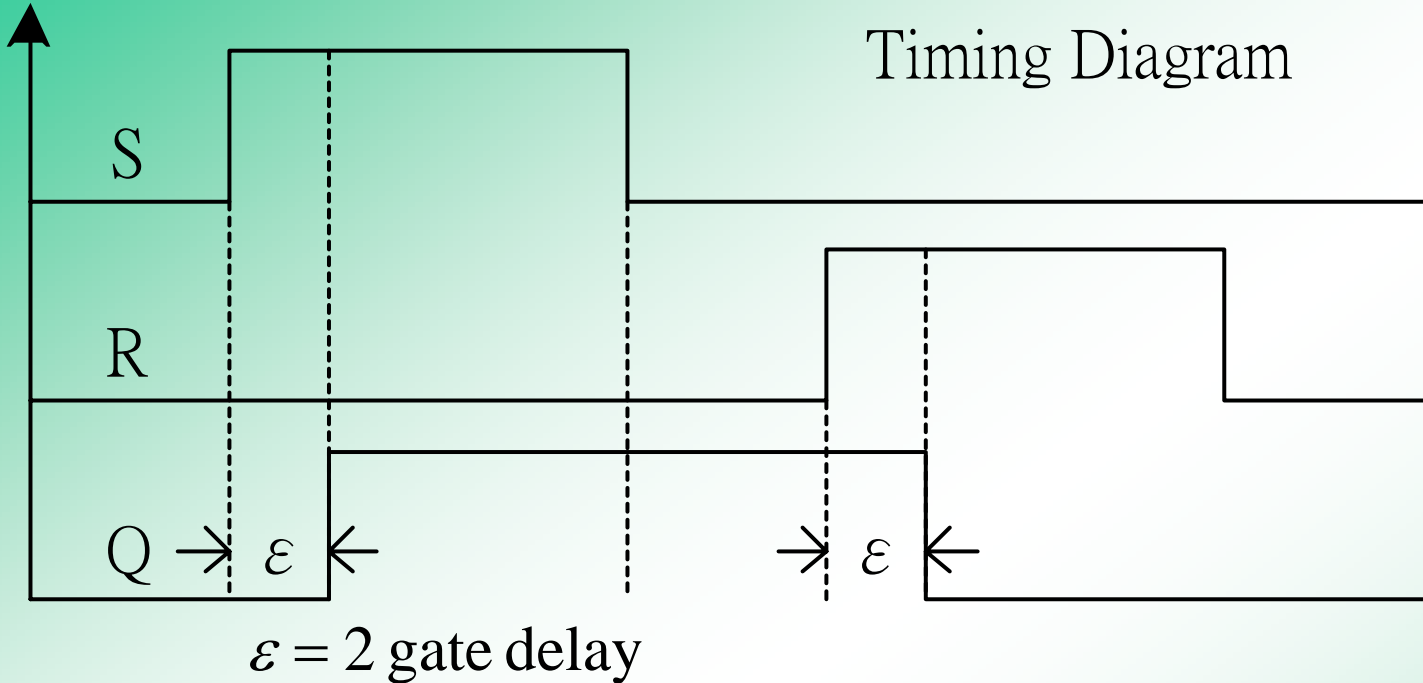


if  $R, S$  同時  $1 \rightarrow 0$ ,

$\Rightarrow Q = Q' = 1 \rightarrow 0$  (not allowed)

or  $Q = 1$  first or  $Q' = 1$  first (undetermined)

$S(t)$	$R(t)$	$Q(t)$	$Q(t + \varepsilon) (= Q^+(t))$
0	0	0	0 $Q_t(Q_n)$ : Present State
0	0	1	1 $Q_t^+(Q_{n+1})$ : Next State
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	—
1	1	1	—

} inputs not allowed

 

$$Q(t + \varepsilon) = S(t) + R'(t)Q(t) \quad (SR = 0) \text{ or}$$

$$\underbrace{Q^+ = S + R'Q}_{\text{characteristic equation}}$$



$$(SR = 0)$$

		S(t)		
		0	1	
R(t)	Q(t)	00	0	1
		01	1	1
		11	0	X
		10	0	X

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	—

$Q_n$  : present state  
 $Q_{n+1}$  : next state

## Alternative form using NAND gates

  


$\bar{S}$	$\bar{R}$	$Q_{n+1}$	
1	1	$Q_n$	$Q_n$ : present state
1	0	0	$Q_{n+1}$ : next state
0	1	1	
0	0	—	







## Usage of SR latch

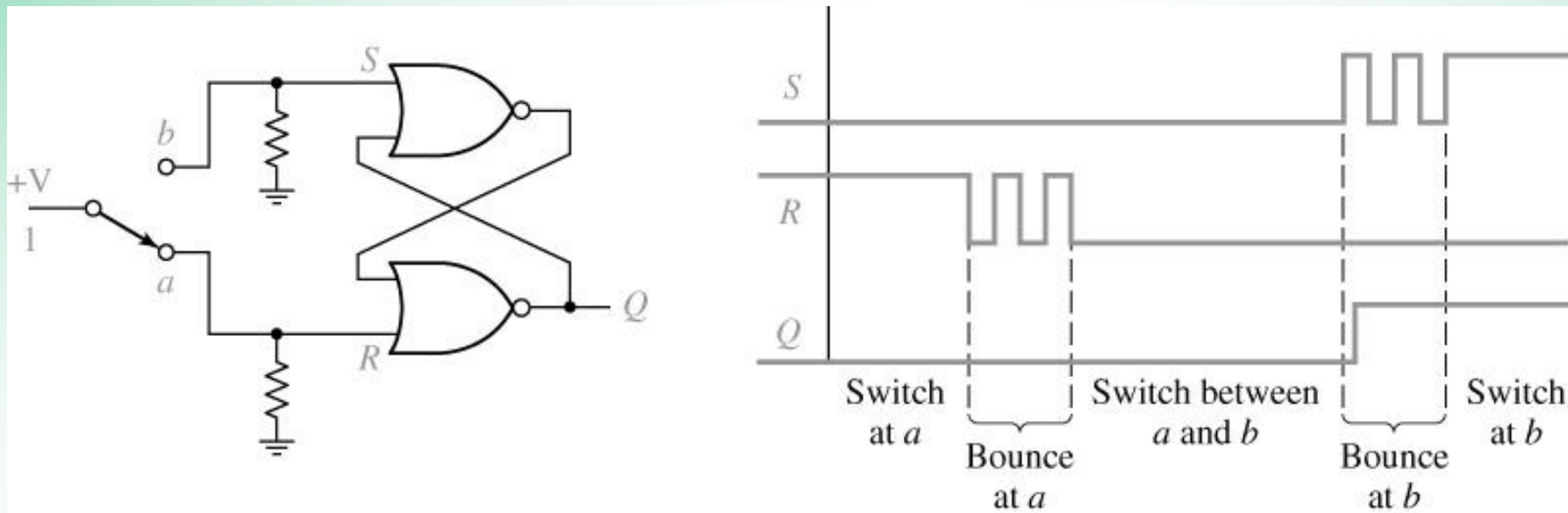1. As component in more complex latches and FFs
2. For debouncing switches




# Gated D Latch

*Transparent* latch since  $G=1, Q = D$

 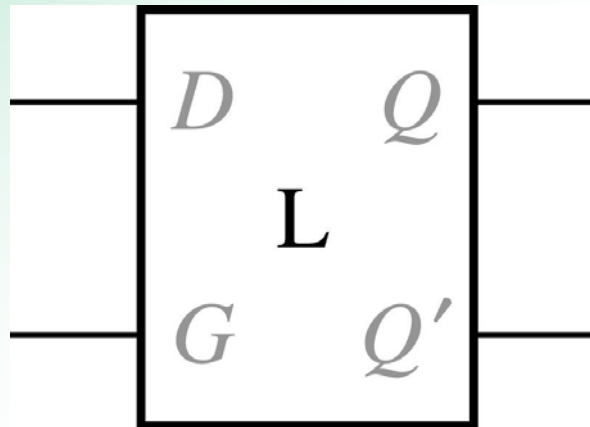  

 
# Edge-Triggered D Flip-Flop


Similar to D latch, but changes only to *clock edge*



(a) Rising-edge trigger


 


(b) Falling-edge trigger

 


$D$	$Q_n$	$Q_{n+1}$	$D$	$Q_n^+$
0	0	0	0	0
0	1	0	1	1
1	0	1		
1	1	1	$Q^+ = D$	
  
## Timing diagram of *falling edge* triggered DFF



 
(a) Construction from two gated D latches



(b) Time analysis

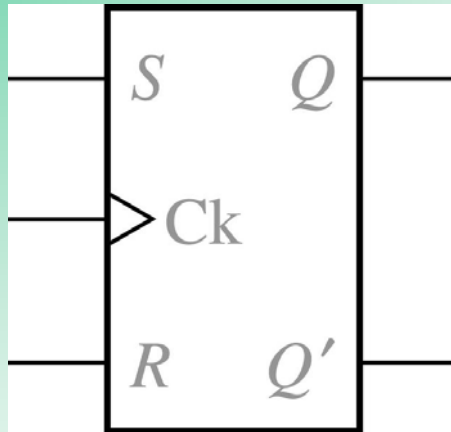
# SR Flip-Flop

Similar to SR latch, but changes only to *clock edge*, and *extra clock in*




$S$	$R$	$Q_{n+1}$	
0	0	$Q_n$ (no state change)	$Q_n$ : present state $Q_n + 1$ : next state
0	1	0(reset Q to 0, after active CLK edge)	
1	0	1(set Q to 1, after active CLK edge)	
1	1	– (not allowed)	

# SR implementation and timing

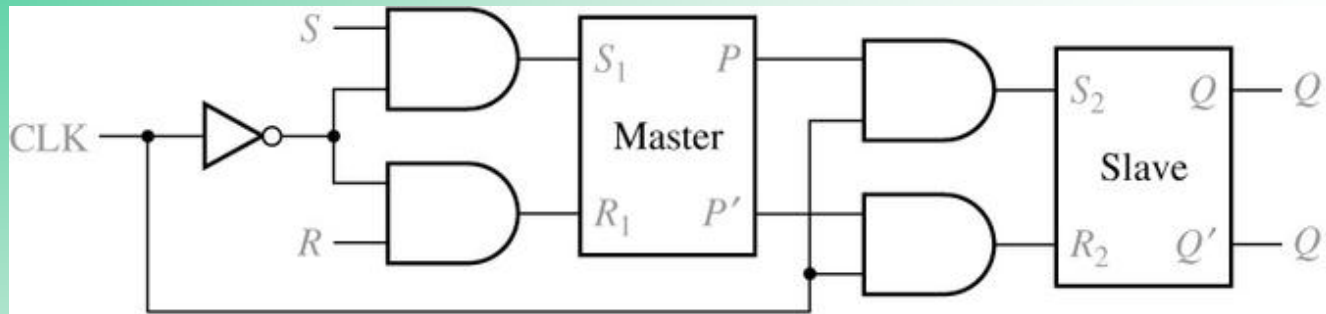

(a) Implementation with two latches



*Master-slave FF*

 


(b) Timing analysis

*Not an edge-triggered FF*

# D F/F (Delay F/F)

  

$D$	$Q_n$	$Q_{n+1}$	$D$	$Q_n^+$
0	0	0	0	0
0	1	0	1	1
1	0	1		
1	1	1		$Q^+ = D$

 



# J-K F/F

Extended version of SR FF

$J$	$K$	$Q$	$Q^+$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$Q^+ = QK' + Q'J$


$J$	$K$	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\overline{Q_n}$

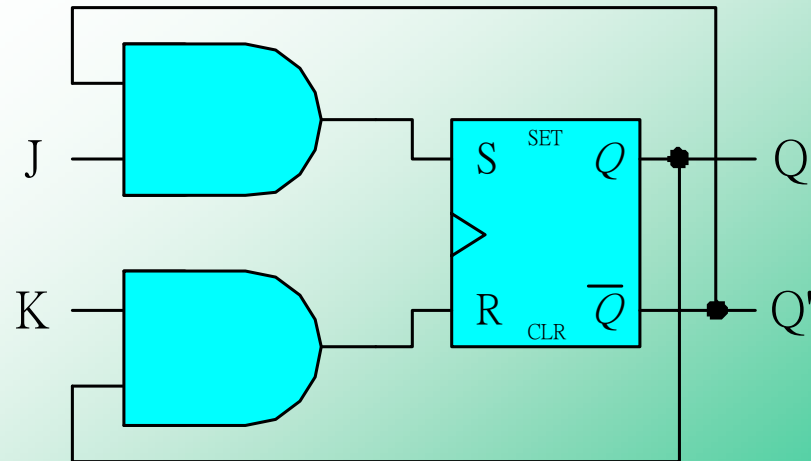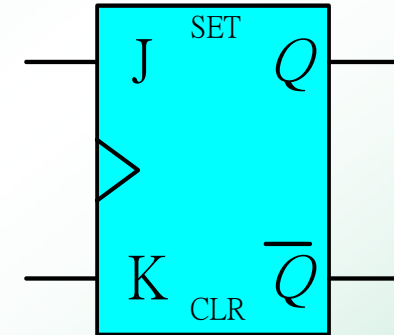



$J = K = 1$ :  $J - K$  F/F acts as a T - F/F

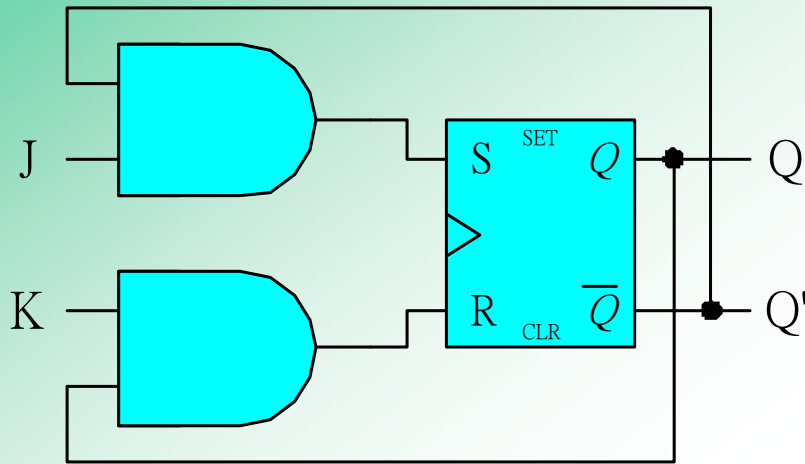otherwise:  $J - K$  F/F acts as a S - R F/F



$$\left\{ \begin{array}{l} J = 1, K = 0 \Rightarrow Q^+ = 1 \\ J = 0, K = 1 \Rightarrow Q^+ = 0 \\ J = 0, K = 0 \Rightarrow Q^+ = Q \\ J = 1, K = 1 \Rightarrow Q^+ = Q' \end{array} \right.$$

Timing Problem:

If  $J = K = 1$ , do not arrive at the same time



$\Rightarrow$  may  $J = 0, K = 1$

or too long


$\Rightarrow$  Q may  $0 \rightarrow 1 \rightarrow 0 \rightarrow 1$  oscillation

$\Rightarrow$  Using clocked J - K F/F


## Clocked JK F/F

  

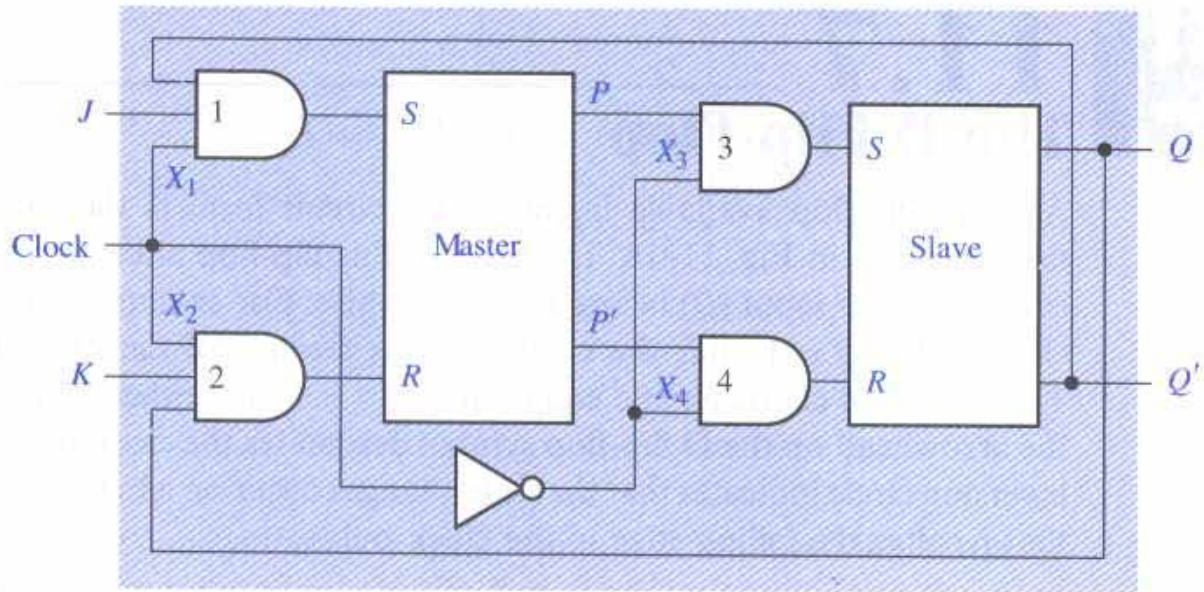The Change of F/F state always occurs on the **falling edge** of the CLK pulse regardless **pulse width**





(a) Master-slave J-K flip-flop

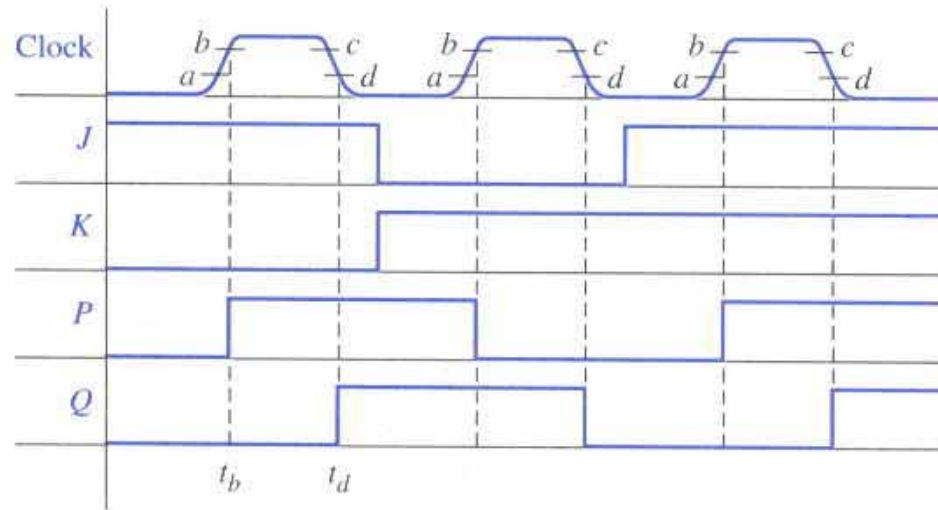


(b) Internal timing diagram for master-slave J-K flip-flop
  
# Trigger F/F (T-F/F)

$$\begin{cases} R = QT \\ S = Q'T \end{cases} \quad \text{i.e.} \quad \begin{array}{l} Q = 1 \xrightarrow{\text{next input}} R = 1 \\ \xrightarrow{\text{next state}} Q = 0 \end{array}$$



$T$	$Q$	$Q_n^+$	$Q_n^+ = T'Q + TQ'$
$0$	$0$	$0$	$= T \oplus Q$
$0$	$1$	$1$	
$1$	$0$	$1$	
$1$	$1$	$0$	

 



$T$	$Q_{n+1}$
$0$	$Q_n$
$1$	$\overline{Q_n}$

$\delta$  : 1AND + 2NOR gate delay


*T must terminate before Q changes state so we add a delay.*
 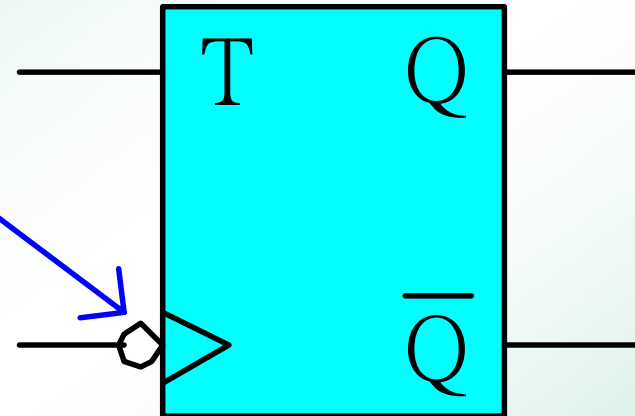
## Clocked T F-F: For Synchronous design

falling edge triggering.  
(Negative edge triggering)



# Clocked F/F with Clear and Preset

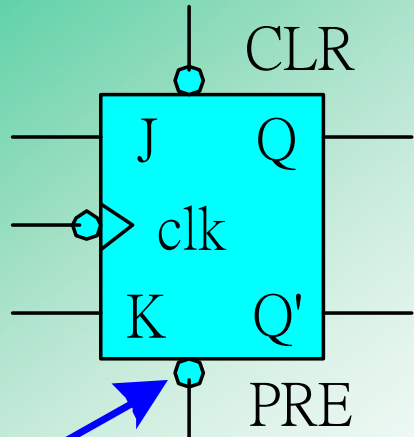


a "0" activates


$$CLR = 0 \Rightarrow Q = 0$$

$$PRE = 0 \Rightarrow Q = 1$$
 
$$CLK = PRE = 1 \Rightarrow \text{Normal Operation}$$



rising edge triggering

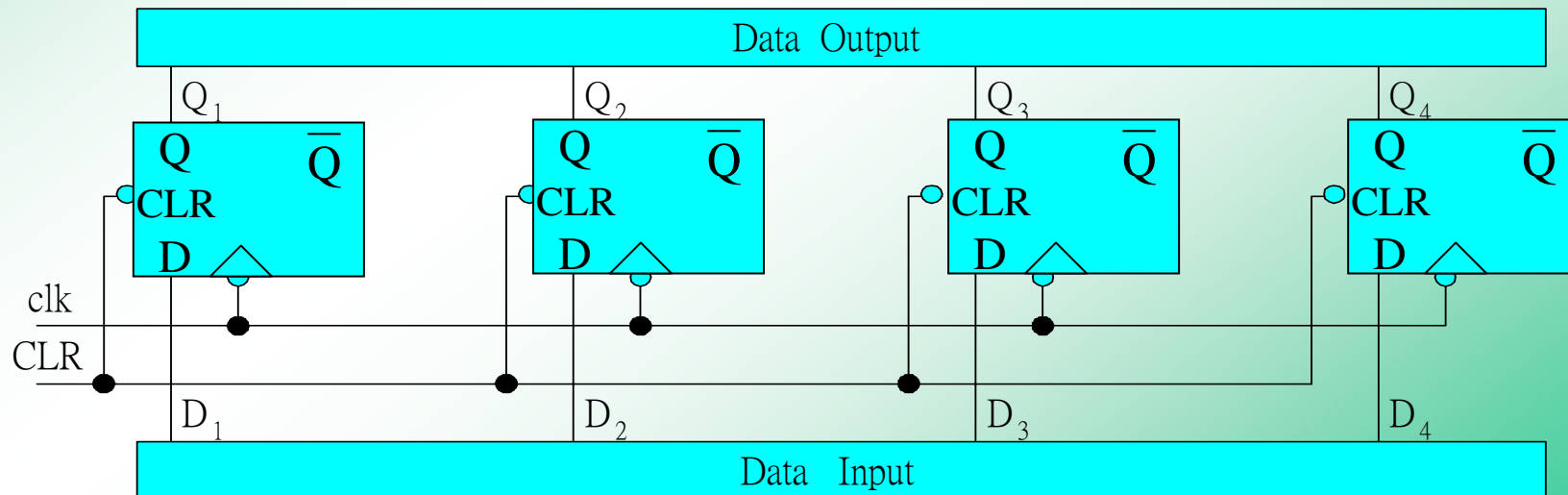

## Characteristic Equations



$$Q^+ = S + R'Q \quad SR \text{ F / F} \quad (SR = 0) \text{ SR 不同時爲 1}$$

$$Q^+ = T \oplus Q \quad T \text{ F / F}$$

$$Q^+ = JQ' + K'Q \quad JK \text{ F / F}$$

$$Q^+ = D \quad D \text{ F / F}$$

## Conversion between F/F

  

# HOMWORK -- Unit 11

- 11.3
- 11.6
- 11.8
- 11.12
- 11.14
- 11.21

