

Chap 12:


Registers and Counters

Objectives


- Registers
 - Operation
 - Application to shift registers
- Counters
 - How to build and how it works
 - Counter application and how to derive the FF's input equations

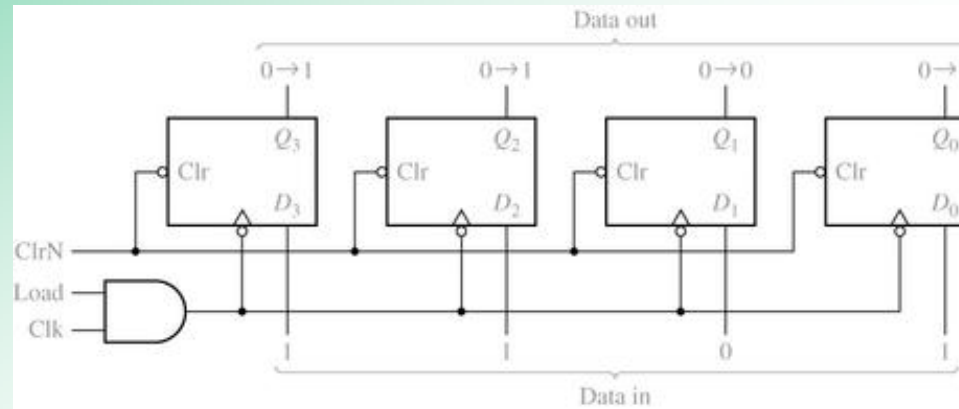12-1 Registers and Register Transfers


Registers: a group of FF with a common clock input, used to **store and shift** binary data




(a) Using gated clock

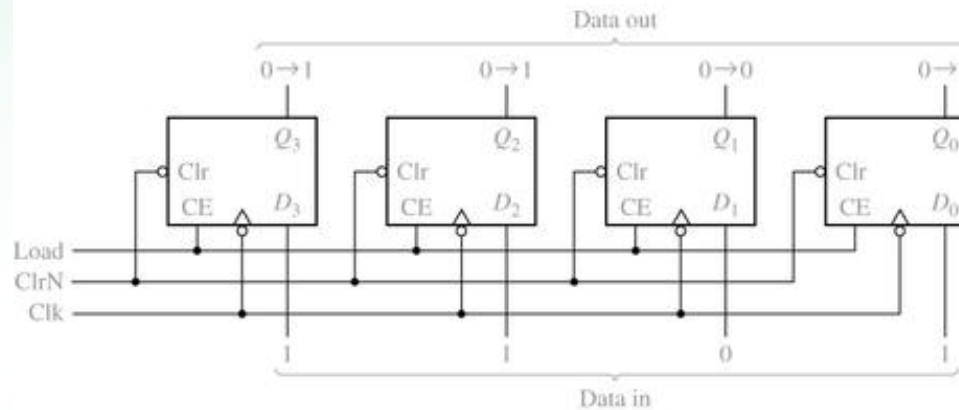

(b) With clock enable


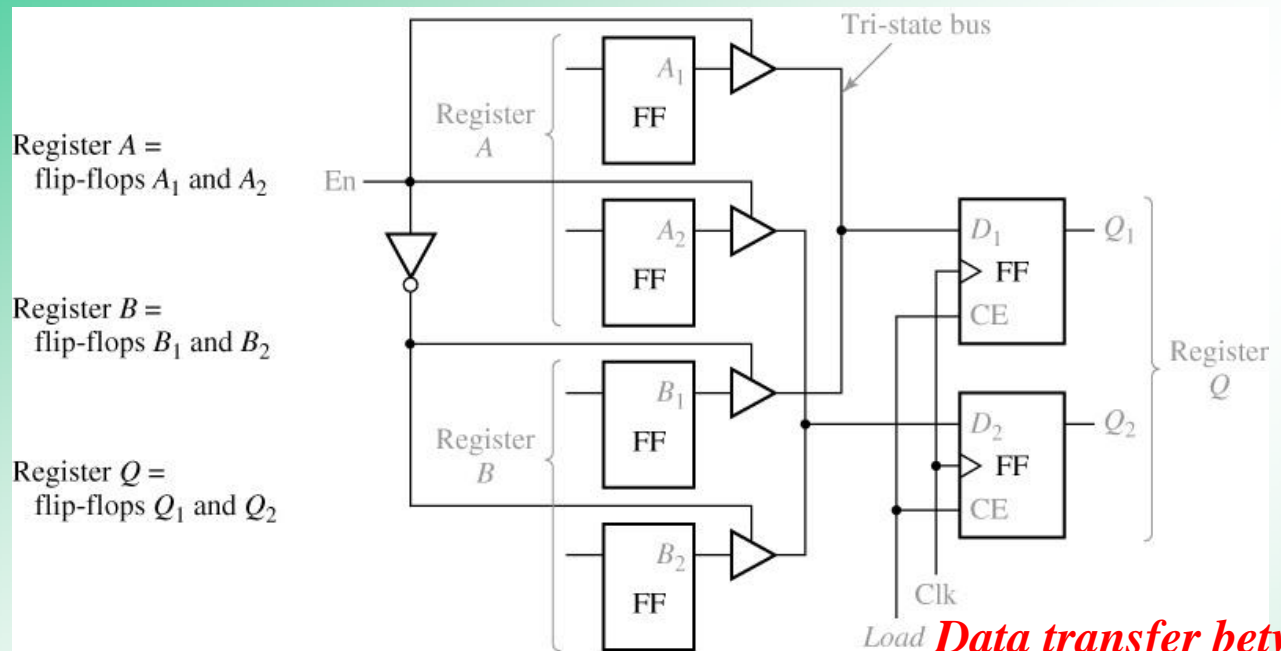


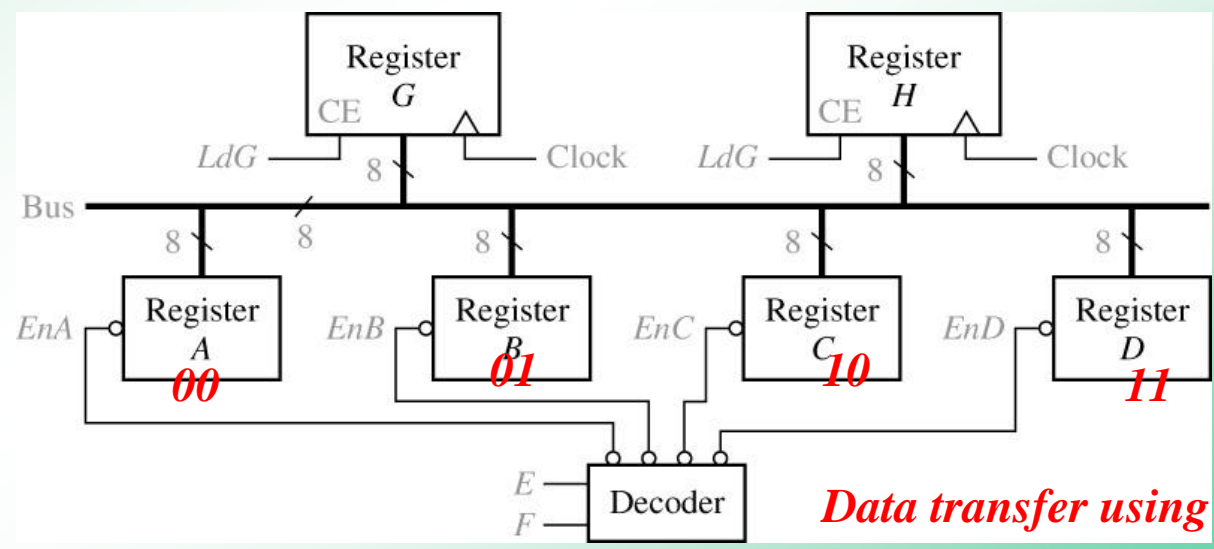*Data transfer between registers
Equiv. to 2:1 MUX*




Data transfer using a tri-state bus

Parallel Adder with Accumulator

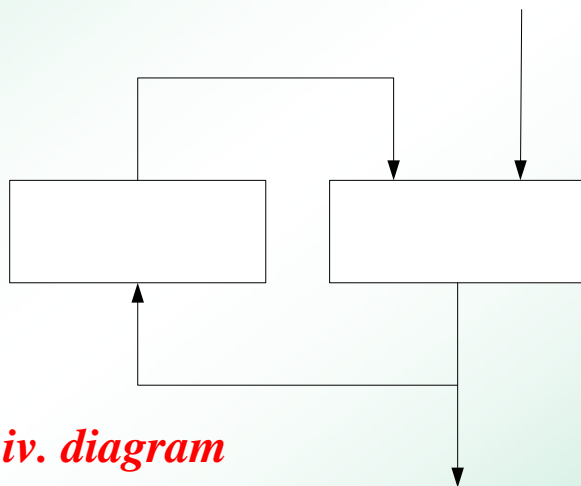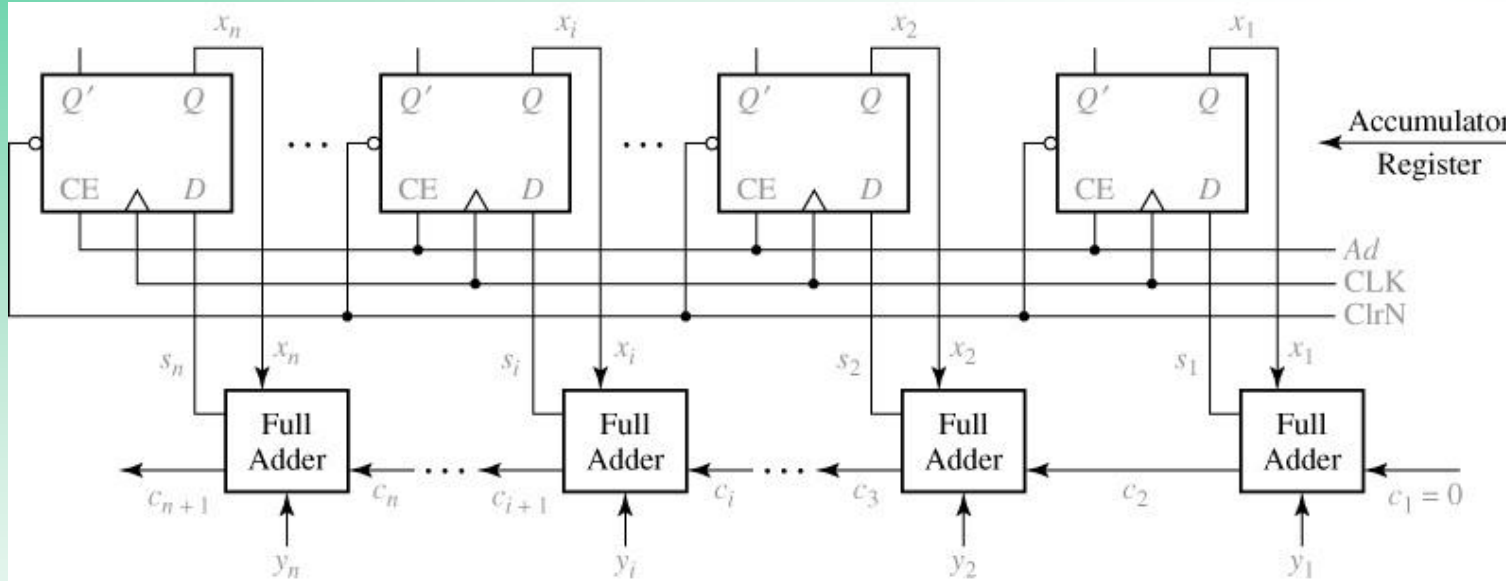



Equiv. diagram

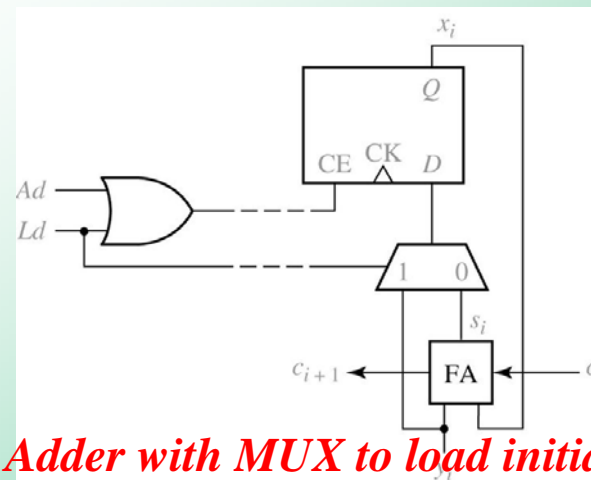


Adder with MUX to load initial value⁶

  12-2 Shift Registers:


A group of F/Fs in which a binary number can be stored. This number can be shifted left or right when a shift signal is applied.




Serial in, Serial out

 

(a) Block diagram

 


(b) Logic diagram

 


Take (n-1) cycles to output for n-bit shift registers

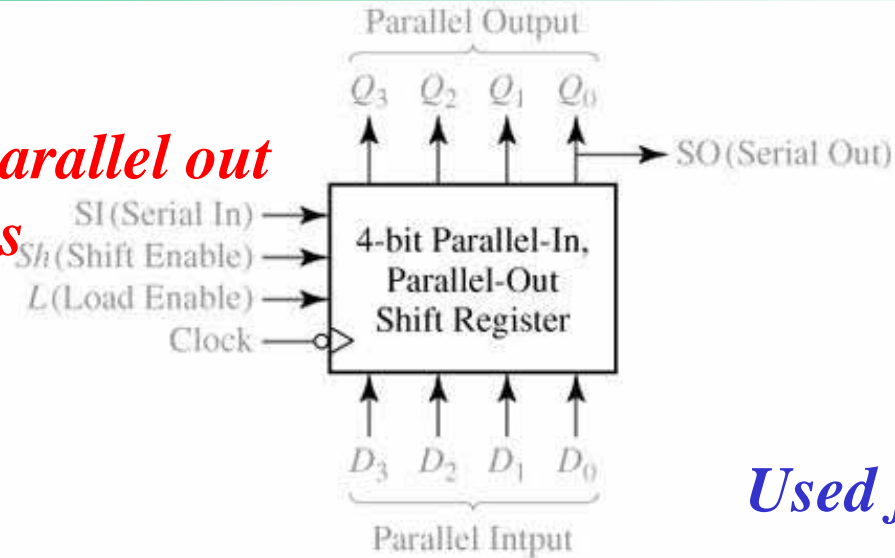**Parallel in, parallel out
Shift registers**




Used for Parallel to serial conversion


(a) Block diagram

 

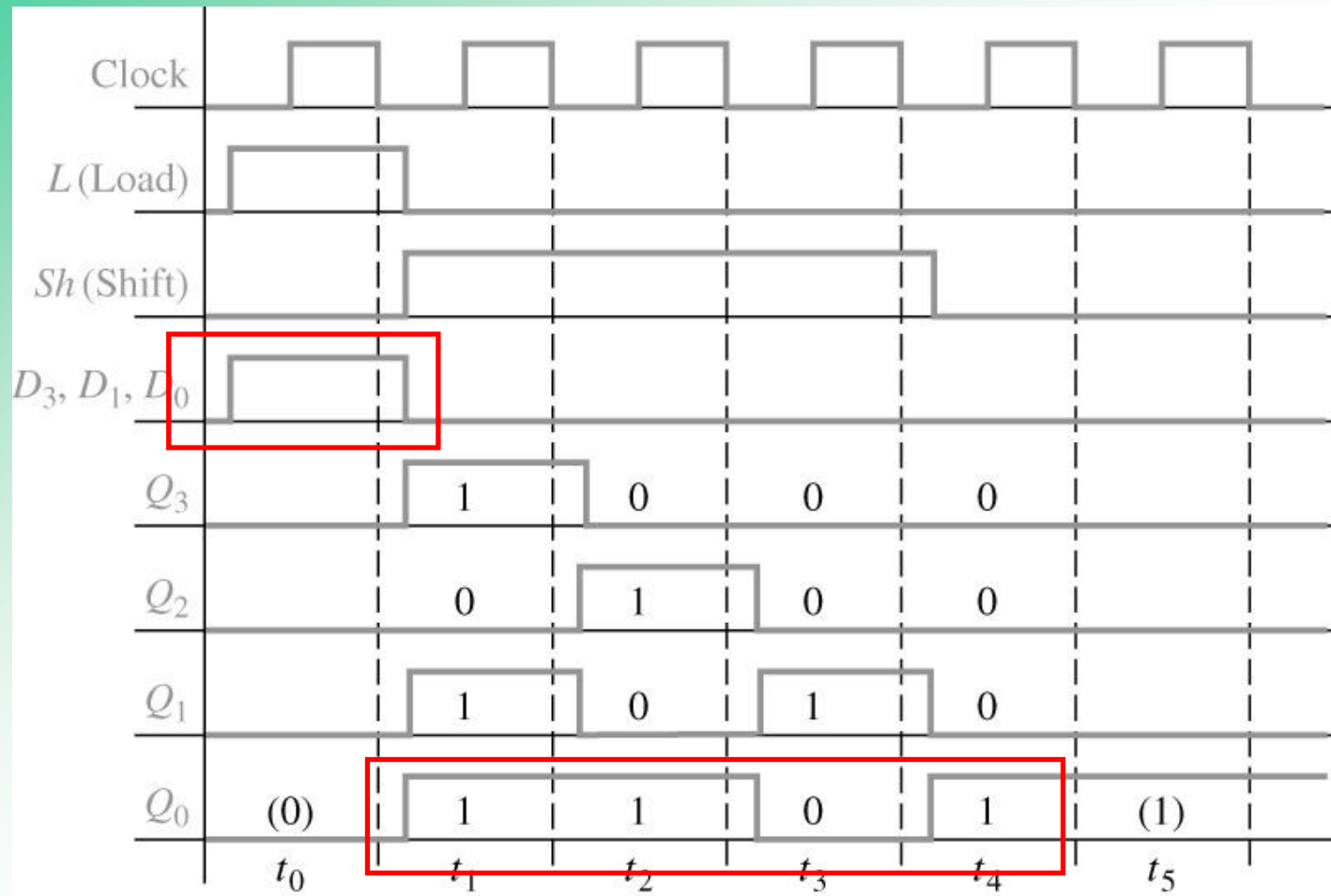(b) Implementation using flip-flops and MUXes




 *Used for Parallel to serial conversion
e.g. convert parallel 1011 to serial 1101*



*Counter: circuit that cycles through a **fixed** sequence of states*
*Johnson counter: shift register with **inverted feedback***

12-3 Design of a Binary Counter

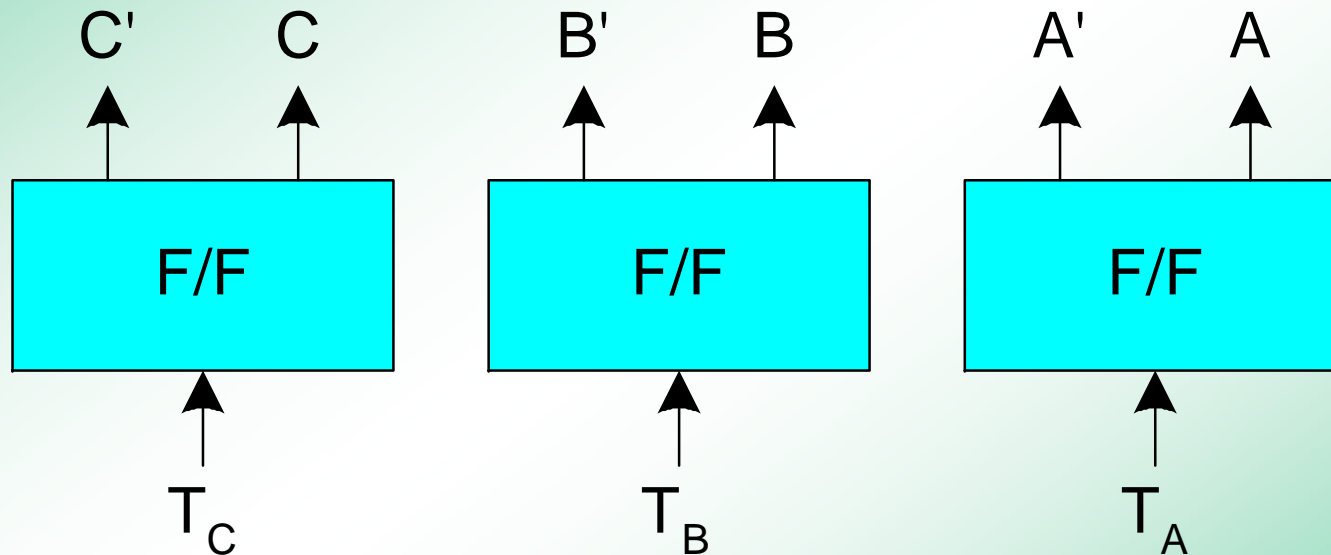


CBA : 000 \rightarrow 001 \rightarrow 010 \rightarrow 011 \rightarrow 100 \rightarrow 101 \rightarrow 110 \rightarrow 111

Synchronous Counter
triggered by a clock 12

CBA : $000 \rightarrow 001 \rightarrow 010 \rightarrow 011 \rightarrow 100 \rightarrow 101 \rightarrow 110 \rightarrow 111$

state graph

 


Systematic method: state table

Q	Q^+	T
0	0	0
0	1	1
1	0	1
1	1	0

Cur. state			Next state			F/F inputs		
C	B	A	C^+	B^+	A^+	T_C	T_B	T_A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1


Tips: $T = 1$ iff $Q \neq Q^+$

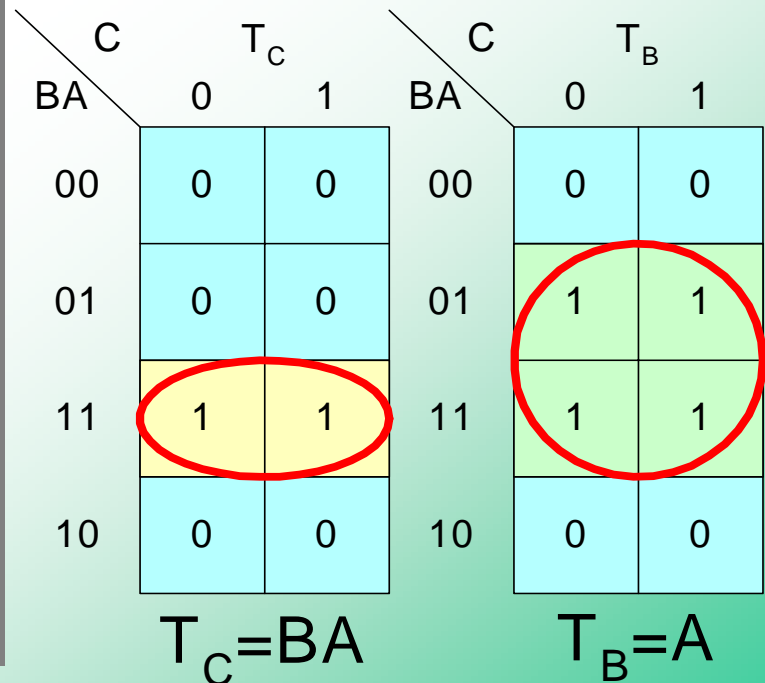


Binary counter with D F/F

Tips: $Q_+ = D$


C	B	A	C^+	B^+	A^+
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

 


$$D_C = C \oplus BA$$

 

$$D_B = B \oplus A$$

 


$$D_A = A'$$

 

Up-down counter

 State graph: $U, D = (1, 1)$ is not allowed





C	B	A	$U=1$ C^+	B^+	A^+	$D=1$ C^+	B^+	A^+
0	0	0	0	0	1	1	1	1
0	0	1	0	1	0	0	0	0
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	1	1	0	1	0	0
1	1	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	0

$$D_A = A \oplus (U+D)$$

$$D_B = B \oplus (UA+DA')$$

$$D_C = C \oplus (UBA+DB'A')$$

Loadable counter

  


Binary counter

12-4 Counters for Other Sequences



Ex.

state graph

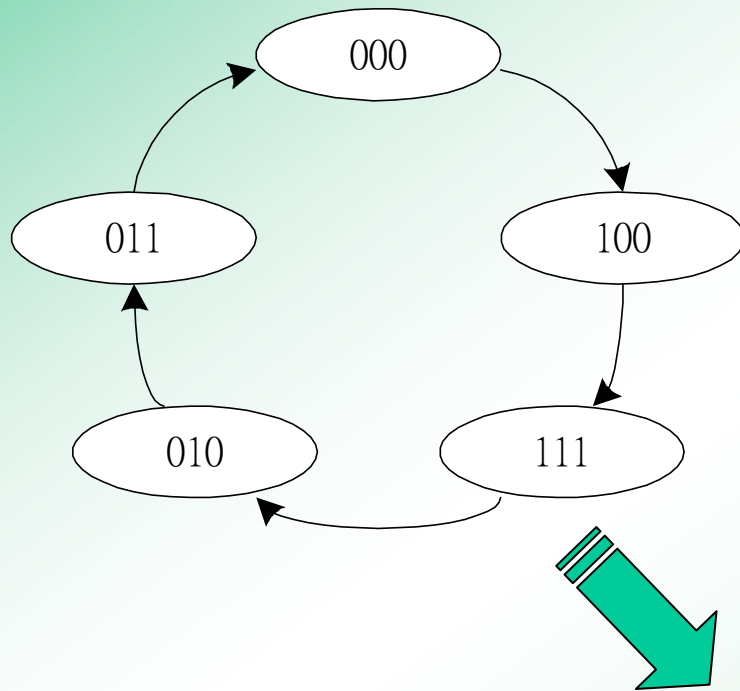


state			table					
C	B	A	C ⁺	B ⁺	A ⁺	T _C	T _B	T _A
0	0	0	1	0	0	1	0	0
0	0	1	-	-	-	-	-	-
0	1	0	0	1	1	0	0	1
0	1	1	0	0	0	0	1	1
1	0	0	1	1	1	0	1	1
1	0	1	-	-	-	-	-	-
1	1	0	-	-	-	-	-	-
1	1	1	0	1	0	-	-	-

Unspecified
Don't care
1 0 status

  

Use T-F/F to implement Next State Maps

state table					
C	B	A	C ⁺	B ⁺	A ⁺
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

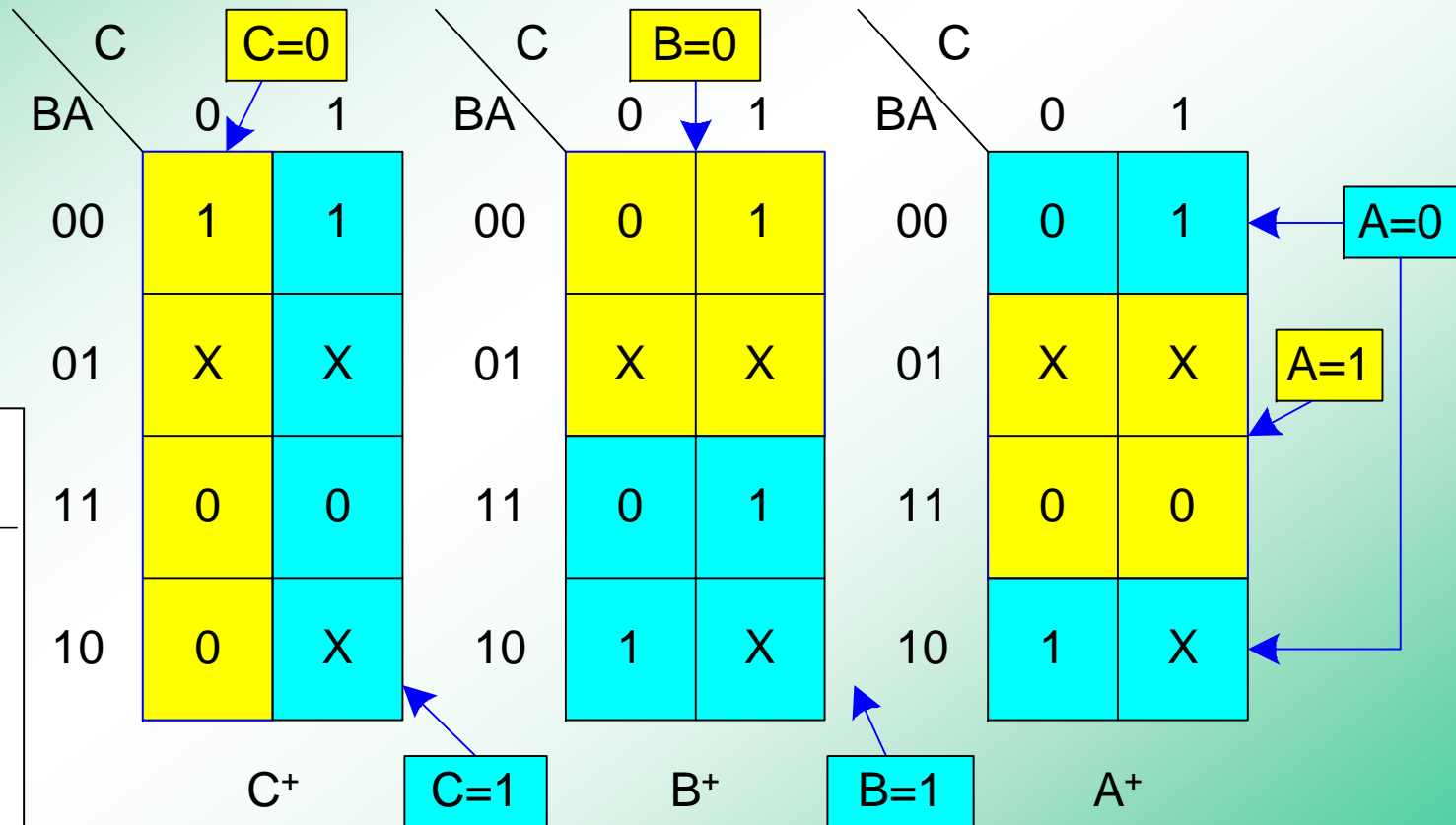

Derive T Maps from Next State Maps

	C	T_C	
		0	1
BA	00	1	0
	01	X	X
	11	0	1
	10	0	X

$$T_C = C'B' + CB$$

$$= (C' + B)(C + B')$$

	C	T_B	
		0	1
BA	00	0	1
	01	X	X
	11	1	0
	10	0	X

$$T_B = C'A + CB'$$


$$= (C' + B')(C + A)$$

	C	T_A	
		0	1
BA	00	0	1
	01	X	X
	11	1	1
	10	1	X

$$T_A = C + B$$

statetable			
C	B	A	
0	0	0	T_C T_B T_A
0	0	1	1 0 0
0	1	0	- - -
0	1	1	0 0 1
1	0	0	0 1 1
1	0	1	- - -
1	1	0	- - -
1	1	1	1 0 1

Implementation

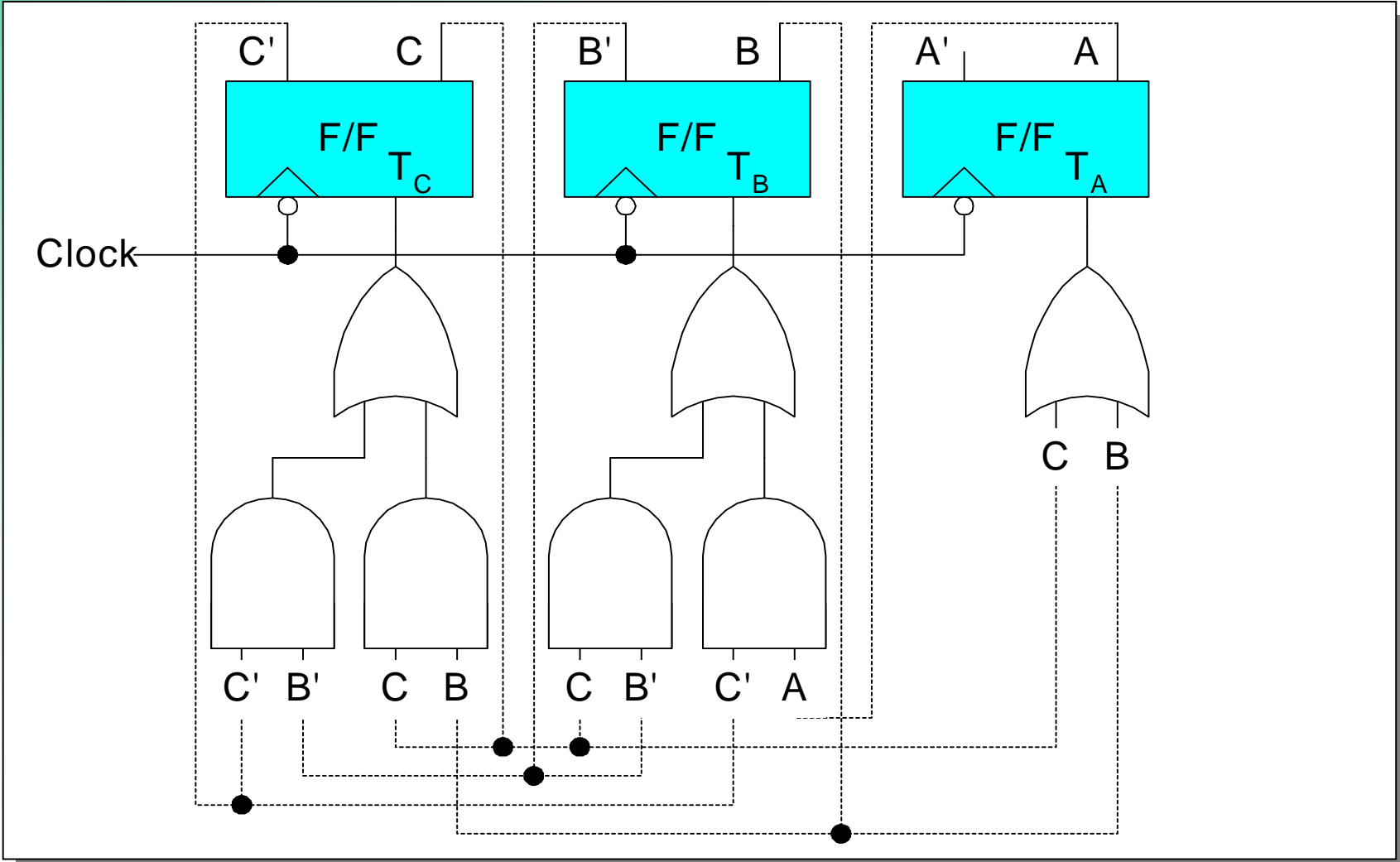


Timing Diagram

$$T_C = C'B' + CB$$

$$T_B = C'A + CB'$$

$$T_A = C + B$$

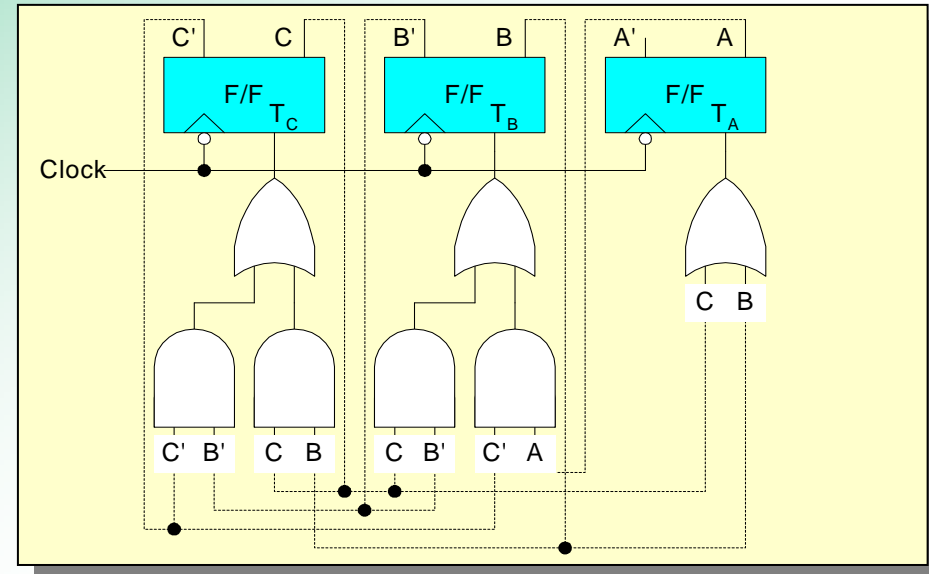

P						
C	0	1	1	0	0	0
B	0	0	1	1	1	0
A	0	0	1	0	1	0
T_C						
T_B						
T_A						

Derive T Maps from Next State Maps

	C	T_C	
BA		0	1
00		1	0
01		X	X
11		0	1
10		0	X

$$T_C = C'B' + CB$$

$$= (C' + B)(C + B')$$

	C	T_B	
BA		0	1
00		0	1
01		X	X
11		1	0
10		0	X

$$T_B = C'A + CB'$$

$$= (C' + B')(C + A)$$

	C	T_A	
BA		0	1
00		0	1
01		X	X
11		1	1
10		1	X


$$T_A = C + B$$

statetable								
C	B	A	C'	B'	A'	T_C	T_B	T_A
0	0	0	1	0	0	1	0	0
0	0	1	1	1	-	1	1	-
0	1	0	0	1	1	0	0	1
0	1	1	0	0	0	0	1	1
1	0	0	1	1	1	0	1	1
1	0	1	-	1	0	-	1	1
1	1	0	0	-	1	1	-	1
1	1	1	0	1	0	1	0	1

In the design process, the next states of states 001, 101, 110 have been specified, even though they are originally not specified.

(This needs to be checked)

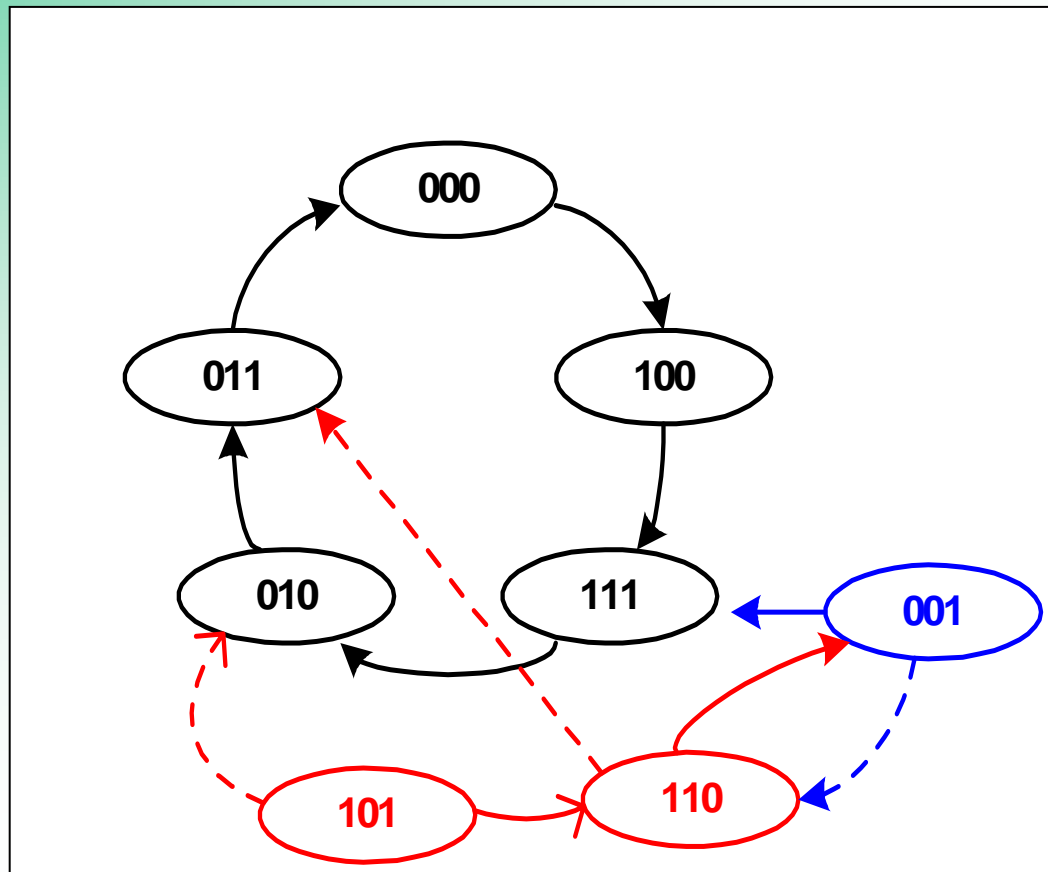∴ Initial power-up may lead to unpredictable states




state table

C	B	A	C ⁺	B ⁺	A ⁺	T _C	T _B	T _A
0	0	0	1	0	0	1	0	0
0	0	1	1	1	-	1	1	-
0	1	0	0	1	1	0	0	1
0	1	1	0	0	0	0	1	1
1	0	0	1	1	1	0	1	1
1	0	1	-	1	0	-	1	1
1	1	0	0	-	1	1	-	1
1	1	1	0	1	0	1	0	1

不可有之情形

進不了main counting loop

 


Using D-F/F's

C	B	A	C^+	B^+	A^+	D_C	D_B	D_A
0	0	0	1	0	0	1	0	0
0	0	1	—	—	—	X	X	X
0	1	0	0	1	1	0	1	1
0	1	1	0	0	0	0	0	0
1	0	0	1	1	1	1	1	1
1	0	1	—	—	—	X	X	X
1	1	0	—	—	—	X	X	X
1	1	1	0	1	0	0	1	0

Q	Q^+	D
0	0	0
0	1	1
1	0	0
1	1	1

D-F/F excitation table

Realization

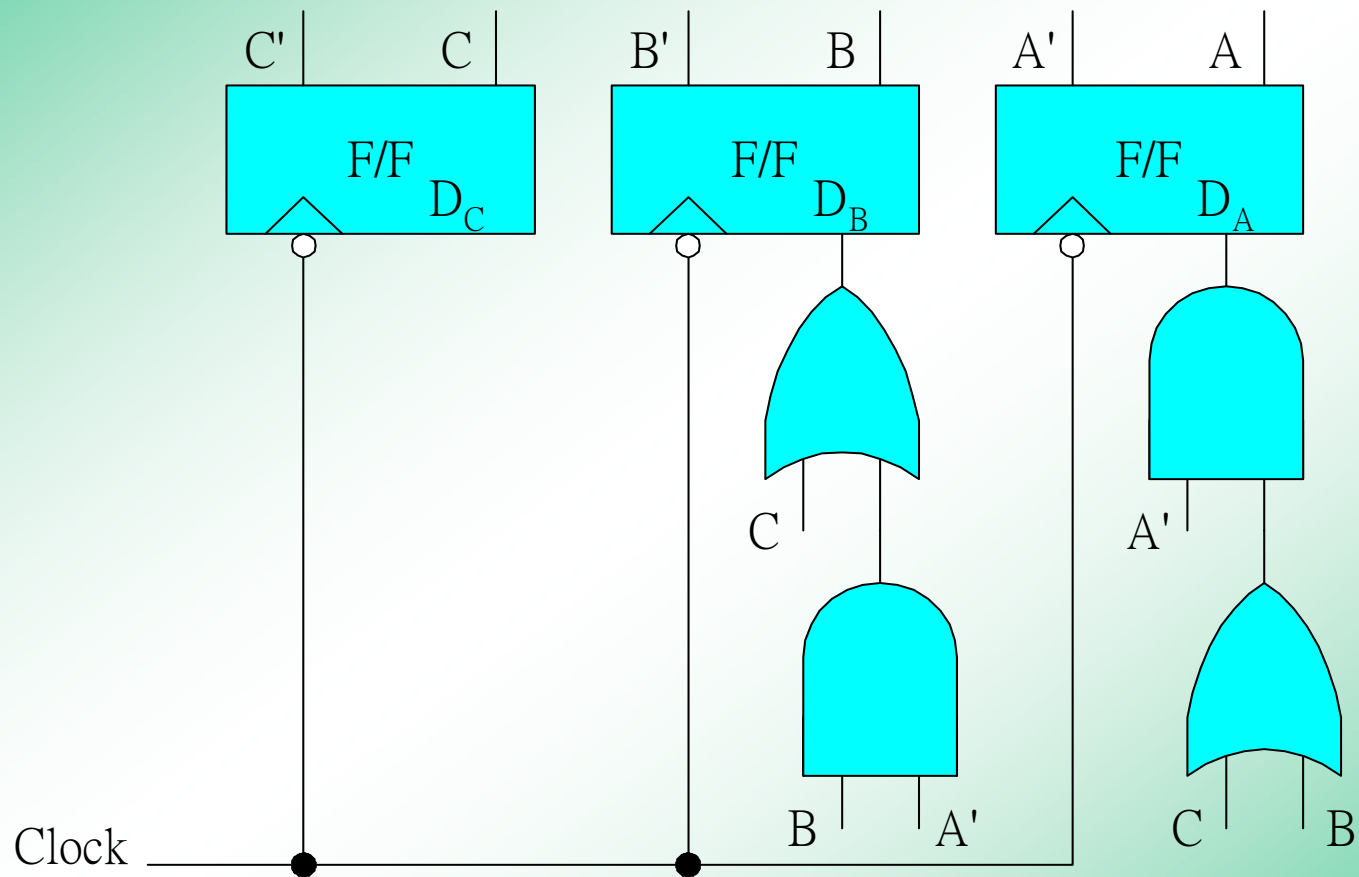


$$D_C = C^+ = \bar{B}$$

$$D_B = B^+ = A + \bar{B}\bar{C}$$


$$D_A = C^+ = \bar{C}\bar{A} + B\bar{A} = \bar{A}(C + B)$$

12-5 Counter Design Using S-R F/Fs

S	R	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	—
1	1	1	—

 

Q	Q^+	S	R
0	0	$\left\{ \begin{array}{l} 0 \\ 0 \end{array} \right.$	$\left\{ \begin{array}{l} 0 \\ 1 \end{array} \right.$
0	1	1	0
1	0	0	1
1	1	$\left\{ \begin{array}{l} 0 \\ 1 \end{array} \right.$	$\left\{ \begin{array}{l} 0 \\ 0 \end{array} \right.$

 

Q	Q^+	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

$Q^+ = S + \bar{R}Q$

Excitation Table

Design the previous example by using SR F/F

Get them by referencing excitation table



A	B	C	A^+	B^+	C^+	S_C	R_C	S_B	R_B	S_A	R_A
0	0	0	1	0	0	1	0	0	X	0	X
0	0	1	—	—	—	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	0
0	1	1	0	0	0	0	X	0	1	0	1
1	0	0	1	1	1	X	0	1	0	1	0
1	0	1	—	—	—	X	X	X	X	X	X
1	1	0	—	—	—	X	X	X	X	X	X
1	1	1	0	1	0	0	1	X	0	0	1

Q	Q^+	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

Using K-map method

		C	
		0	1
BA	00	0	0
	01	X	X
	11	X	1
	10	X	X

$$R_C = A$$

		C	
		0	1
BA	00	1	X
	01	X	X
	11	0	0
	10	0	X

$$S_C = B'$$



Similarly :

$$R_B = C' A, \quad S_B = C$$


$$R_A = A, \quad S_A = CA' + BA' = A'(C + B)$$

Directly use next state map to derive K-map for $R_C, S_C, R_B, S_B, R_A, S_A$ by referencing

Q	Q^+	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

 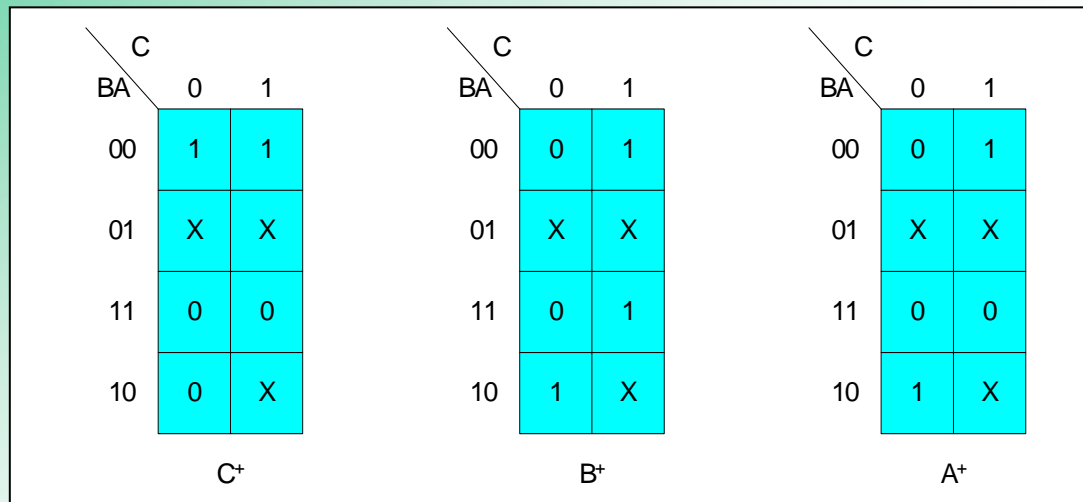

Realization of Logic Circuit

 

§ Counter Design Using J-K F/F


Q	Q^+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

**JK-F/F
excitation table**

C	B	A	C^+	B^+	A^+	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	1	0	0	1	X	0	X	0	X
0	0	1	–	–	–	X	X	X	X	X	X
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	0	0	0	0	X	X	1	X	1
1	0	0	1	1	1	X	0	1	X	1	X
1	0	1	–	–	–	X	X	X	X	X	X
1	1	0	–	–	–	X	X	X	X	X	X
1	1	1	0	1	0	X	1	X	0	X	1

$$J_C = B' \quad K_C = A \quad J_B = C \quad K_B = C'A \quad J_A = C+B \quad K_A = 1$$

Realization

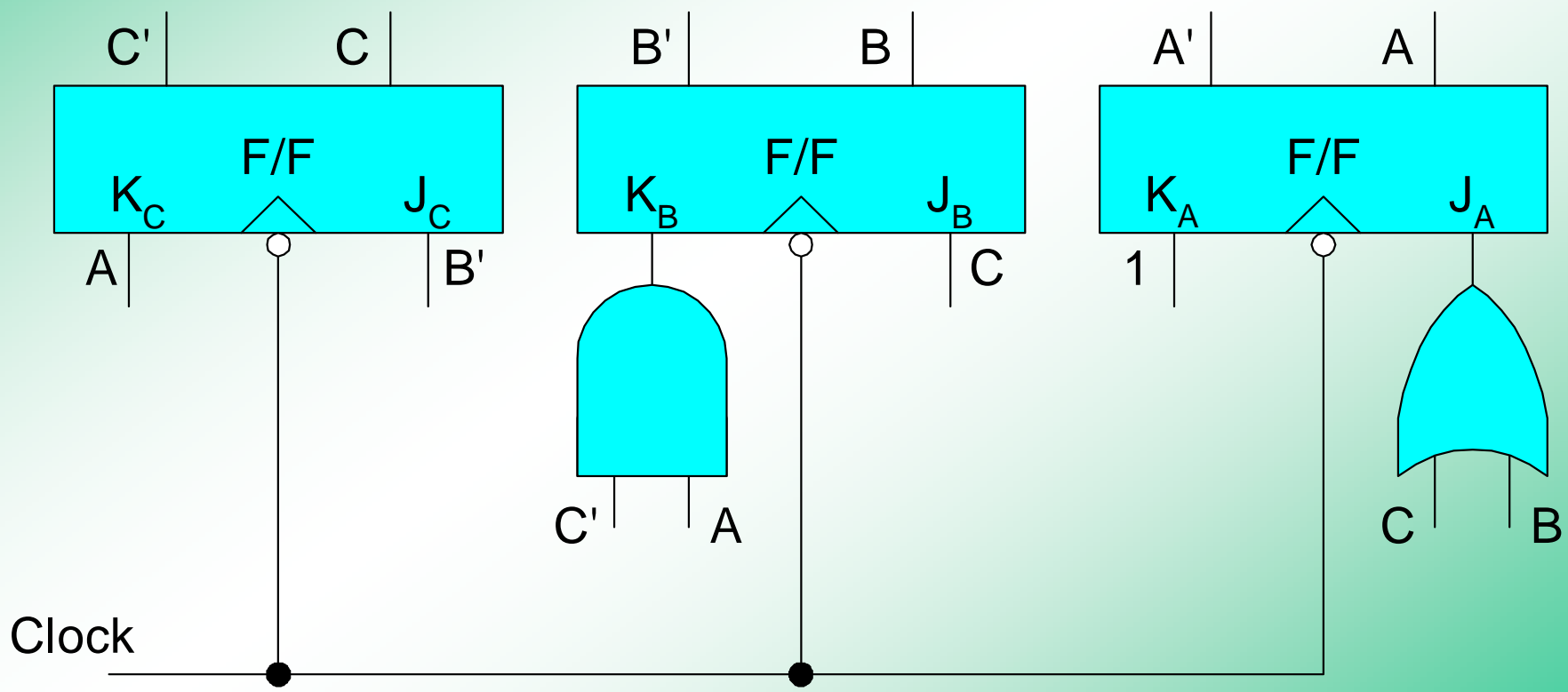

12-6 Summary

how to derive F/F input equations

Type of FF	Input	Q=0		Q=1		Rules	
		Q+=0	Q+=1	Q+=0	Q+=1	Q=0 half	Q=1 half
Delay	D	0	1	0	1	No change	No change
Trigger	T	0	1	1	0	No change	Complement
Set-Reset	S	0	1	0	X	No change	Replace 1's with X's
	R	X	0	1	0	Replace 0's with X's	Complement
J-K	J	0	1	X	X	No change	Fill in with X's
	K	x	x	1	0	Fill in with X's	complement

Always copy 'x' from the next state map on the input maps first

Sequential circuit design with a single pulse to imitate state changes and no other inputs

Ex. 8421 BCD to Excess-3 code converter

A	B	C	D	A^+	B^+	C^+	D^+
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Initially BCD code stored in F/F. After a clock corresponding Excess-3 code outputs

A	B	C	D	A^+	B^+	C^+	D^+	J_A	K_A	J_B	K_B	J_C	K_C	J_D	K_D
0	0	0	0	0	0	1	1	0	X	0	X				
0	0	0	1	0	1	0	0	0	X	1	X				
0	0	1	0	0	1	0	1	0	X	1	X				
0	0	1	1	0	1	1	0	0	X	1	X				
0	1	0	0	0	1	1	1	0	X	X	0				
0	1	0	1	1	0	0	0	1	X	X	1				
0	1	1	0	1	0	0	1	1	X	X	1				
0	1	1	1	1	0	1	0	1	X	X	1				
1	0	0	0	1	0	1	1	X	0	0	X				
1	0	0	1	1	1	0	0	X	0	1	X				

Q	Q^+	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

$$J_A = BC + BD = B(C + D)$$

$$K_A = 0$$

$$J_B = C + D$$

$$K_B = C + D$$


$$J_C = \bar{D}$$

$$K_C = \bar{D}$$

$$J_D = 1$$

$$K_D = 1$$

Ex. 8421 BCD to Excess-3 code converter

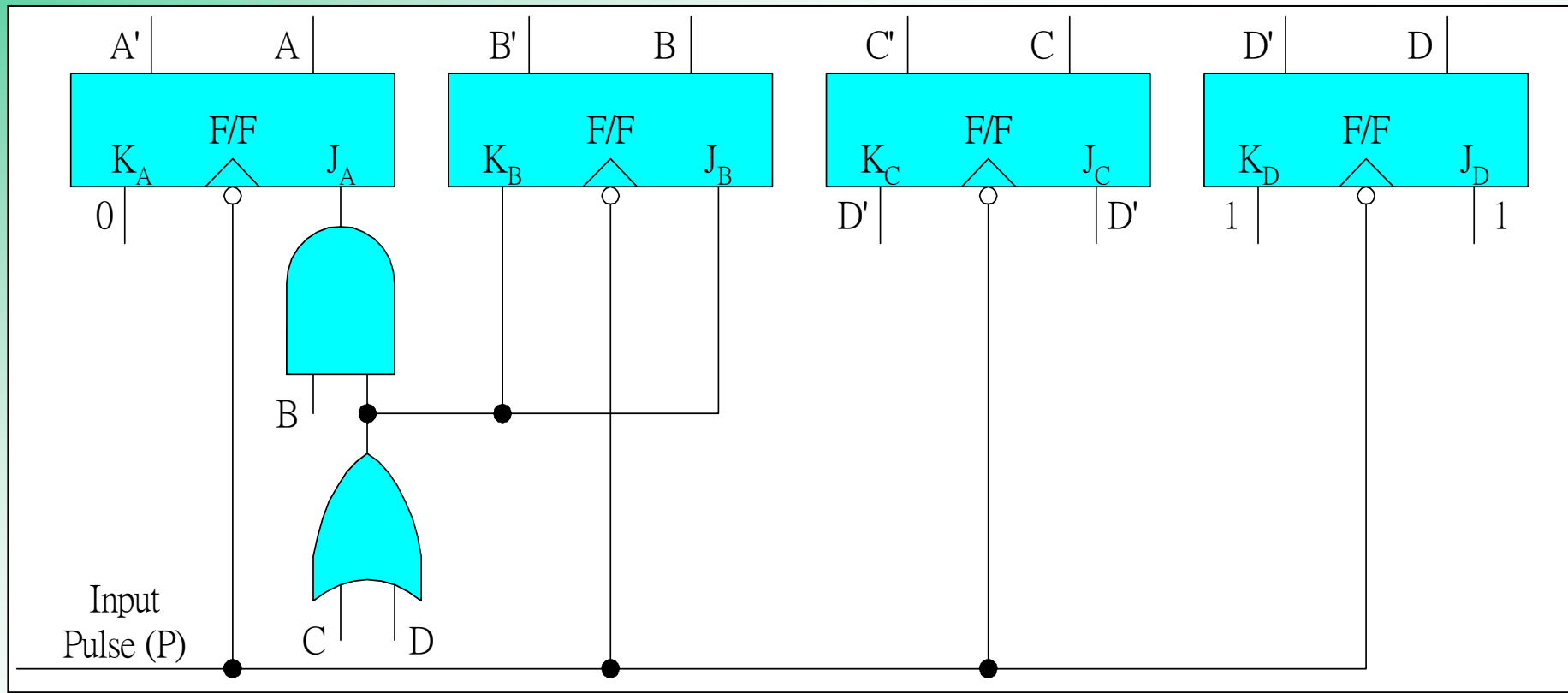

Initially BCD code stored in F/F.
 After a clock corresponding Excess-3 code outputs.

HOMework -- Unit 12

- 12.2
- 12.11
- 12.15
- 12.17(b)(e)

