

Chap 14:

Derivation of State Graph and Table


Sequential Circuit Design

- To design a sequential circuit, given a problem statement,
 - 1. construct a **state table or state graph** (unit 14)
 - Further simplification (unit 15)
 - 2. derive FF input eq. and output eq. (in unit 12)

14-1 Design of a Sequence Detector

Given problem statement \Rightarrow state graph
state table

– Mealy Machine –

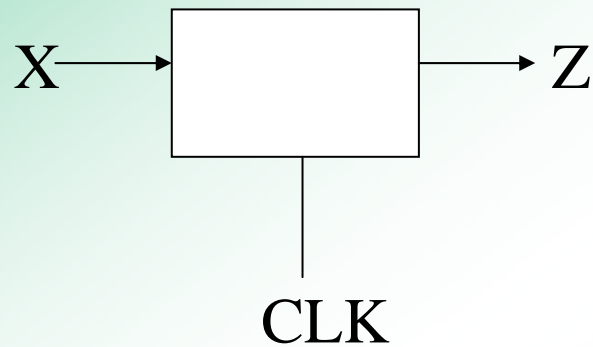

Z gives "1" when X is "101"


X	=	0	0	1	1	0	1	1	0	0	1	0	1	0	1	0	0	
Z	=	0	0	0	0	0	1	0	0	0	0	0	1	0	1	0	0	
(Time	:	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15)

*Construction of state graph


Start with a reset state S_0



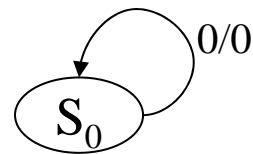S_0 : receives a "0" \Rightarrow stays at S_0 , $Z = 0$



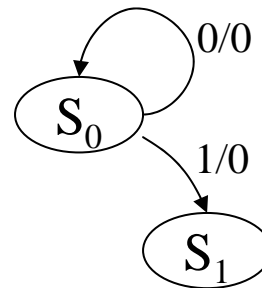receives a "1" \Rightarrow a new state S_1 , $Z = 0$




2






S_1 : receives "0" $\Rightarrow S_2, Z = 0$

010

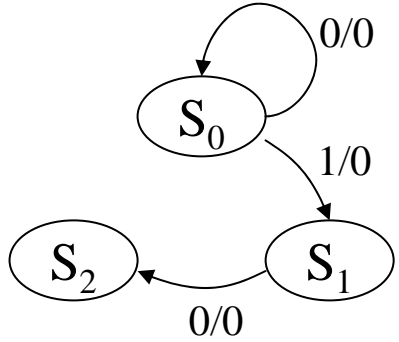

receives "1" $\Rightarrow S_1, Z = 0$

0110

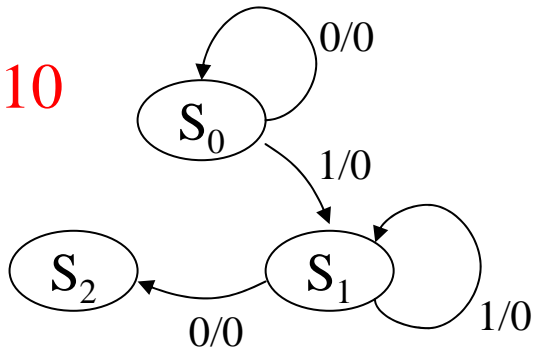


3

Go back to S_1 since it is also the first 1 in new sequence

S_2 : receives "1" $\Rightarrow Z = 1$


and goes back to S_1

0101

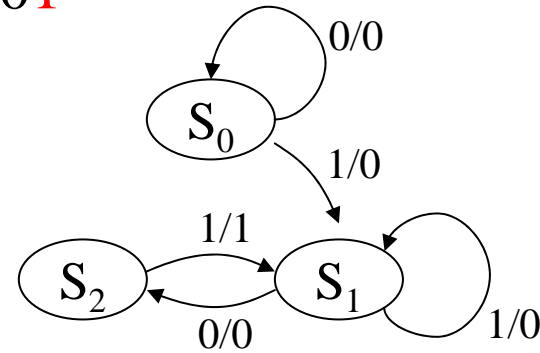

receives "0" $\Rightarrow S_0, Z = 0$

0100

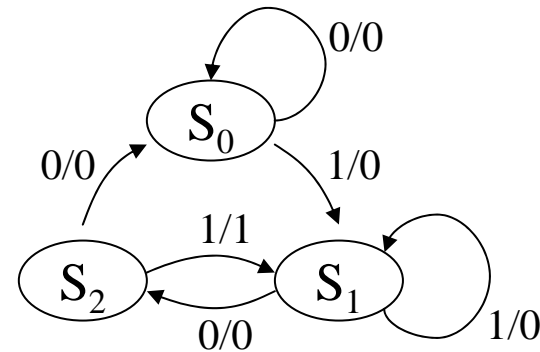

4

Go back to S_0 since 00 is not a part of desired sequence


* State Table

P.S.	N.S.		Output Z	
	X = 0	X = 1	X = 0	X = 1
S ₀	S ₀	S ₁	0	0
S ₁	S ₂	S ₁	0	0
S ₂	S ₀	S ₁	0	1

* State Assignment

A F/F can code 2 states

⇒ 3 states → 2 F/Fs (A, B)

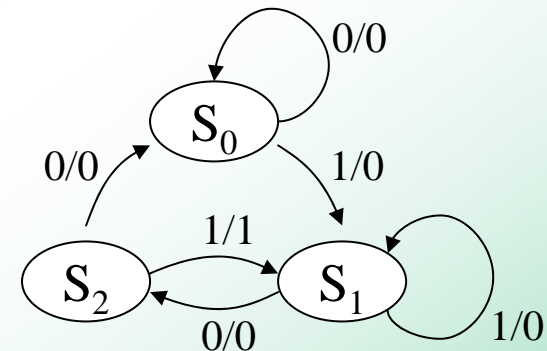

	AB	A+B+		Z	
		X = 0	X = 1	X = 0	X = 1
S ₀ : AB = 00	00	00	01	0	0
S ₁ : AB = 01	01	10	01	0	0
S ₂ : AB = 10	10	00	01	0	1

* Choose F/F

Ex : use D - F/F

AB	A^+B^+		D_A		D_B	
	X = 0	X = 1	X = 0	X = 1	X = 0	X = 1
00	0	0	0	0	0	1
01	1	0	1	0	0	1
10	0	0	0	0	0	1

* K - map Simplification

AB	X	
	0	1
00	0	0
01	1	0
11	x	x
10	0	0

$$A^+ = X'B$$


AB	X	
	0	1
00	0	1
01	0	1
11	x	x
10	0	1

$$B^+ = X$$

AB	X	
	0	1
00	0	0
01	0	0
11	x	x
10	0	1

$$Z = XA$$

* Circuit Realization

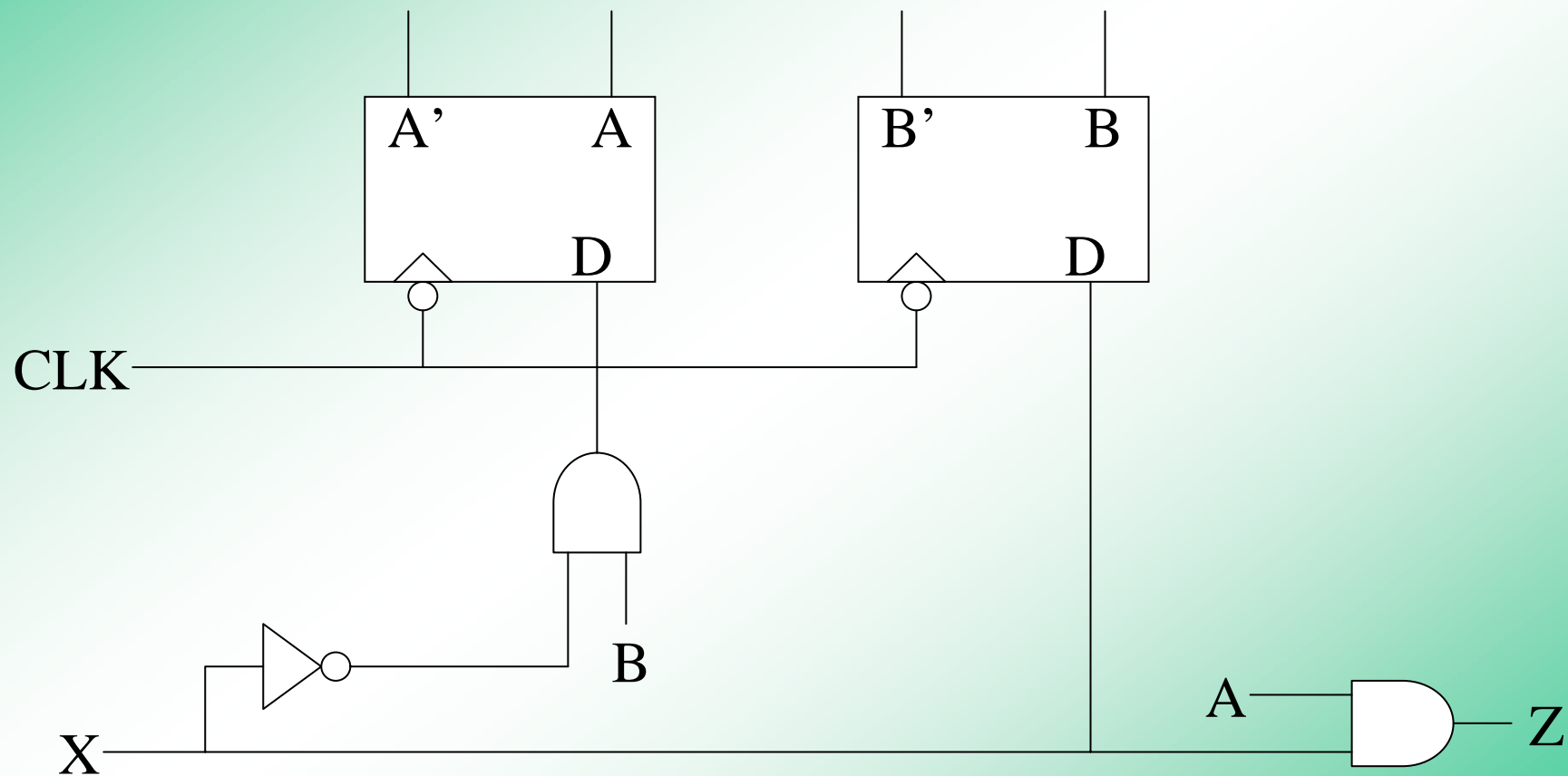


$$A^+ = D_A = X'B \quad B^+ = D_B = X \quad Z = XA$$

– Moore Machine –


*Construction of state graph

Start with a reset state S_0


$S_0: Z = 0$

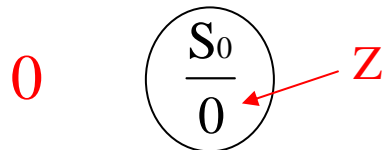


receives "0" $\Rightarrow S_0$

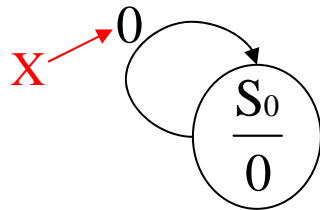

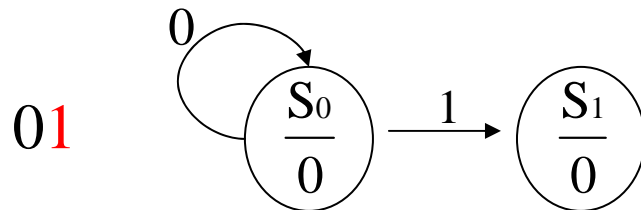receives "1" $\Rightarrow S_1$ ($S_1, Z = 0$)




1

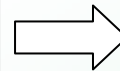


$S_1: Z = 0$

receives "1" $\Rightarrow S_1$

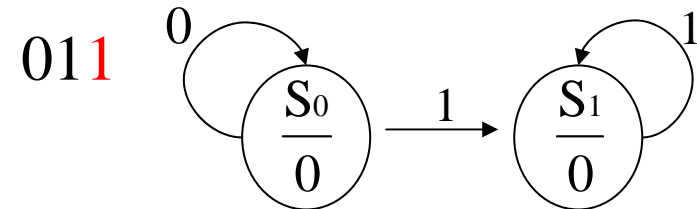


receives "0" $\Rightarrow S_2$ ($Z = 0$)

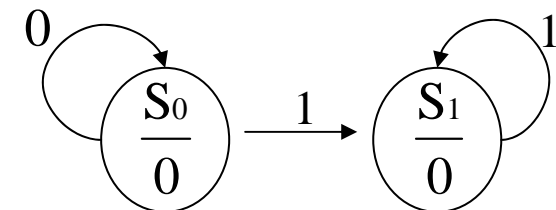




0110

010

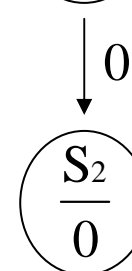


2



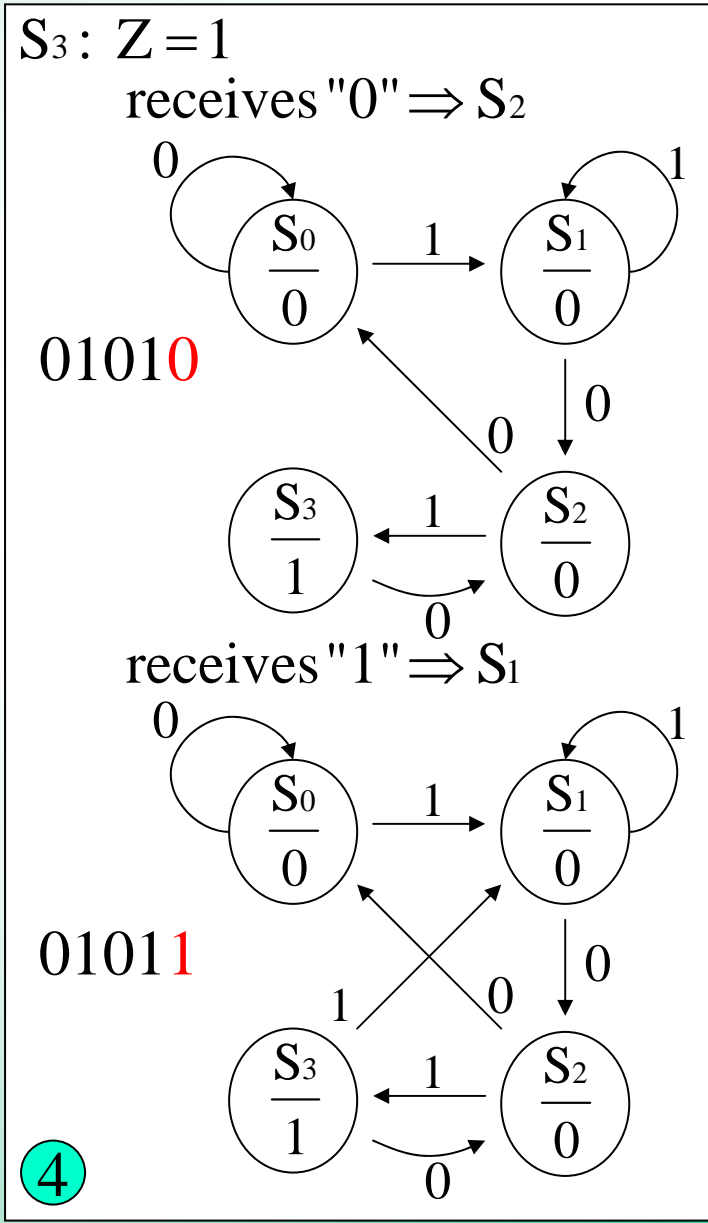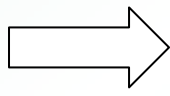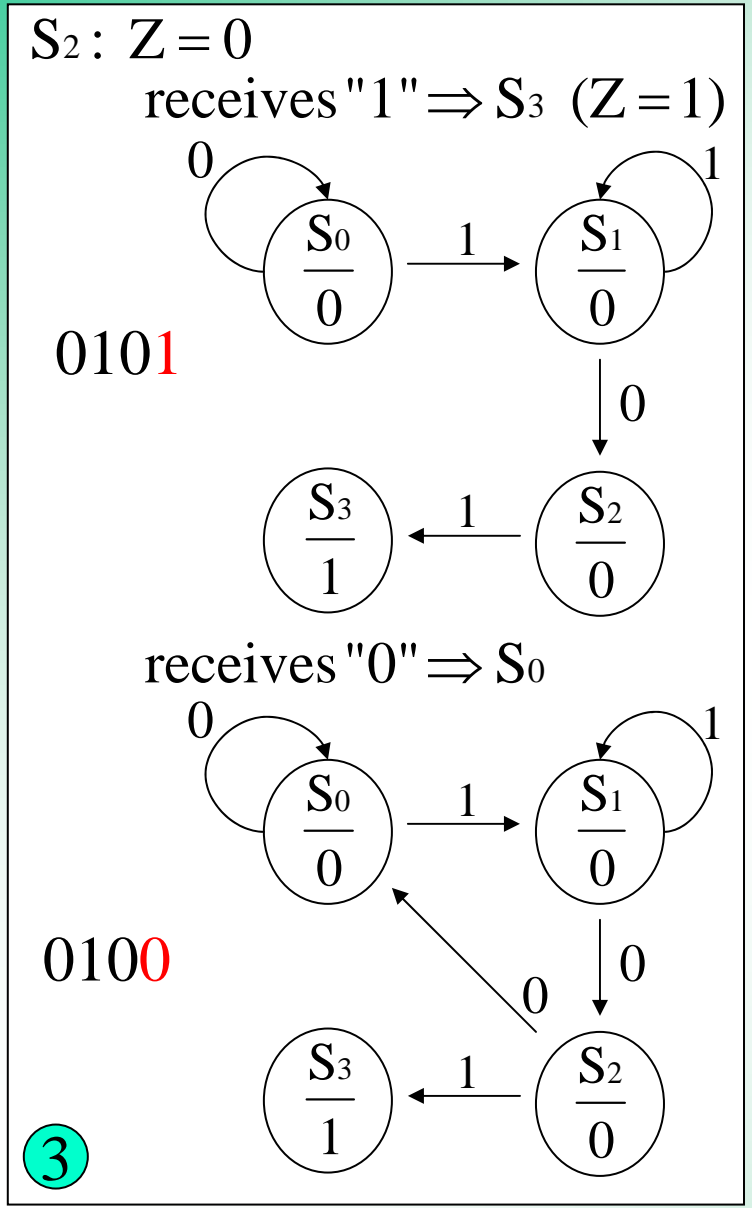

* State Table

P.S.	N.S.		Present Output Z
	X = 0	X = 1	
S ₀	S ₀	S ₁	0
S ₁	S ₂	S ₁	0
S ₂	S ₀	S ₃	0
S ₃	S ₂	S ₁	1

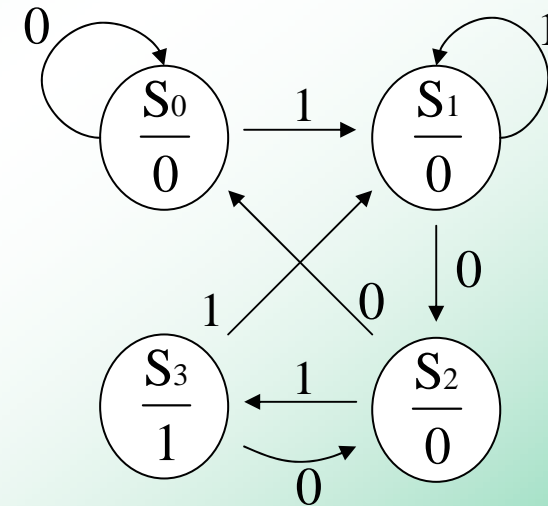

* State Assignment

4 states \Rightarrow 2 F/Fs (A, B)

AB	A+B ⁺		Z
	X = 0	X = 1	
S ₀ 00	00	01	0
S ₁ 01	11	01	0
S ₂ 11	00	10	0
S ₃ 10	11	01	1

* Choose F/F

use D - F/F

AB	A^+B^+				D_A		D_B	
	X = 0		X = 1		X = 0	X = 1	X = 0	X = 1
00	0	0	0	1	0	0	0	1
01	1	1	0	1	1	0	1	1
11	0	0	1	0	0	1	0	0
10	1	1	0	1	1	0	1	1

* K - map Simplification

AB \ X	0	1
00	0	0
01	1	0
11	0	1
10	1	0

$$A^+ = X' A' B + XAB + X' AB'$$

AB \ X	0	1
00	0	1
01	1	1
11	0	0
10	1	1

$$B^+ = XA' + A' B + AB'$$

B \ A	0	1
0	0	1
1	0	0


$$Z = AB'$$

* Circuit Realization

$$A^+ = X'A'B + XAB + X'AB'$$

$$B^+ = XA' + A'B + AB'$$


$$Z = AB'$$

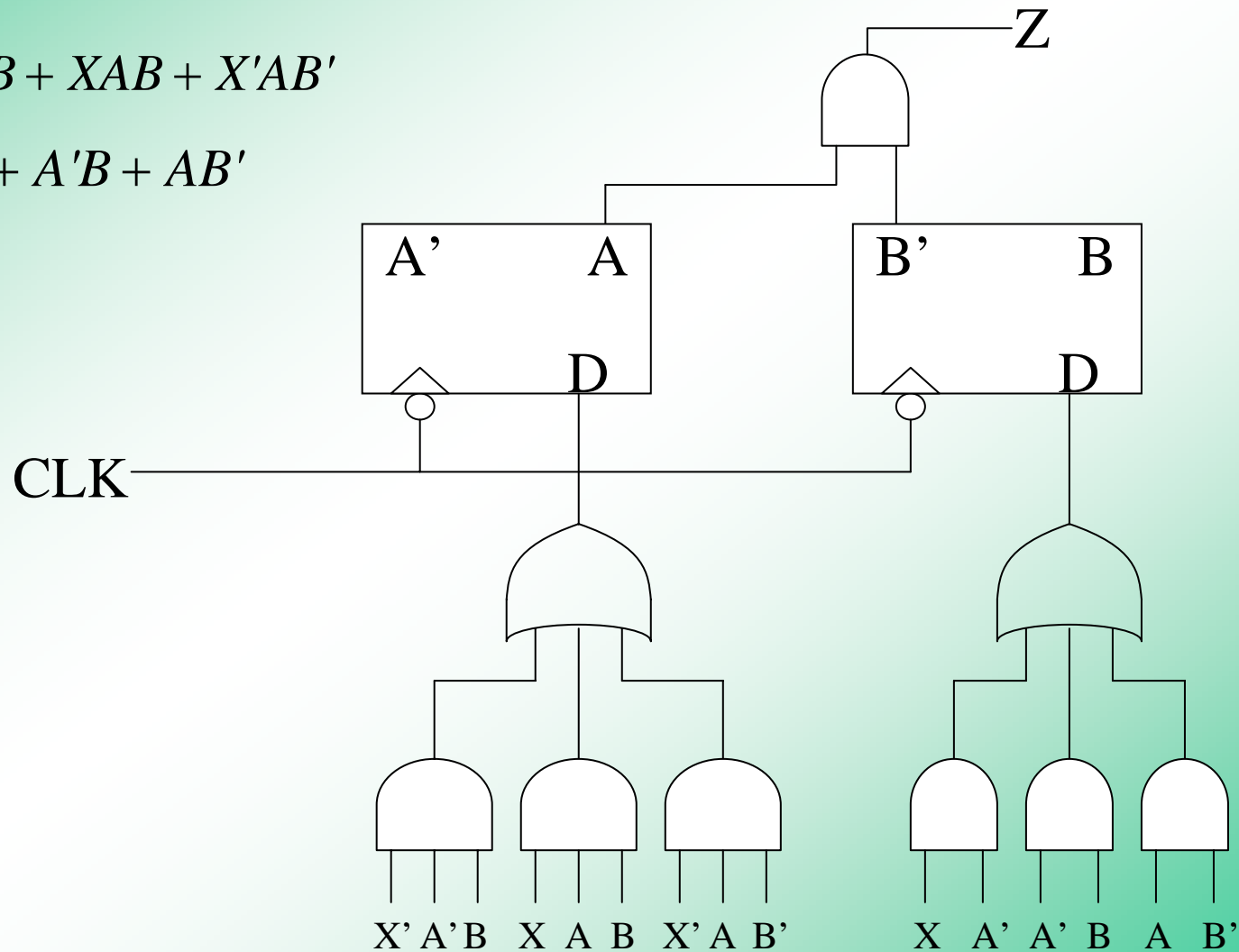

14-2 More Complex Problems


– Mealy Machine Example –

Sequence detector

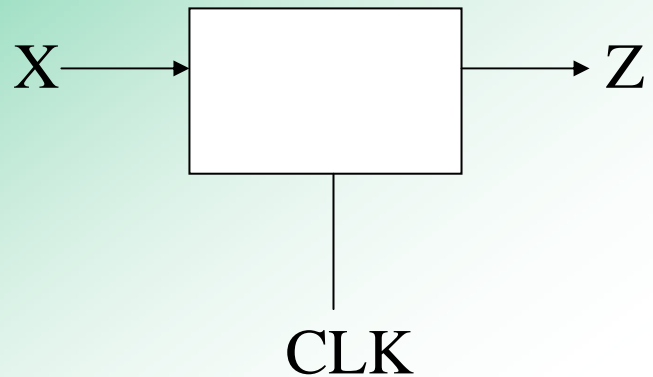


Z gives "1" if X = 010 or 1001
Otherwise, Z = 0


X	=	0	0	1	0	1	0	0	1	0	0	0	1	0	0	1	1	0
Z	=	0	0	0	1	0	1	0	1	1	0	0	0	1	0	1	0	0

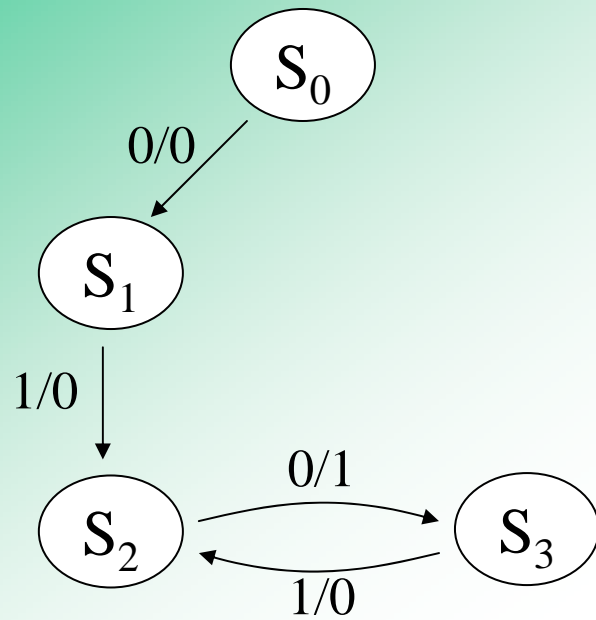

<u>State</u>	<u>Sequence received</u>
S_0	reset
S_1	0
S_2	01
S_3	010


partial state graph construction for 010

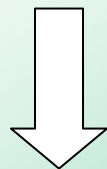

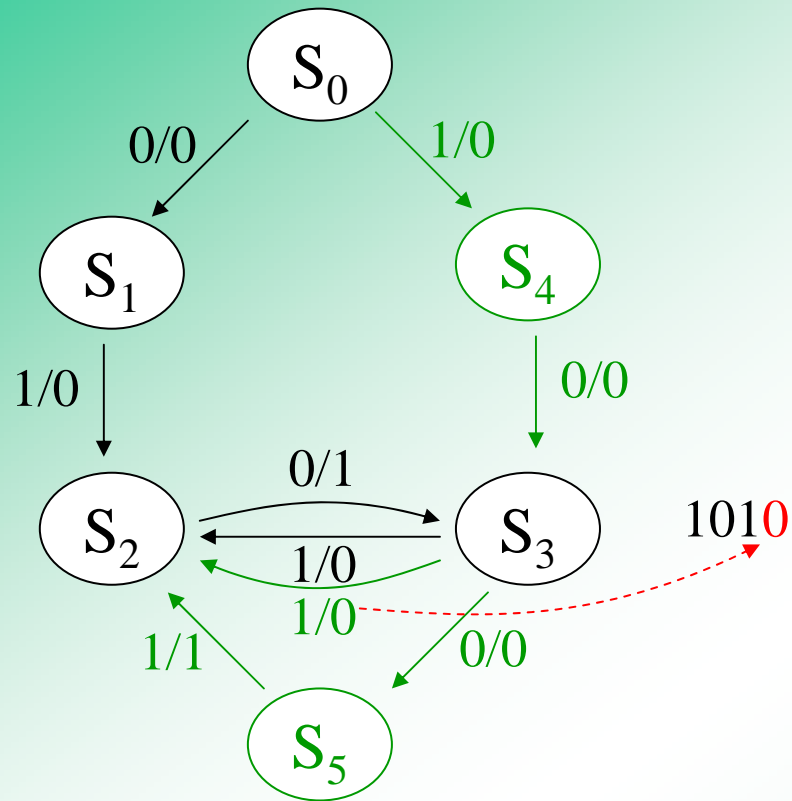


State	Sequence received
S_0	reset
S_1	0
S_2	01
S_3	010 or 10
S_4	1
S_5	100


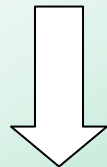
partial state graph construction for 1001





Completion of state graph

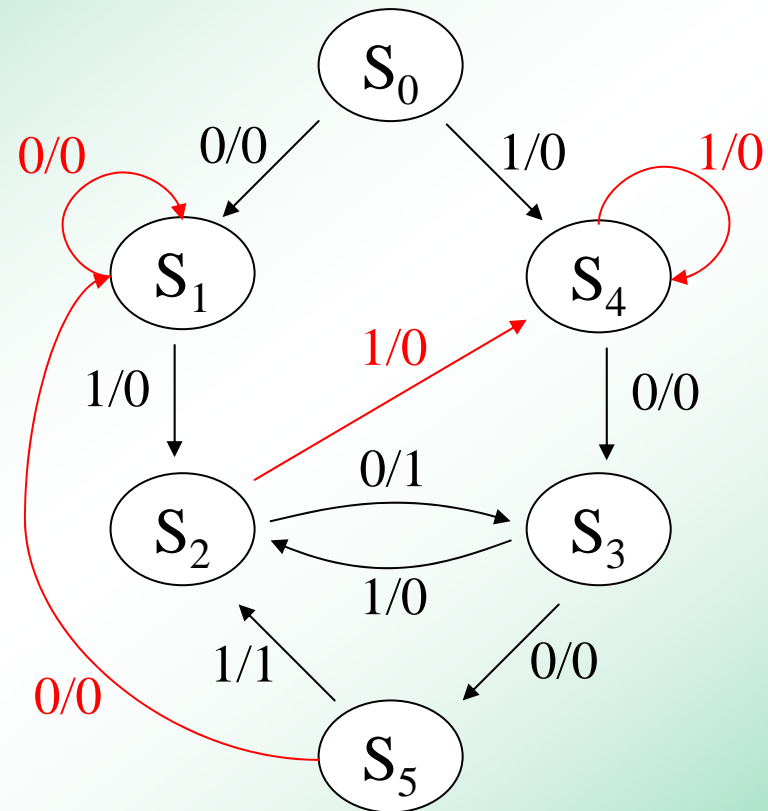



If :

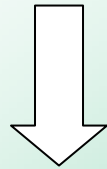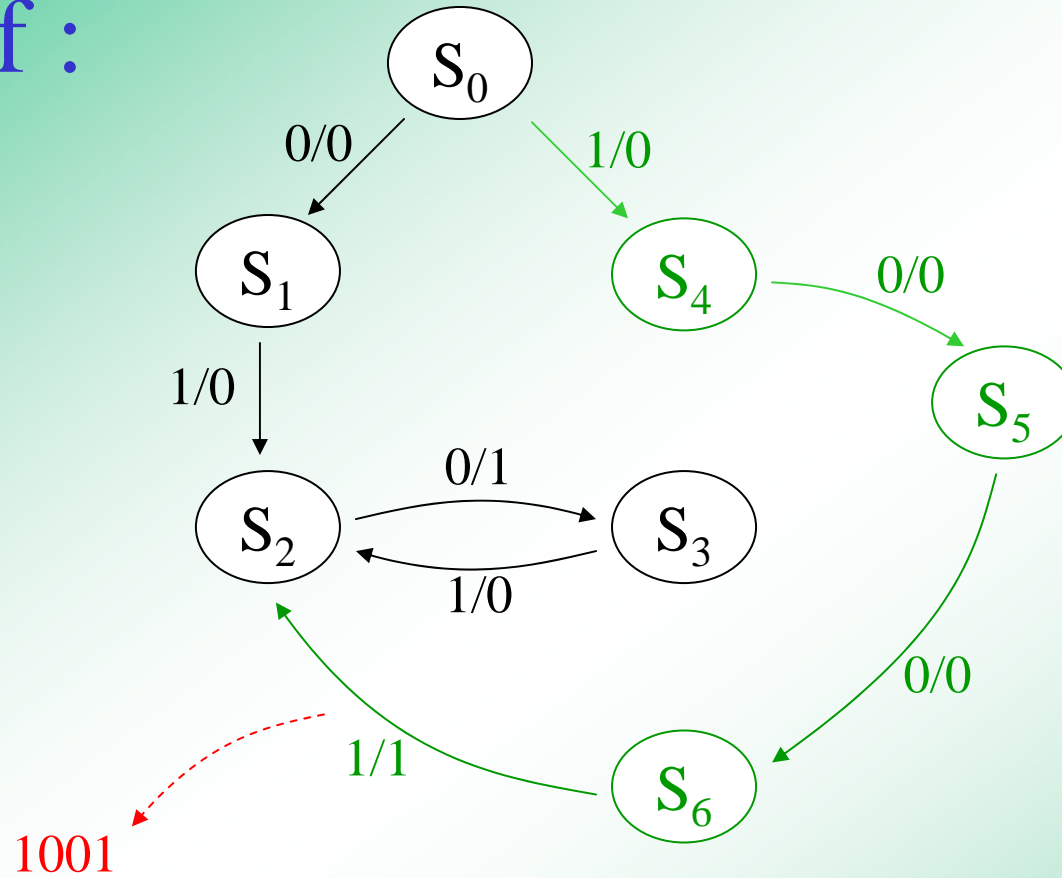


If :

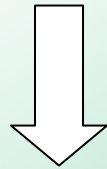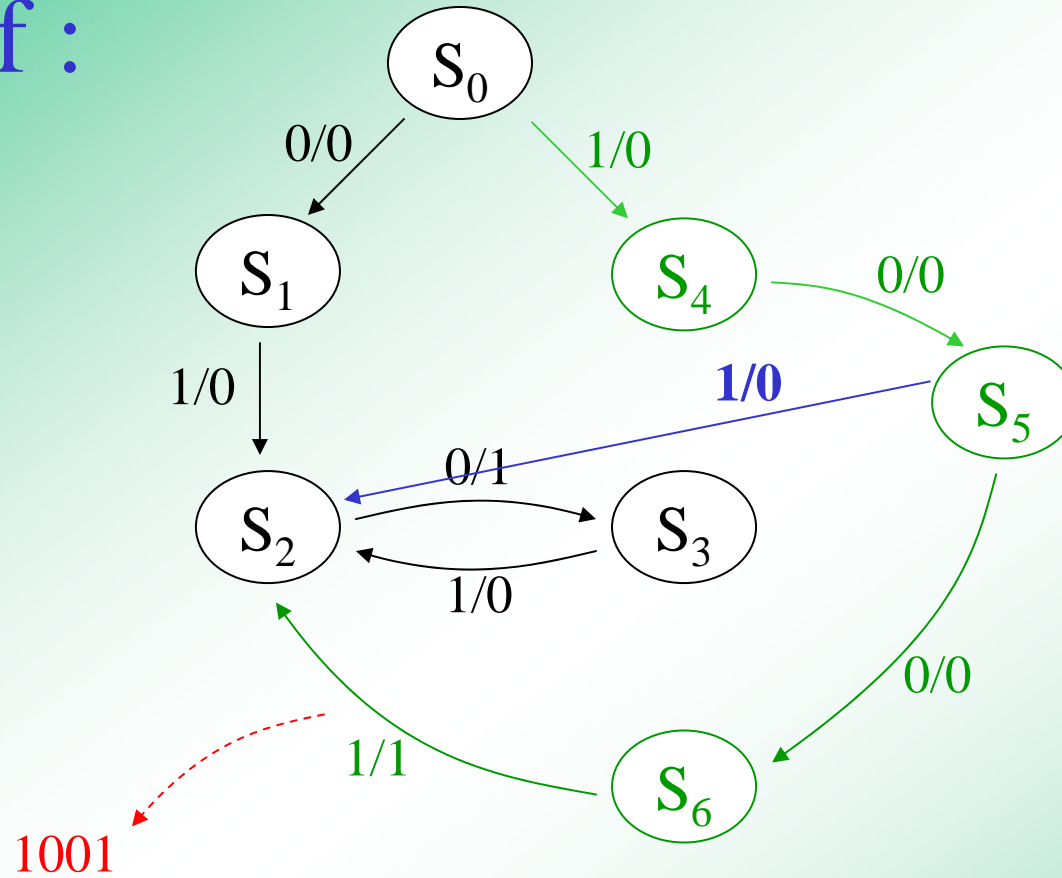


If :

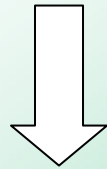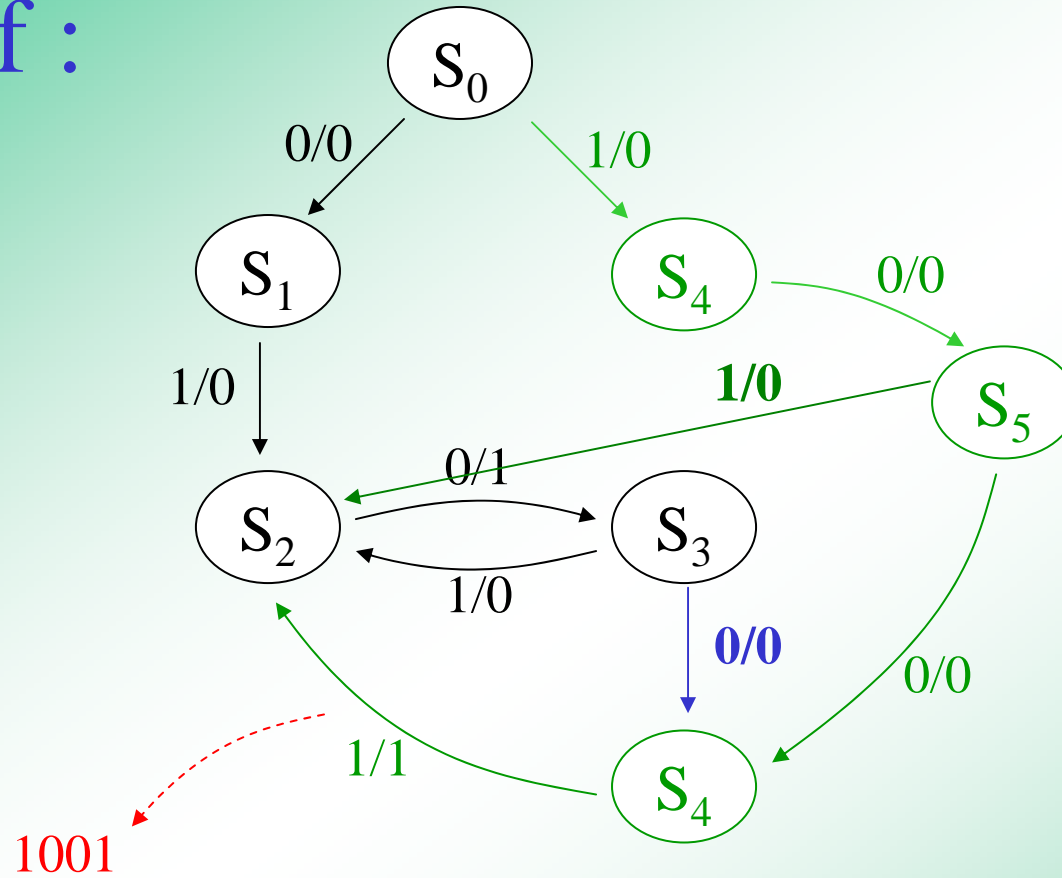

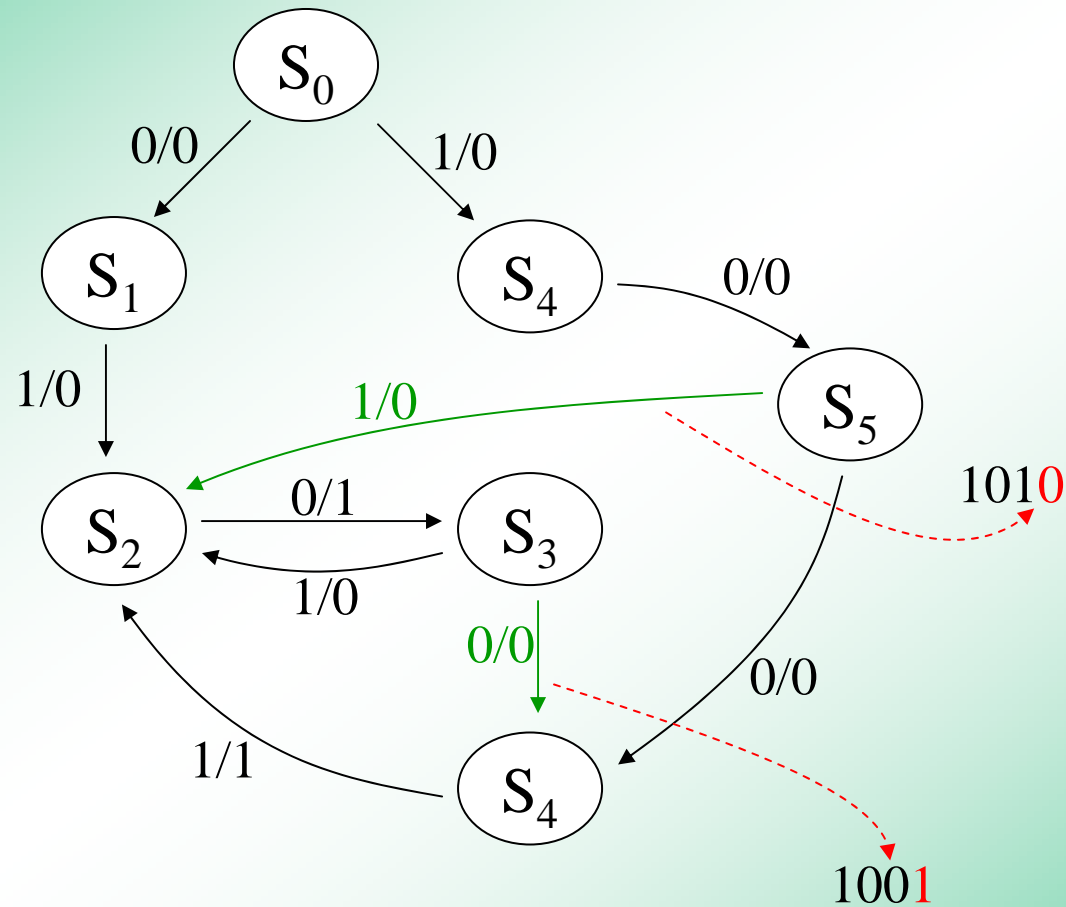

S_3, S_5 have the same next states (S_2, S_6)

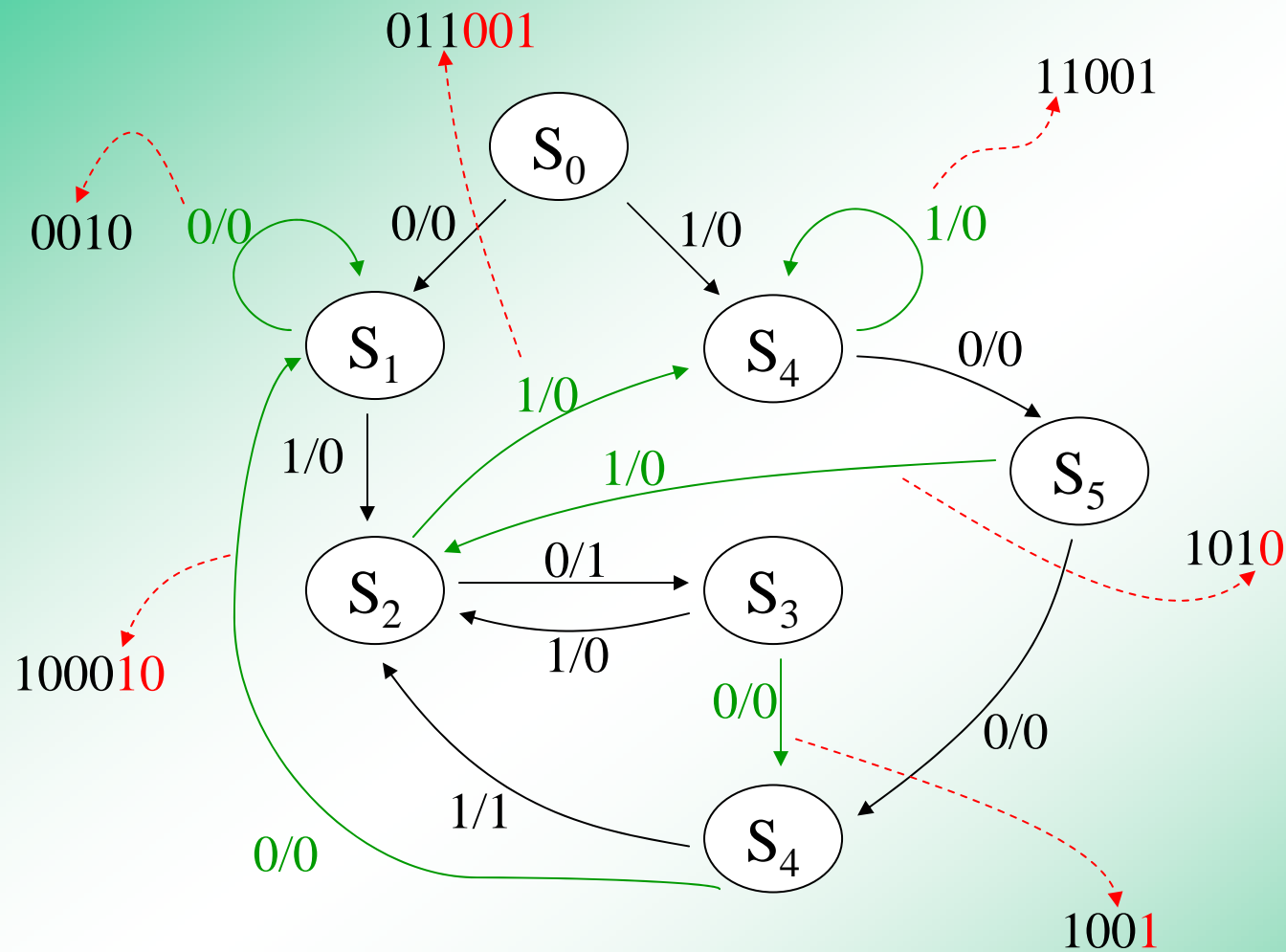
$\Rightarrow S_3 \equiv S_5$ (equivalent)



S_3, S_5 have the same next states (S_2, S_6)

$\Rightarrow S_3 \equiv S_5$ (equivalent)

– Moore Machine Example –

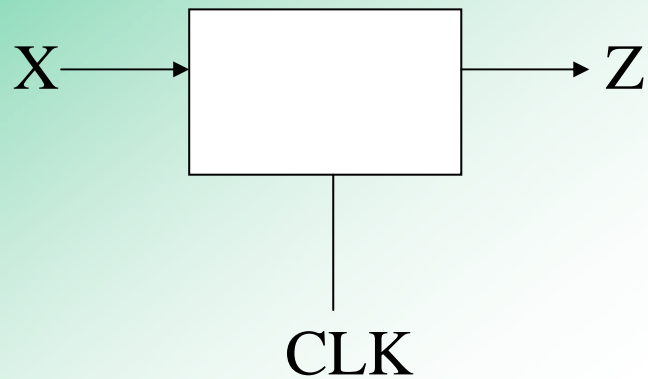




Z gives "1" if total number of "1" received is "odd" and at least 2 consecutive "0" received
Otherwise, Z gives "0"

X	=	1	0	1	1	0	0	1	1	
Z	=	(0)	0	0	0	0	0	1	0	1

Reset




and

Even "1"s

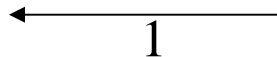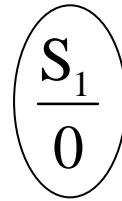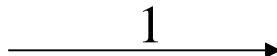




1



Odd "1"s

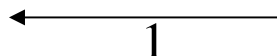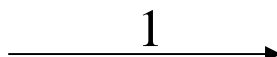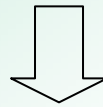

2



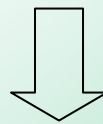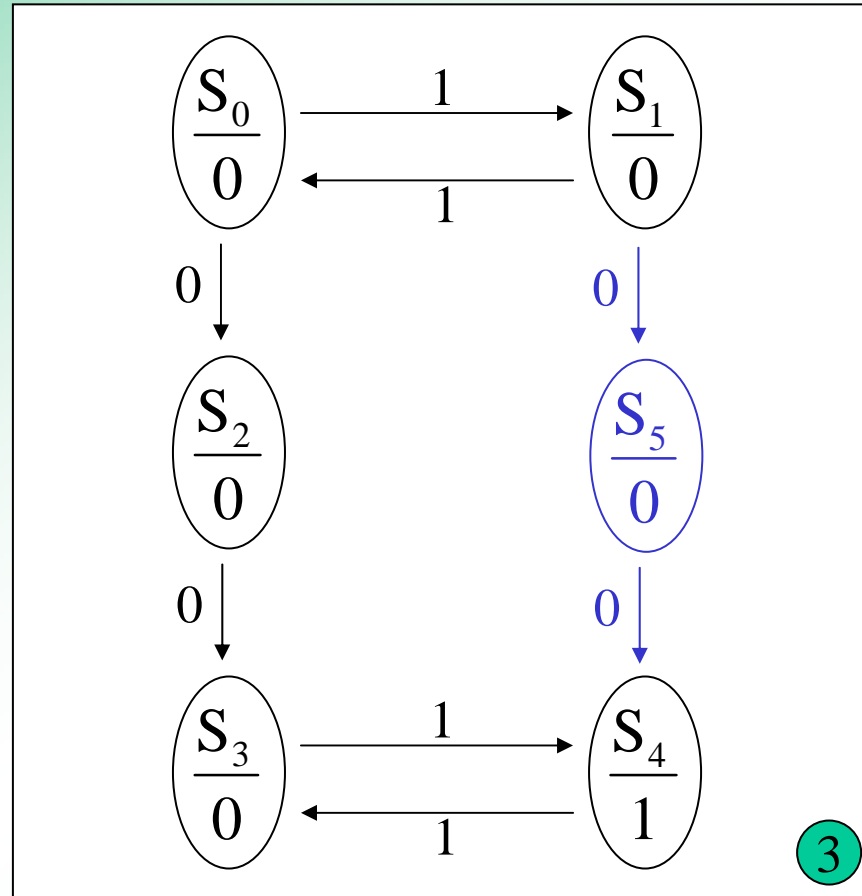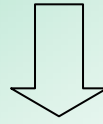

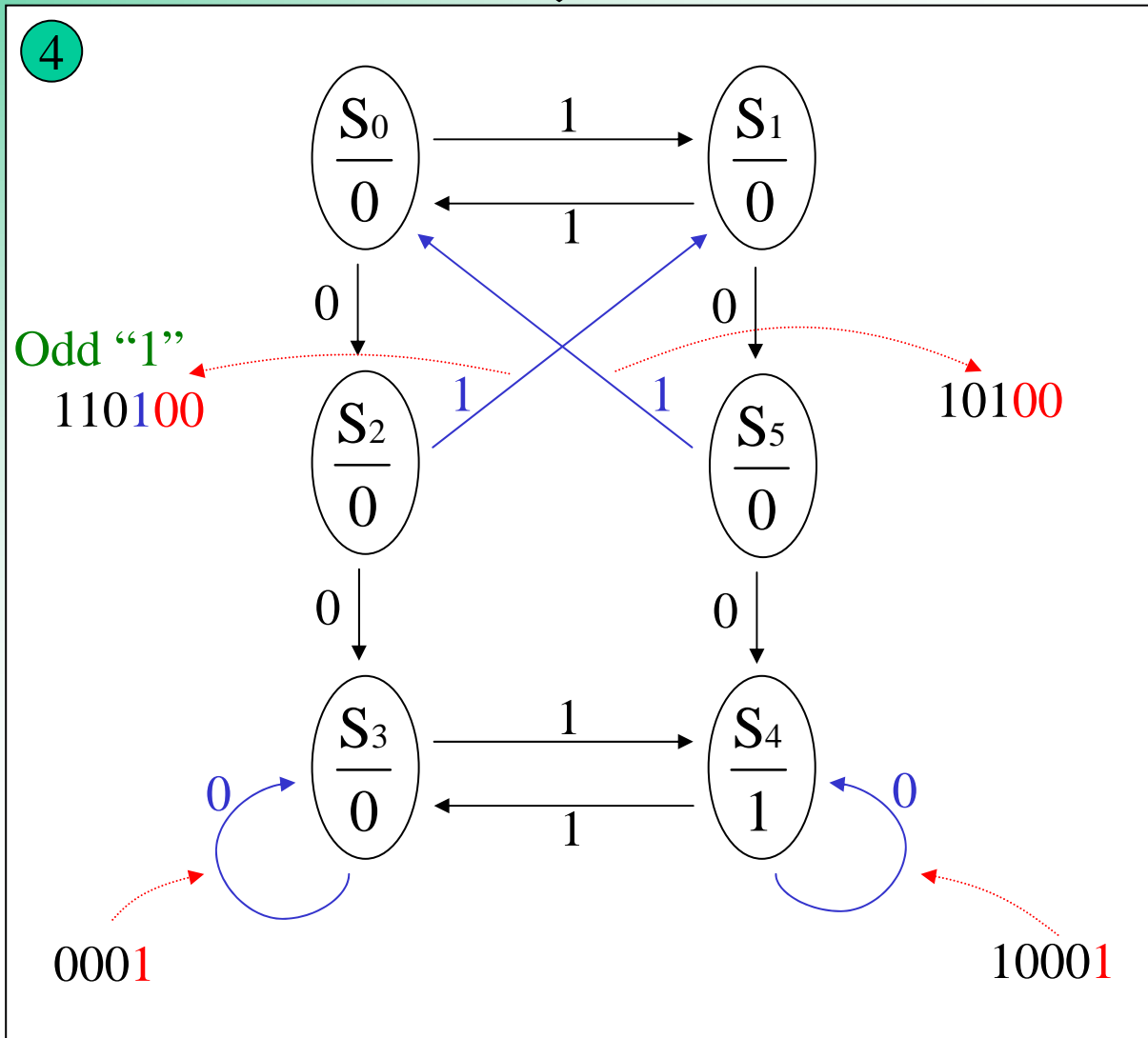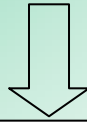

14-3 Guidelines for Construction of State Graphs

§ Guidelines for Construction of State Graphs

1. Understand problem by constructing sample sequences.

2. Determine reset state


3. Construct partial graph to obtain "1" output

4. Construct remaining partial graphs to obtain "1" output.


5. When setting up a new state, see whether it can go to an existing state.

6. Complete the graph. (Check all output 組合 !!)

7. 驗算 !!

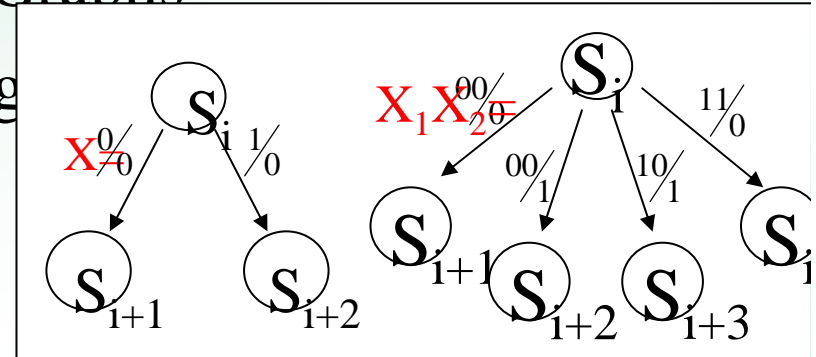


Example : A Mealy Machine

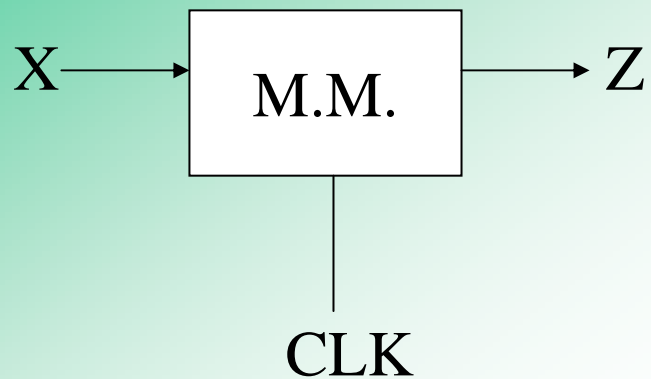

Check 4 consecutive outputs as a group , then resets
gives "1" when $X = 0101$ or 1001


X	=	0	1	0	1		0	0	1	0		1	0	0	1		0	1	0	0
Z	=	0	0	0	1		0	0	0	0		0	0	0	1		0	0	0	0

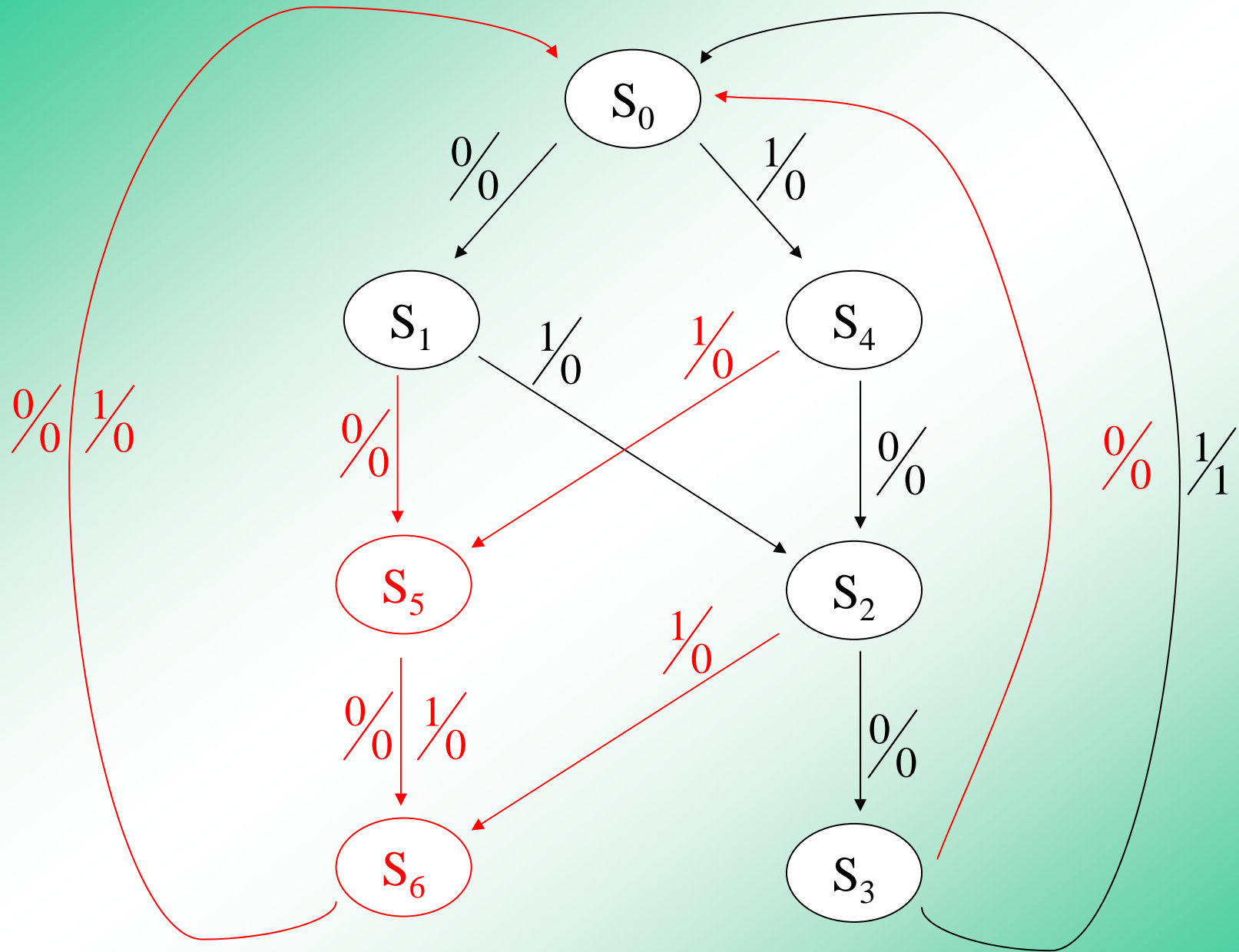分析 : gives "1" if either "01" or "10" followed
by "01"




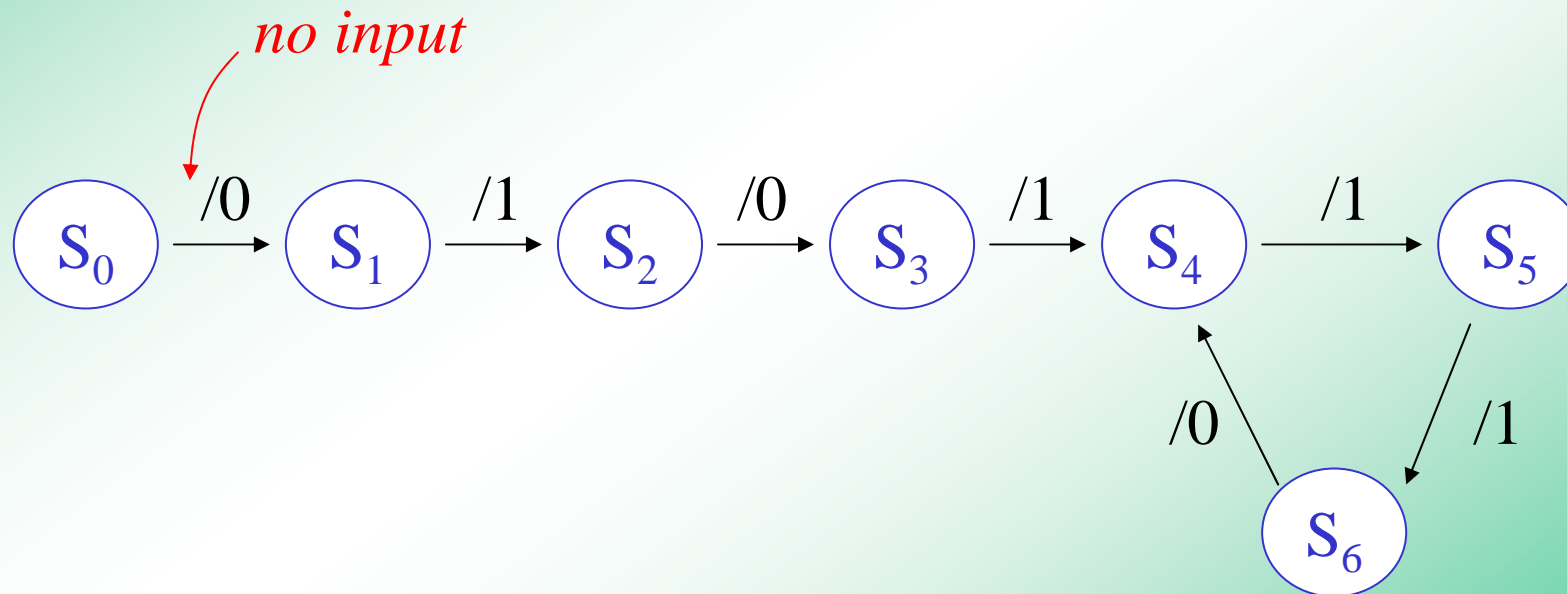Example:

*Find the Mealy state graph for a network that generates **0101 110 110 110***



Example:

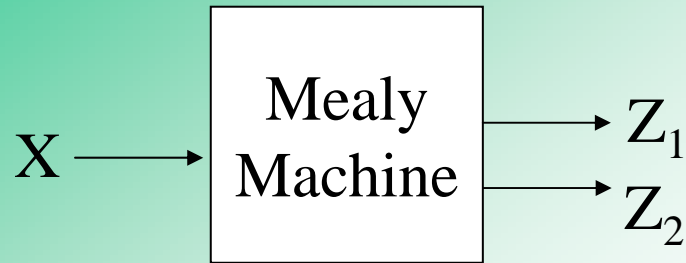

$Z_1=1$ if sequence 100 occurs,

Assume 010 has never occurred

$Z_2=1$ if sequence 010 occurs,


Note. Once a $Z_2=1$, $Z_1=1$ never occur.

But not vice versa


$X1 = 100110010 | 1010010110100$

$Z1 = 001000100 | 0000000000000$


$Z2 = 0000000001 | 0101001000010$

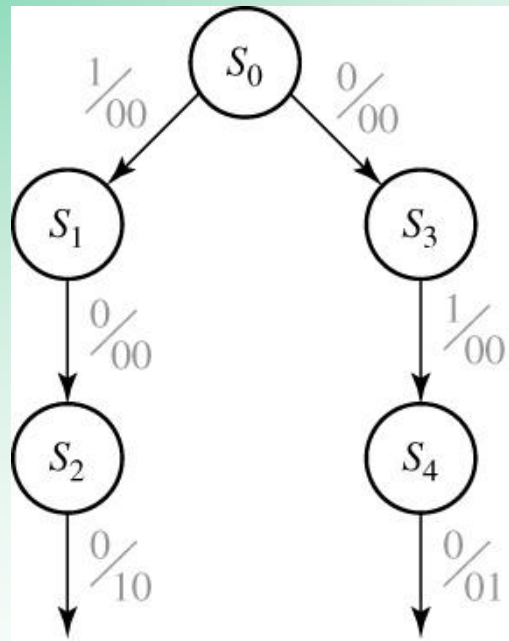


(a)

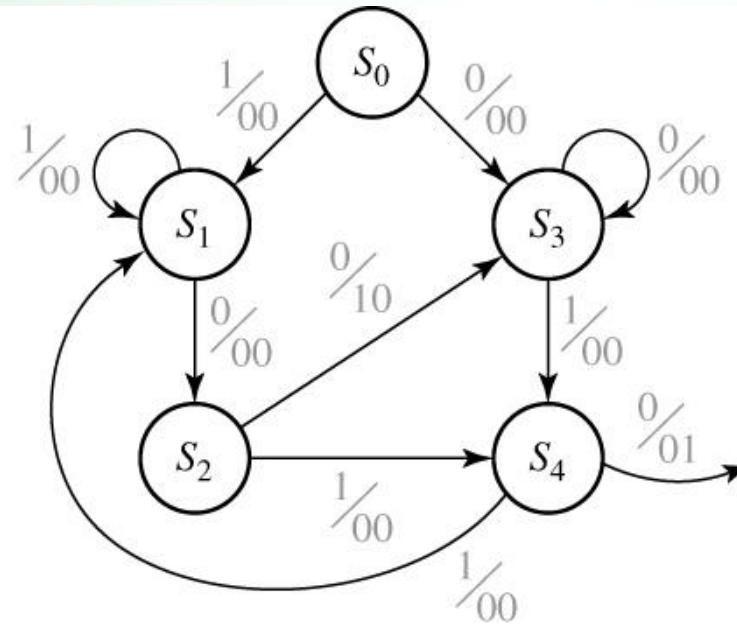

(b)

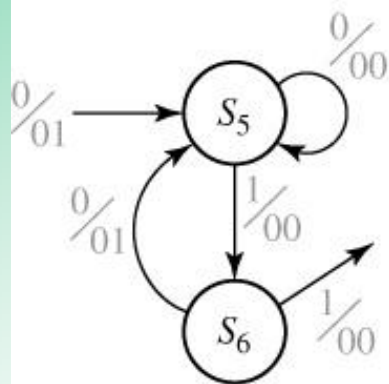


(a) Partial graph for 010

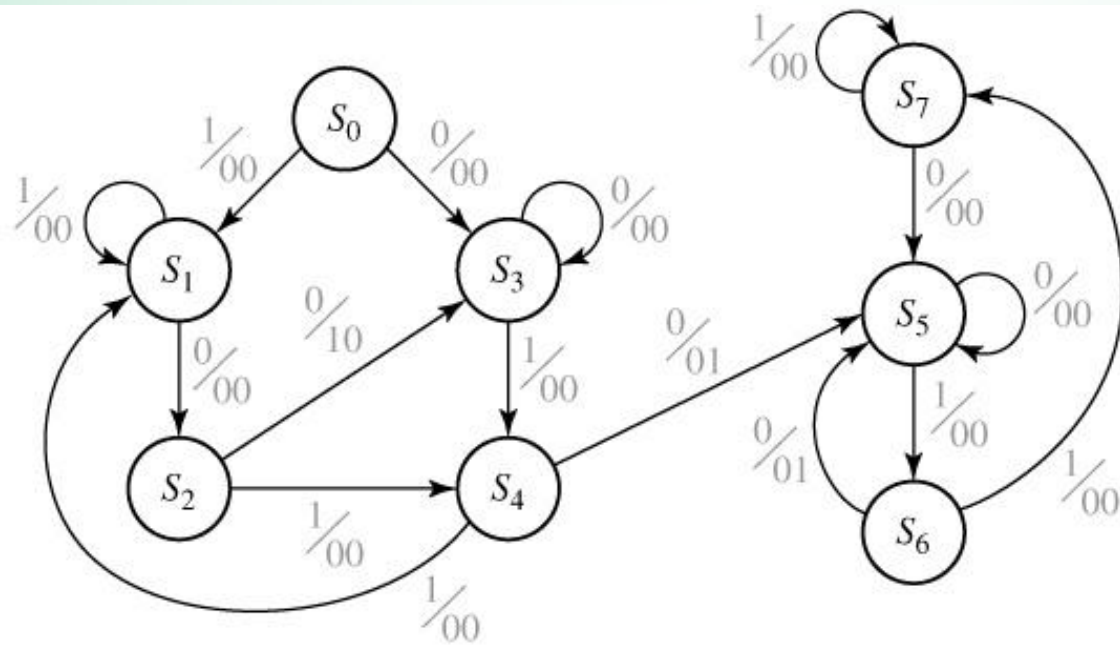

(b) Complete state graph

Example:

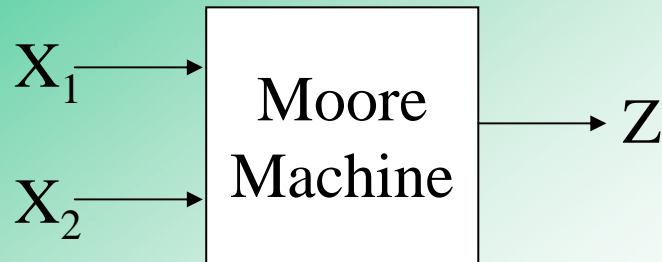

Z remains a constant value ("0" or "1") unless the following input occurs.

$$X_1X_2 = 01, 11 \quad Z = 0$$

$$10, 11 \quad Z = 1$$

$$10, 01 \quad Z \text{ changes value}$$

Previous inputs (x_1x_2)	Output (Z)	State Designation
00 or 11	0	S_0
00 or 11	1	S_1
01	0	S_2
01	1	S_3
10	0	S_4
10	1	S_5

Z remains a constant value ("0" or "1")
unless the following input occurs.

$X_1X_2 = 01, 11 \quad Z = 0$

10, 11 $Z = 1$

10, 01 Z changes value


Previous inputs (x_1x_2)	Output (Z)	State Designation
00 or 11	0	S_0
00 or 11	1	S_1
01	0	S_2
01	1	S_3
10	0	S_4
10	1	S_5

P.S.	Z	$x_1x_2 =$	00	01	11	10
S_0	0		S_0	S_2	S_0	S_4
S_1	1		S_1	S_3	S_1	S_5
S_2	0		S_0	S_2	S_0	S_4
S_3	1		S_1	S_3	S_0	S_5
S_4	0		S_0	S_3	S_1	S_4
S_5	1		S_1	S_2	S_1	S_5


⇒ State table

P.S.	Z	$x_1 x_2 =$	00	01	11	10
S_0	0		S_0	S_2	S_0	S_4
S_1	1		S_1	S_3	S_1	S_5
S_2	0		S_0	S_2	S_0	S_4
S_3	1		S_1	S_3	S_0	S_5
S_4	0		S_0	S_3	S_1	S_4
S_5	1		S_1	S_2	S_1	S_5


* State graph

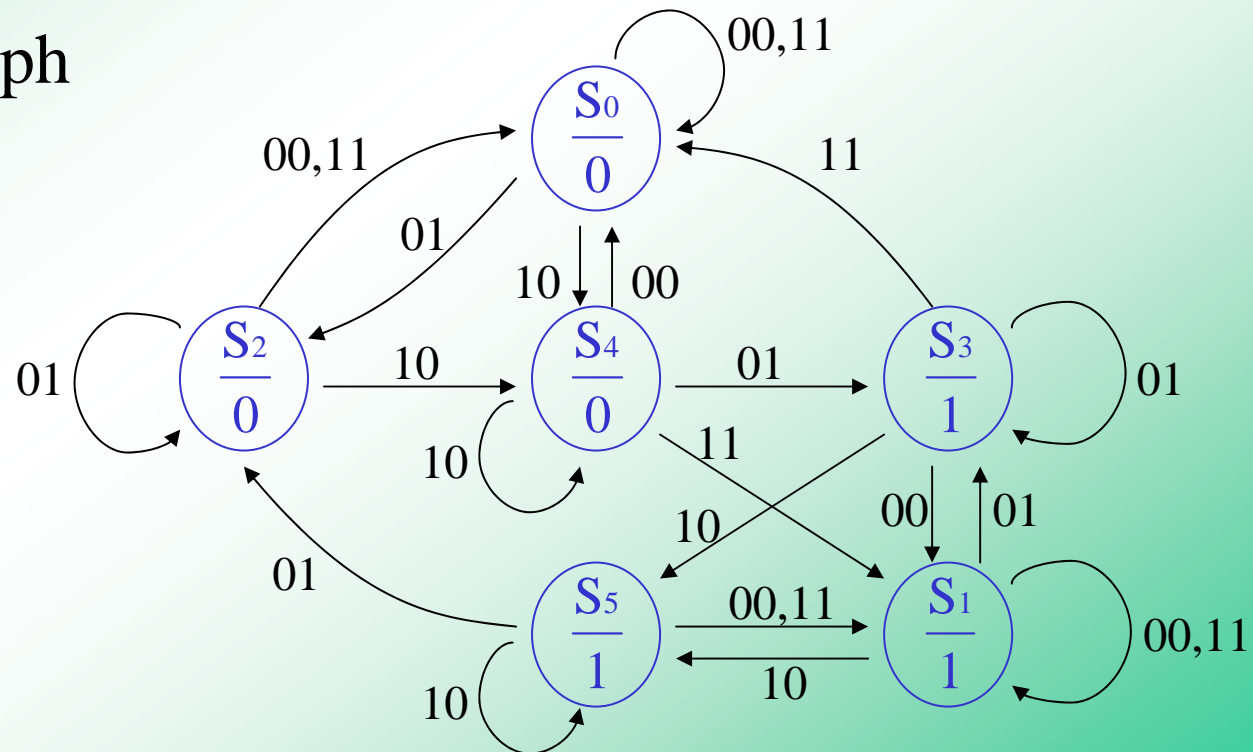


14-4 Serial Data Code Conversion


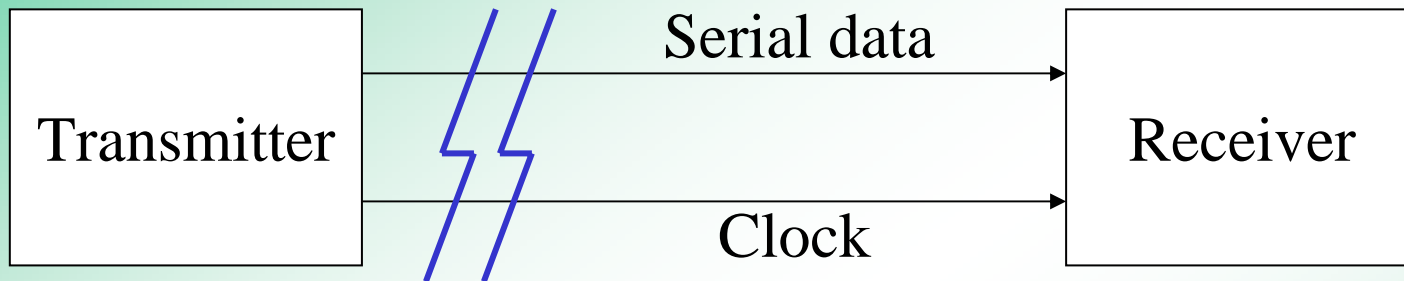


↳ Use 2 cables (not good)

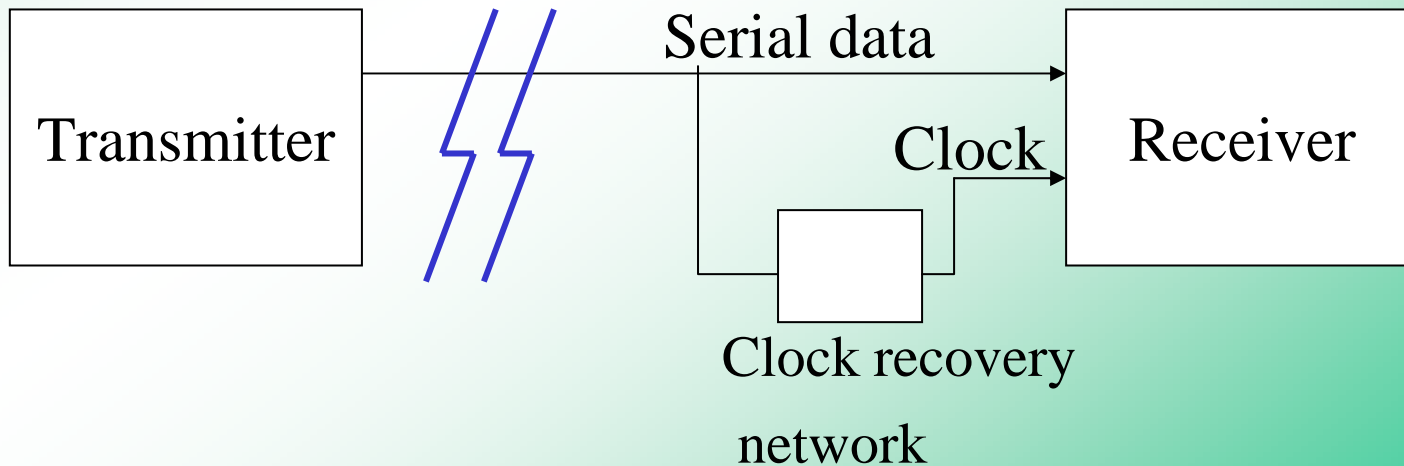

* Coding schemes

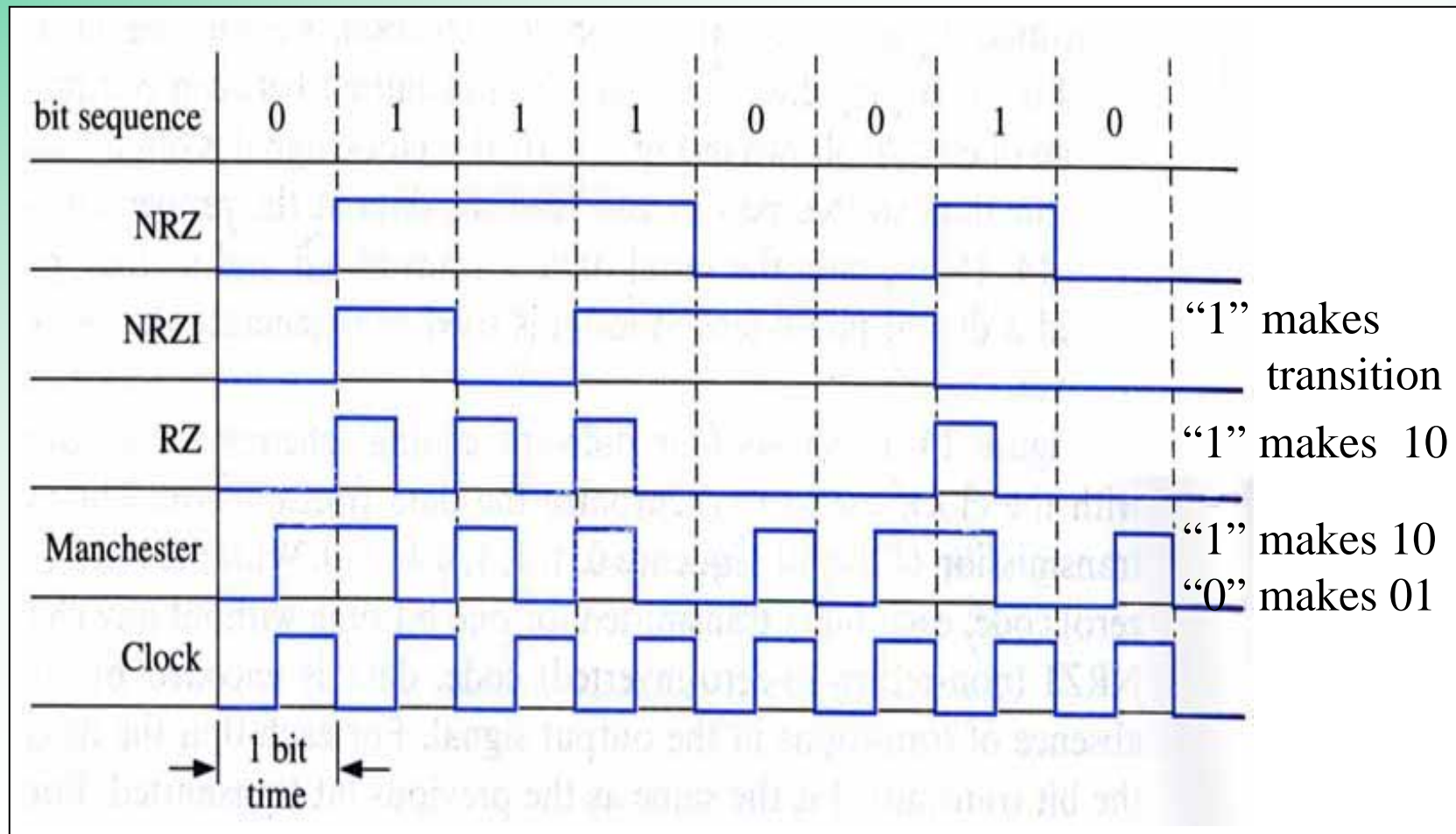


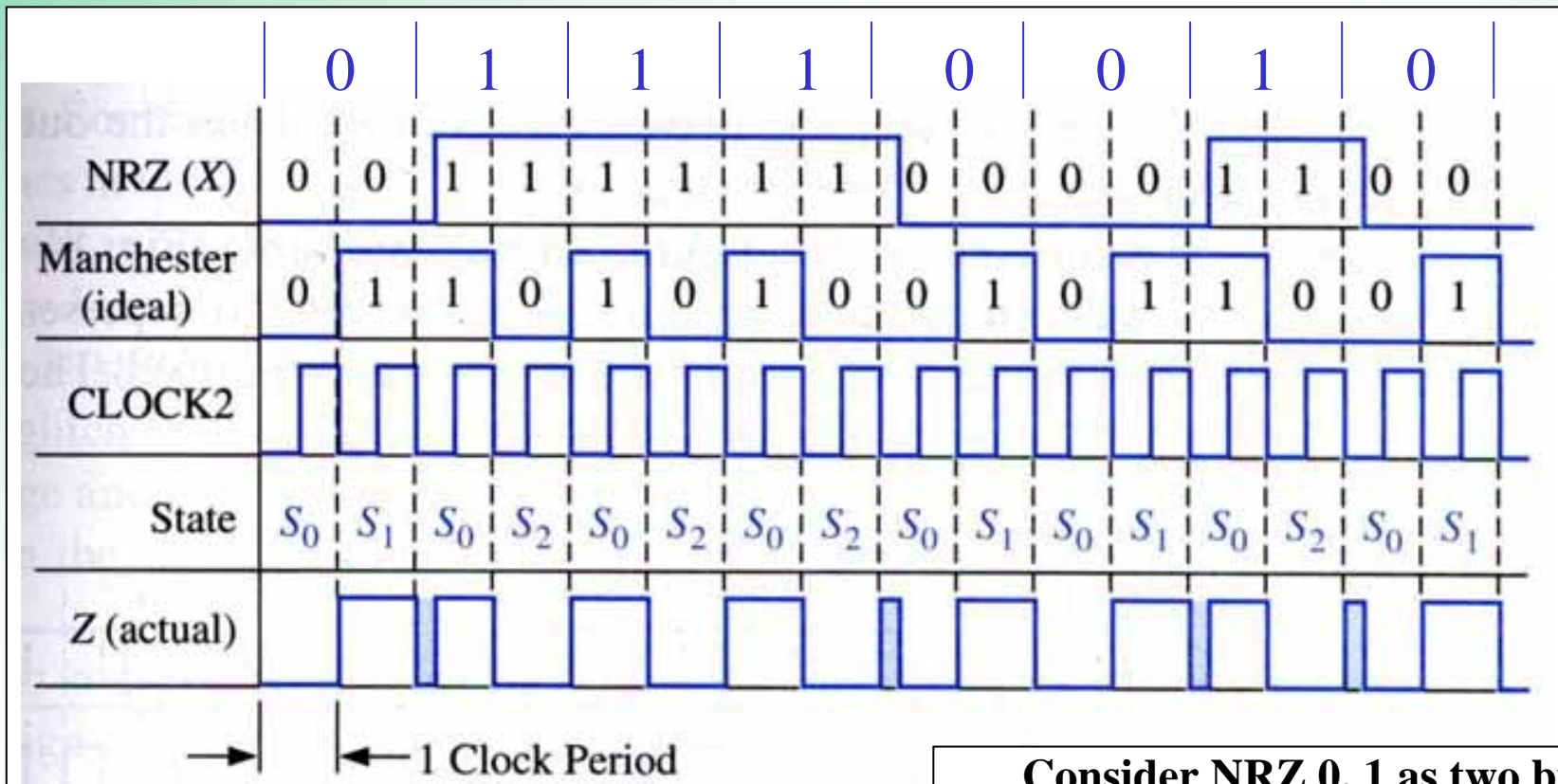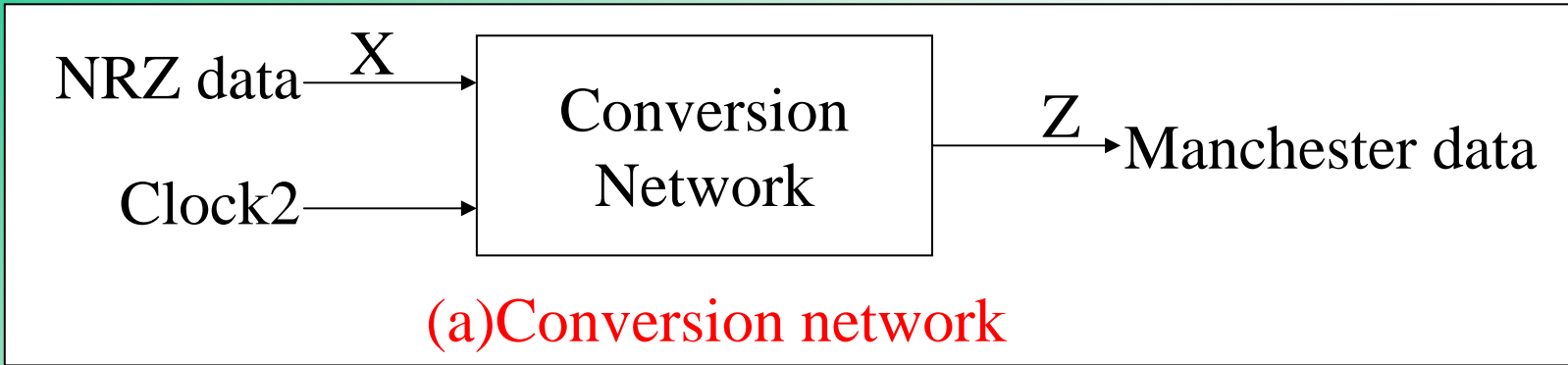



(b) Timing Chart

Consider NRZ 0, 1 as two bits which occur consecutively! Every two bits, machine returns to reset state


(c) State graph

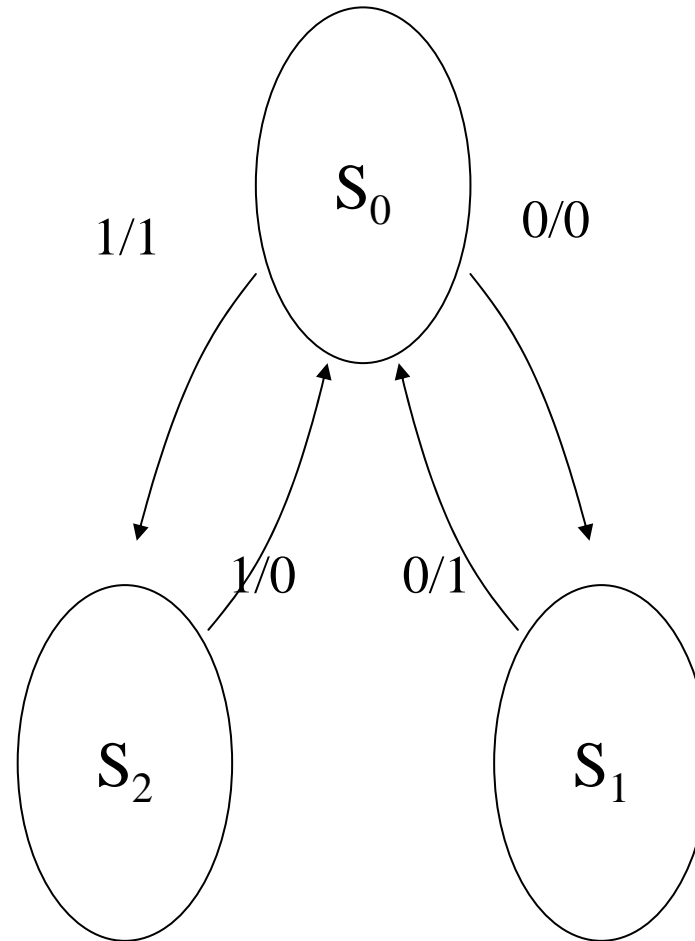

(c) State graph


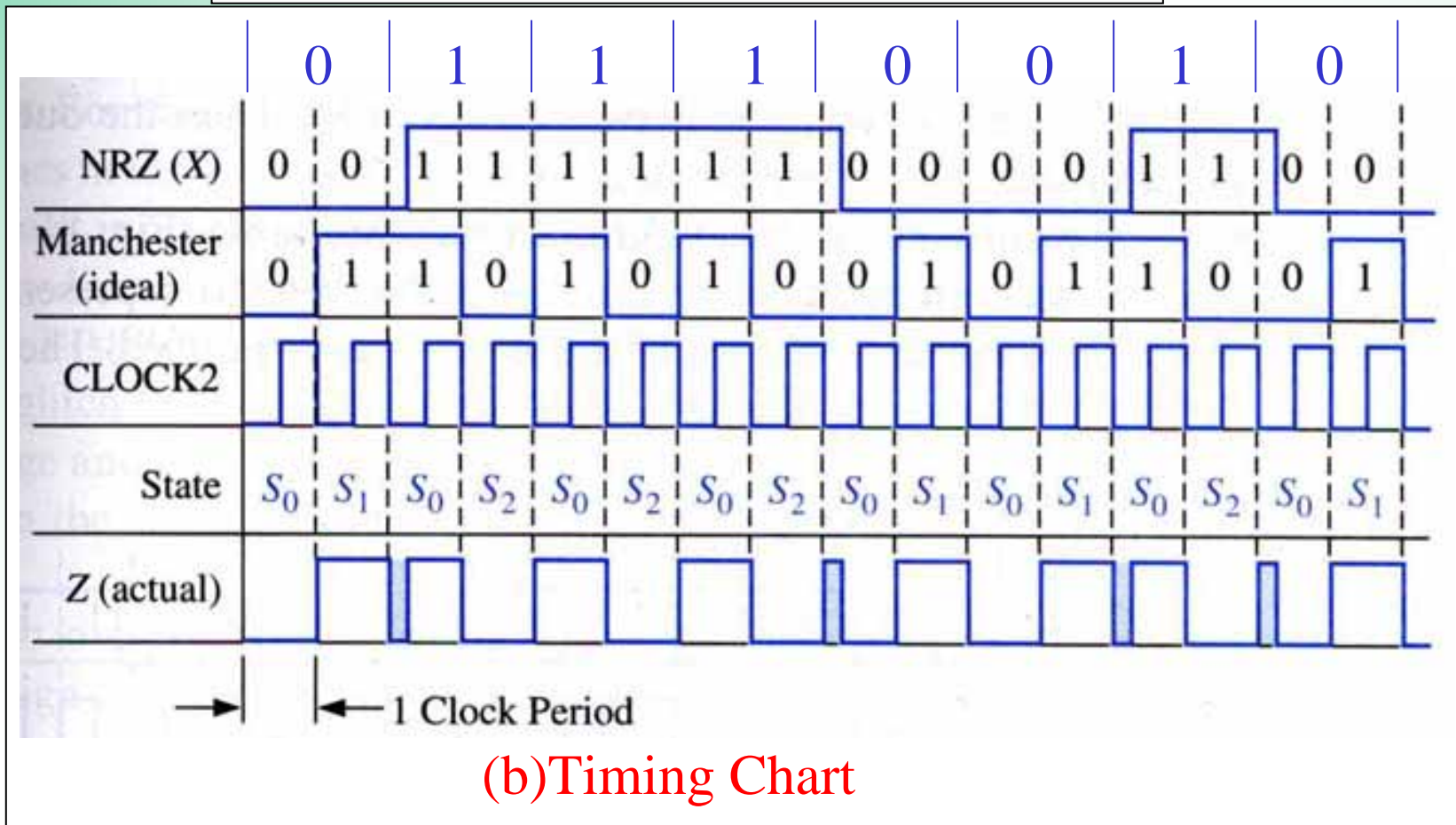
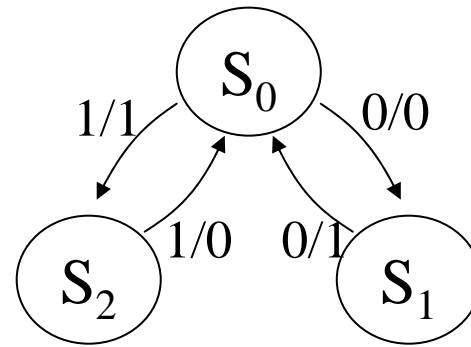


(c) State graph

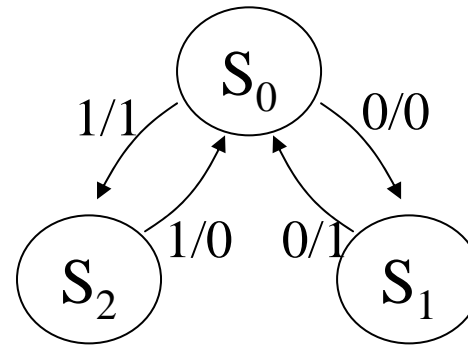


Present state	Next state		Output (Z)	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
S_0	S_1	S_2	0	1
S_1	S_0	—	1	—
S_2	—	S_0	—	0



(d) State table

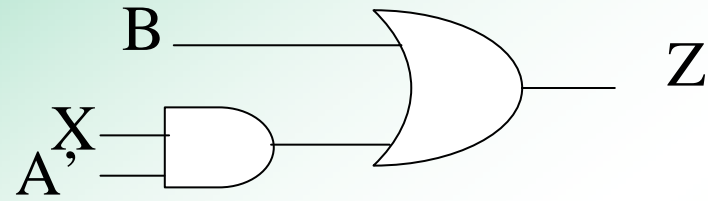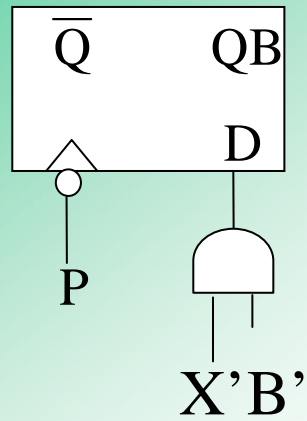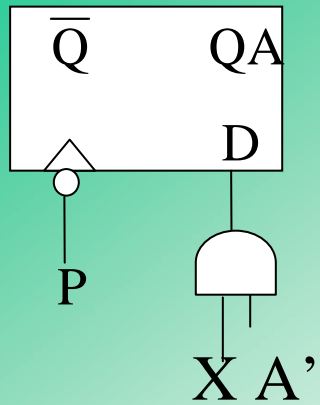

S0	AB = 00	X=0, Z=0	X=1, Z=1
S1	10	X=0, Z=0	X=1, Z=0
S2	01	X=0, Z=0	X=1, Z=1


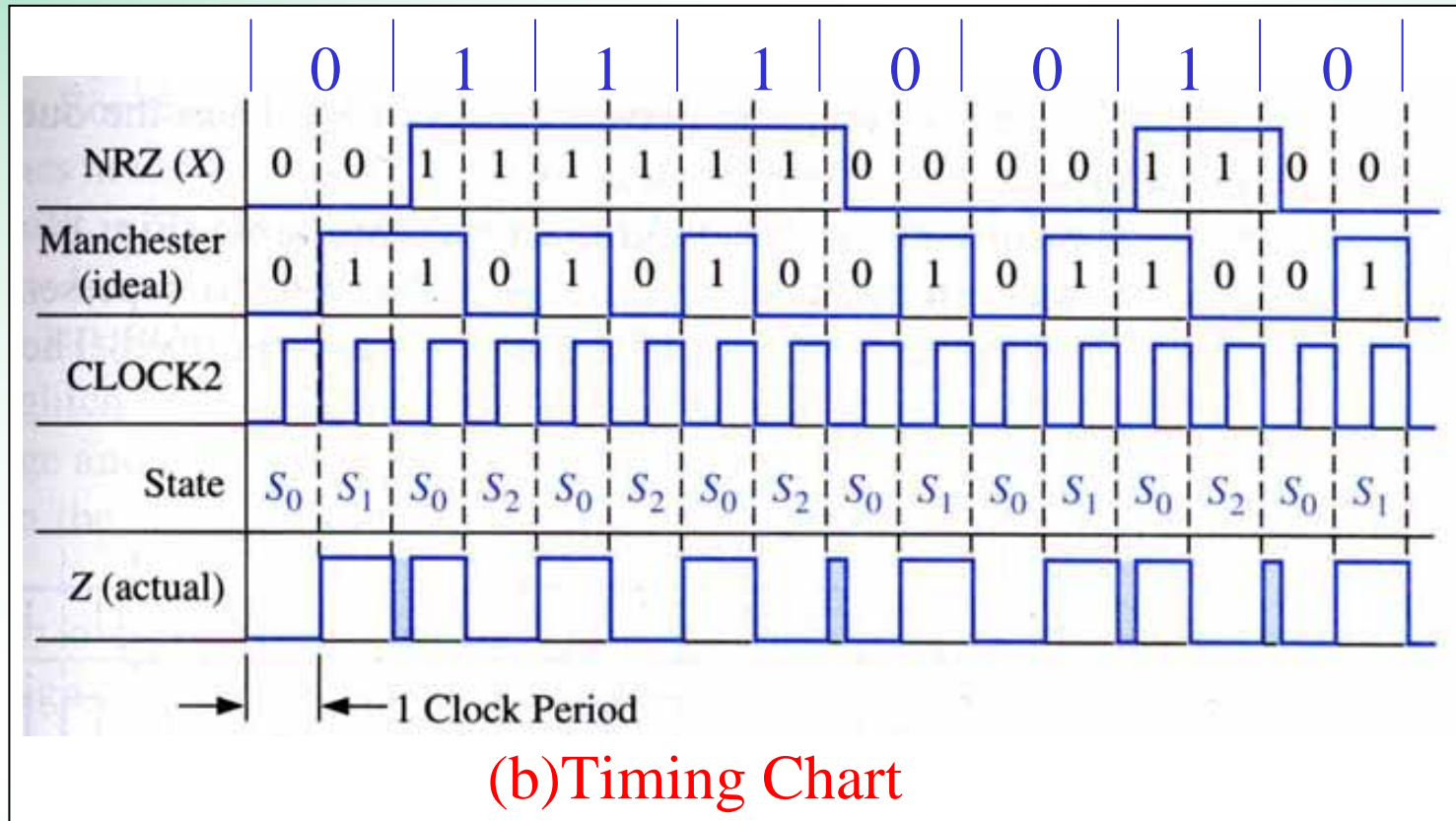


*Moore Machine

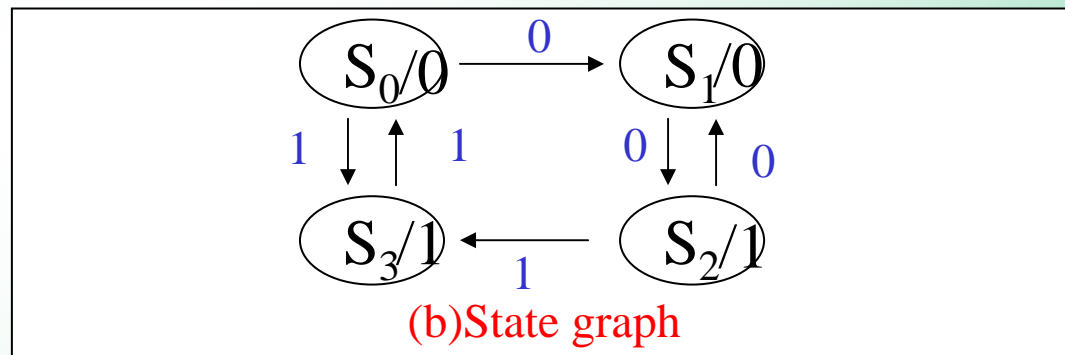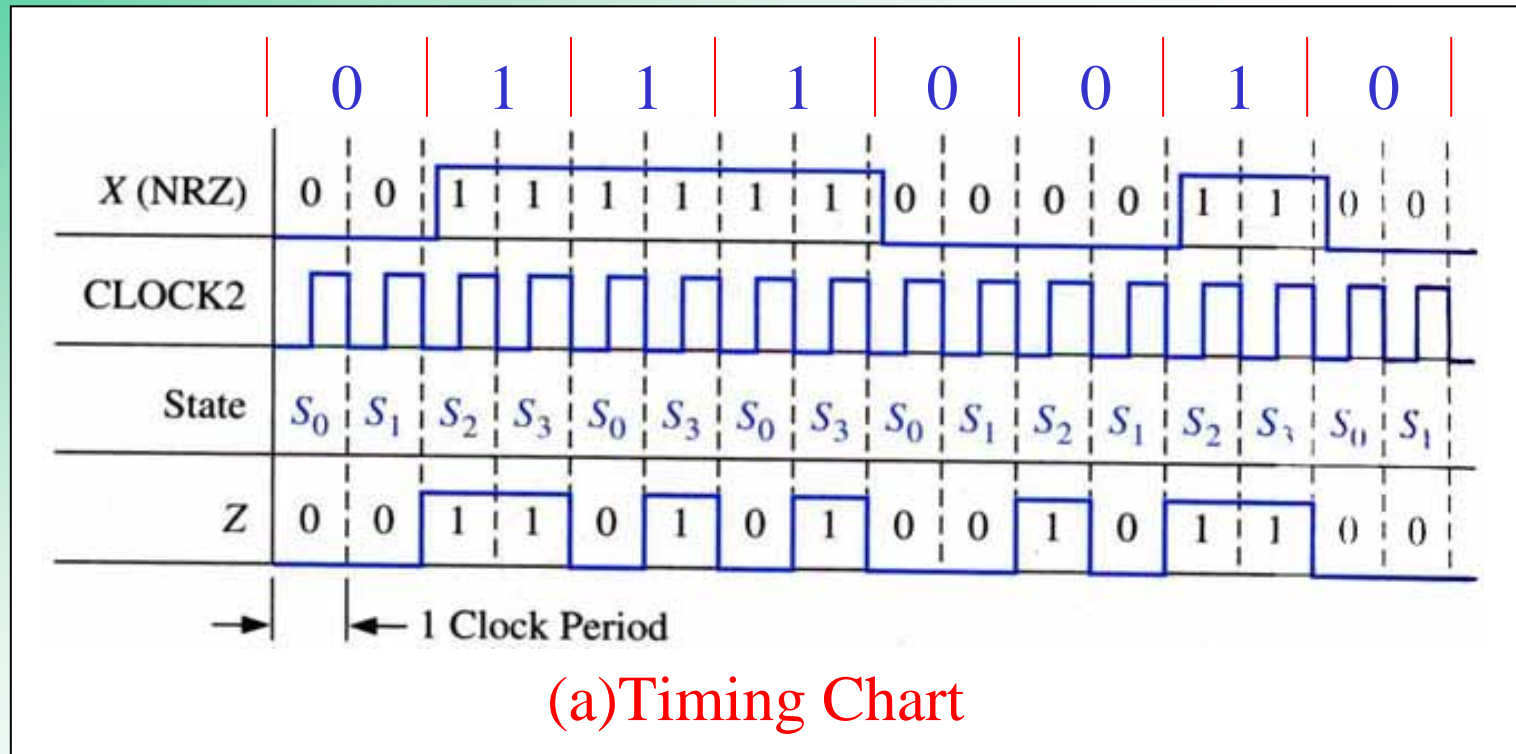


Present state	Nest state		Present Output (Z)
	$x = 0$	$x = 1$	
S_0	S_1	S_3	0
S_1	S_2	—	0
S_2	S_1	S_3	1
S_3	—	S_0	1

(C)State table

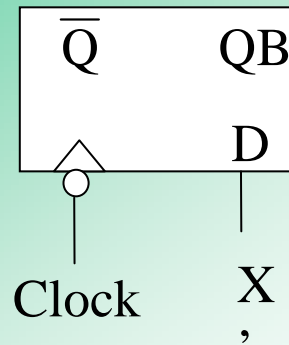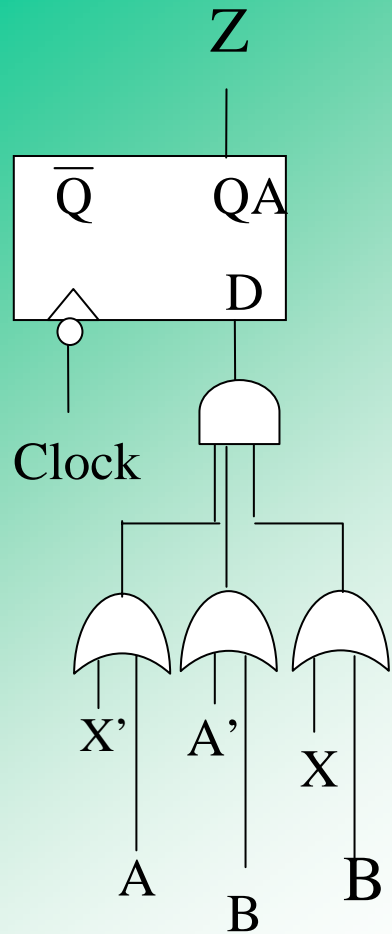

S0	AB = 00
S1	01
S2	11
S3	10

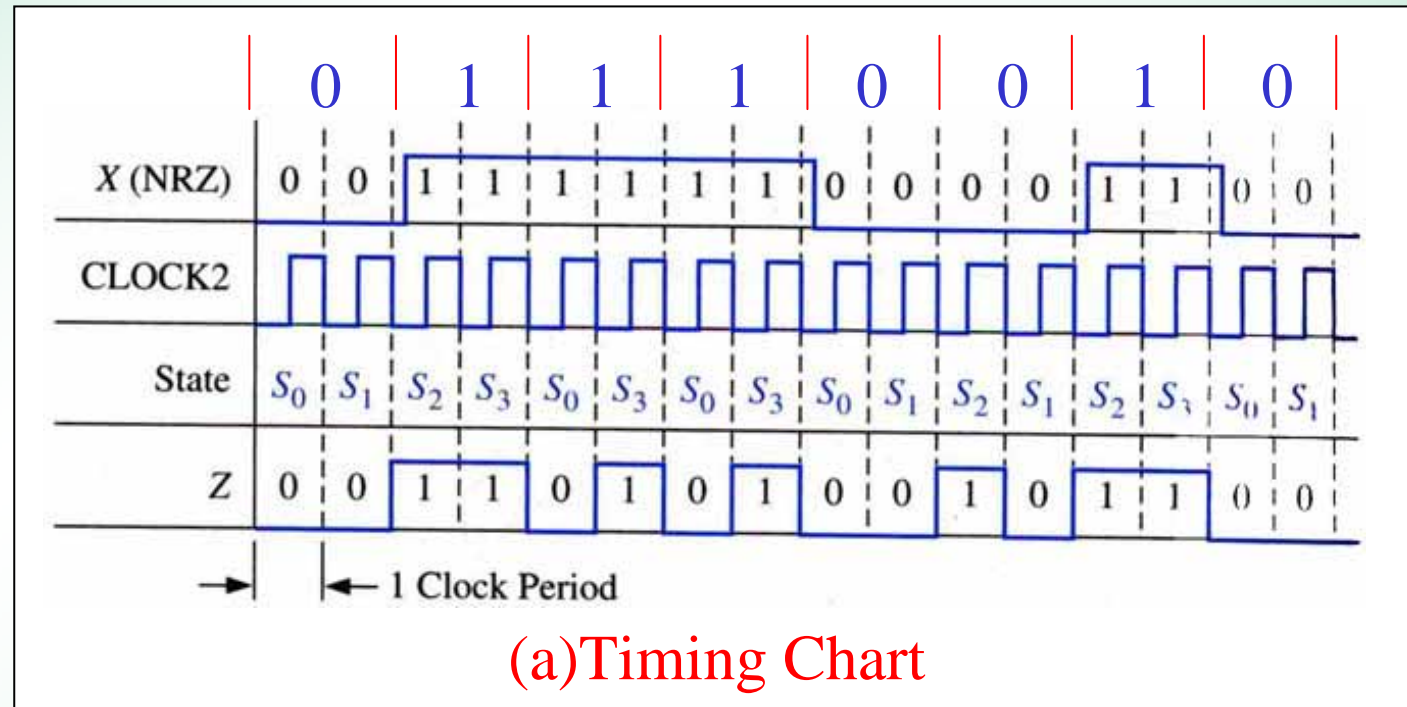


- **Property of the complete specified state graph**

- **OR** together all input labels on arcs emanating from a state, the result can reduce to 1

$$F + F'R + F'R' = F + F' = 1$$

- **AND** together any pair of input labels on arcs emanating from a state, the result can reduce to 0
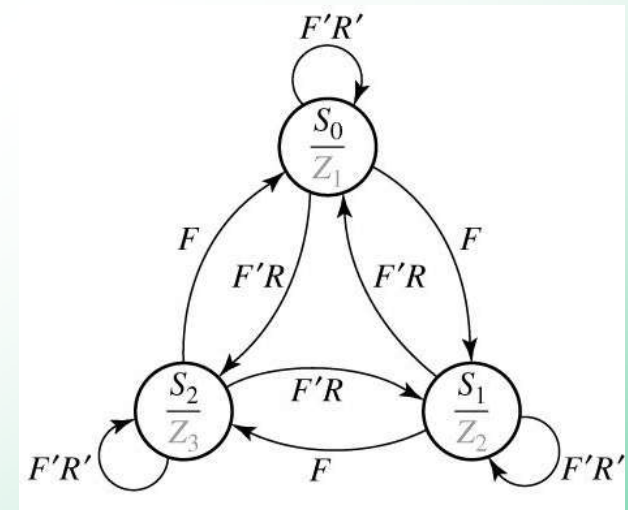
$$F \cdot F'R = 0, \quad F \cdot F'R' = 0, \quad F'R \cdot F'R' = 0$$



- For large sequential circuits (4 inputs, 4 outputs)

- X_1X_4'/Z_2Z_3 1--0/0110

- $-/Z_1$ for any combination of input values,
the indicated state will occur and output $Z_1=1$

HOMEWORK -- Unit 14

- 14.07(a)
- 14.17
- 14.21
- 14.31

