

Chap. 15:

# Reduction of State Tables/ State Assignment

Statement of Problem



State Graph



State Table



Reduction of States



State Assignment



Choice of F/F's



Derivation of  
F/F Input Equation and  
Z Output Equation




Circuit Realization and  
Timing Chart

## 15-1 Elimination of Redundant States

When setting up states, some extra states may be included.

⇒ eliminate these states


*Ex: a previous example*

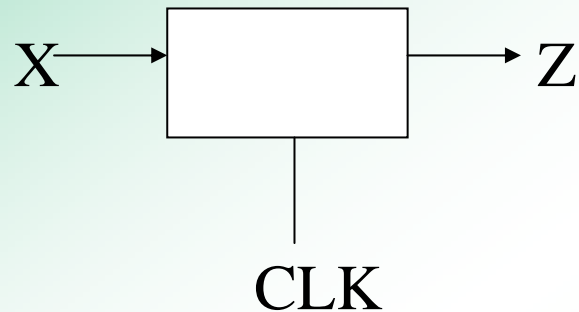


Z gives "1" after X receiving  
0101 or 1001
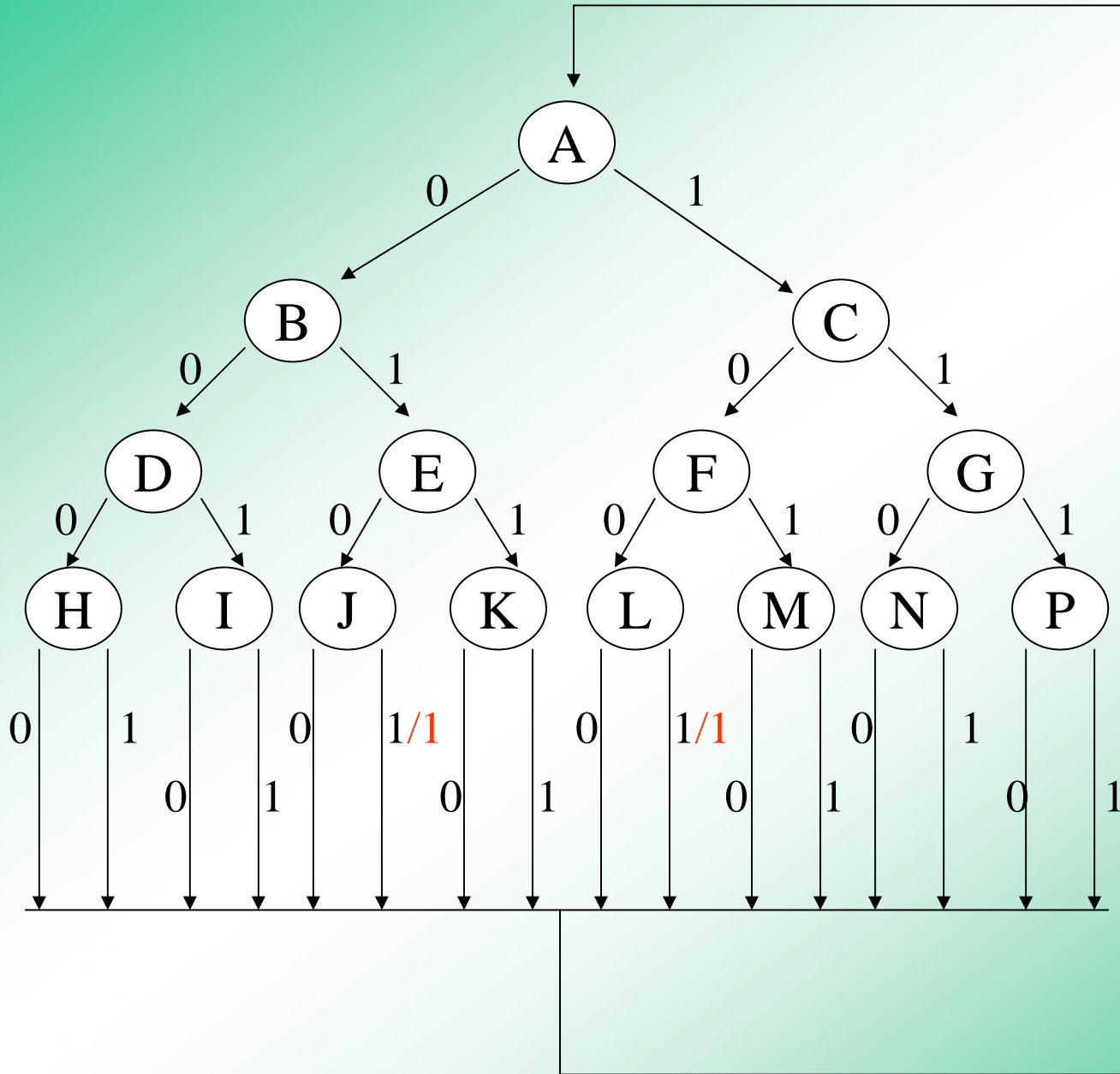
### **A brute force solution:**

Reset state A, checks 3 consequent bits of every possible combinations.  
After 4th bit coming-in, give output and reset to state A.




Input Sequence	P.S.	N.S.		Present Output	
		x = 0	x = 1	x = 0	x = 1
Reset	A	B	C	0	0
0	B	D	E	0	0
1	C	F	G	0	0
00	D	H	I	0	0
01	E	J	K	0	0
10	F	L	M	0	0
11	G	N	P	0	0
000	H	A	A	0	0
001	I	A	A	0	0
010	J	A	A	0	1
011	K	A	A	0	0
100	L	A	A	0	1
101	M	A	A	0	0
110	N	A	A	0	0
111	P	A	A	0	0

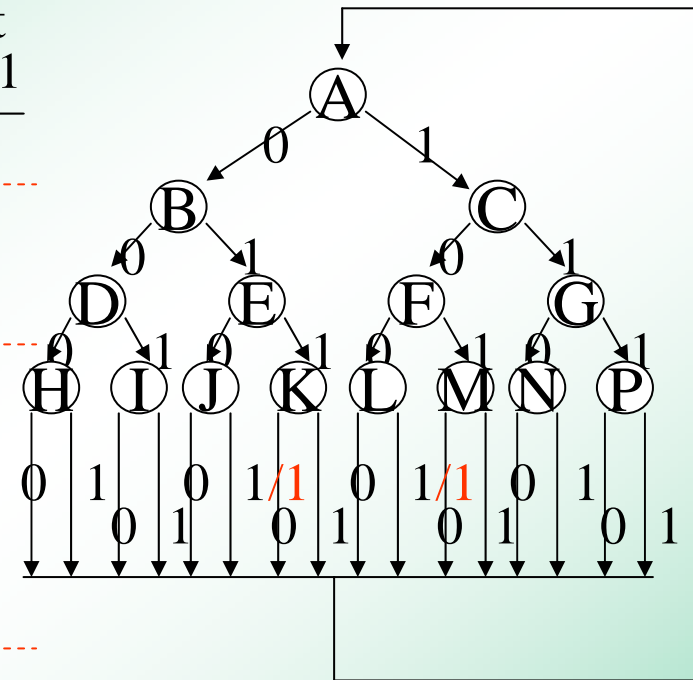

Input Sequence	P.S.	N.S.		Present Output	
		x = 0	x = 1	x = 0	x = 1
Reset	A	B	C	0	0
0	B	D	E	0	0
1	C	<del>E</del> F	<del>D</del> G	0	0
00	D	H	<del>H</del> I	0	0
01	E	J	<del>H</del> K	0	0
→ 10	<del>E</del> F	<del>J</del> L	<del>H</del> M	0	0
→ 11	<del>D</del> G	<del>H</del> N	<del>H</del> R	0	0
000	H	A	A	0	0
→ 001	<del>H</del> I	A	A	0	0
010	J	A	A	0	1
→ 011	<del>H</del> K	A	A	0	0
→ 100	<del>J</del> L	A	A	0	1
→ 101	<del>H</del> M	A	A	0	0
→ 110	<del>H</del> N	A	A	0	0
→ 111	<del>H</del> R	A	A	0	0

Equivalent state :  
 The same N.S.  
 The same Z

P.S.	N.S.		P.O.	
	x = 0	x = 1	x = 0	x = 1
A	B	C	0	0
B	D	E	0	0
C	E	D	0	0
D	H	H	0	0
E	J	H	0	0
H	A	A	0	0
J	A	A	0	1

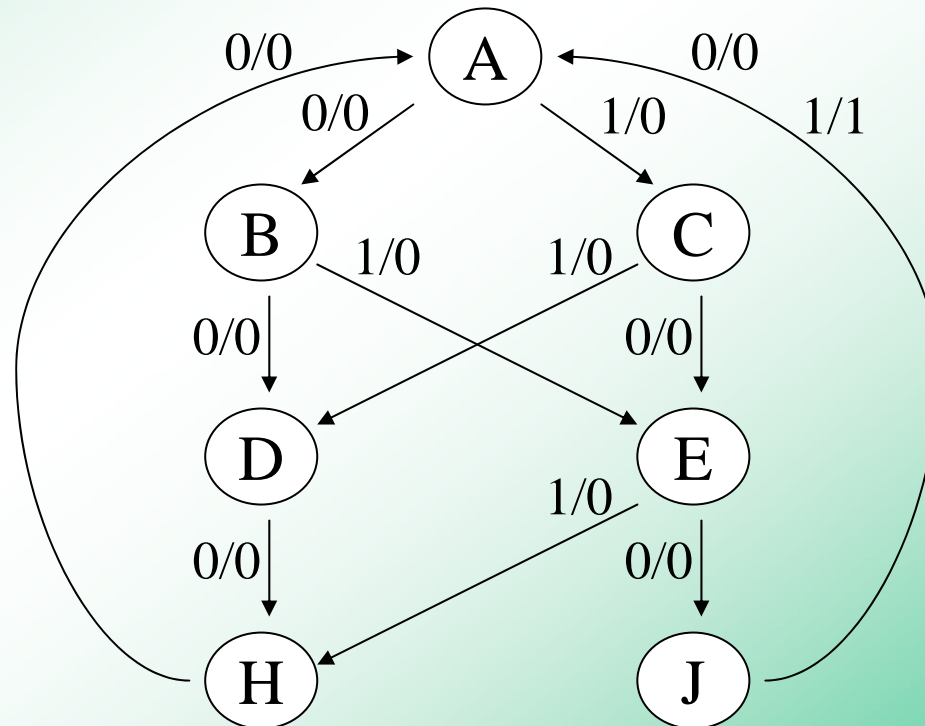


## 15-2 Equivalent States

Equivalent States "  $\equiv$  "

2 machines :  $N_1, N_2$

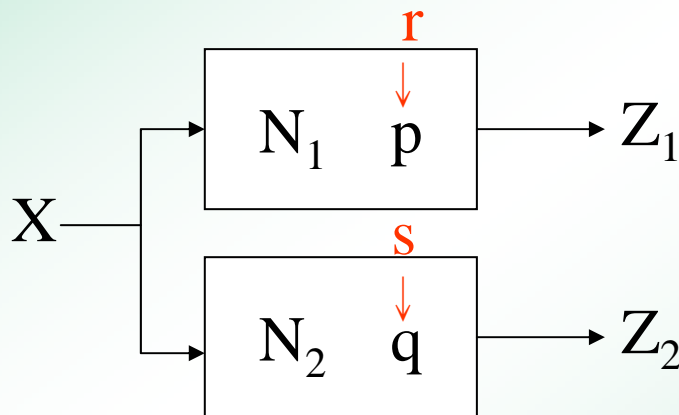$\left\{ \begin{array}{l} \text{A state } p \text{ in } N_1 \\ \text{A state } q \text{ in } N_2 \end{array} \right.$



If  $Z_1 = Z_2$  and  $r \equiv s$   
then  $p \equiv q$

$\lambda(p, x) = \lambda(q, x)$  : output

$\delta(p, x) = \delta(q, x)$  : next state



## 15-3 Determination of State Equivalence by using an Implication Table

*Ex:*

P.S.	x = 0	N.S. x = 1	Z
a	<del>d</del> a	c	0
b	f	h	0
c	<del>e</del> c	<del>d</del> a	1
<del>d</del>	a	e	0
<del>e</del>	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

# Implication chart construction

- state comparison by implied pair (only for the same output)

b	d - f c - h						
c	X	X					
d	a - d c - e	a - f c - h	X				
e	X	X	a - d c - e	X			
f	X	X	b - d e - f	X	a - b c - f		
g	b - d c - h	b - f	X	a - b c - h	X	X	
h	X	X	d - g c - e	X	a - g	b - g c - f	X
	a	b	c	d	e	f	g



Output shall be the same

P.S.	x = 0	N.S. x = 1	Z
a	d	c	0
b	f	h	0
c	e	d	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

2. Check implied pair iteratively

b	<del>d-f</del> <del>c-h</del>						
c	X	X					
d	a-d c-e	<del>a-f</del> <del>c-h</del>	X				
e	X	X	a-d c-e	X			
f	X	X	<del>b-d</del> <del>e-f</del>	X	<del>a-b</del> <del>c-f</del>		
g	<del>b-d</del> <del>c-h</del>	<del>b-f</del>	X	<del>a-b</del> <del>c-h</del>	X	X	
h	X	X	<del>d-g</del> <del>c-e</del>	X	<del>a-g</del> <del>b-g</del> <del>c-f</del>	X	X
	a	b	c	d	e	f	g

	P.S. x = 0	N.S. x = 1	Z
a	<del>d</del> a	c	0
b	f	h	0
c	<del>e</del> c	<del>d</del> a	1
d	a	e	0
e	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

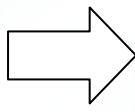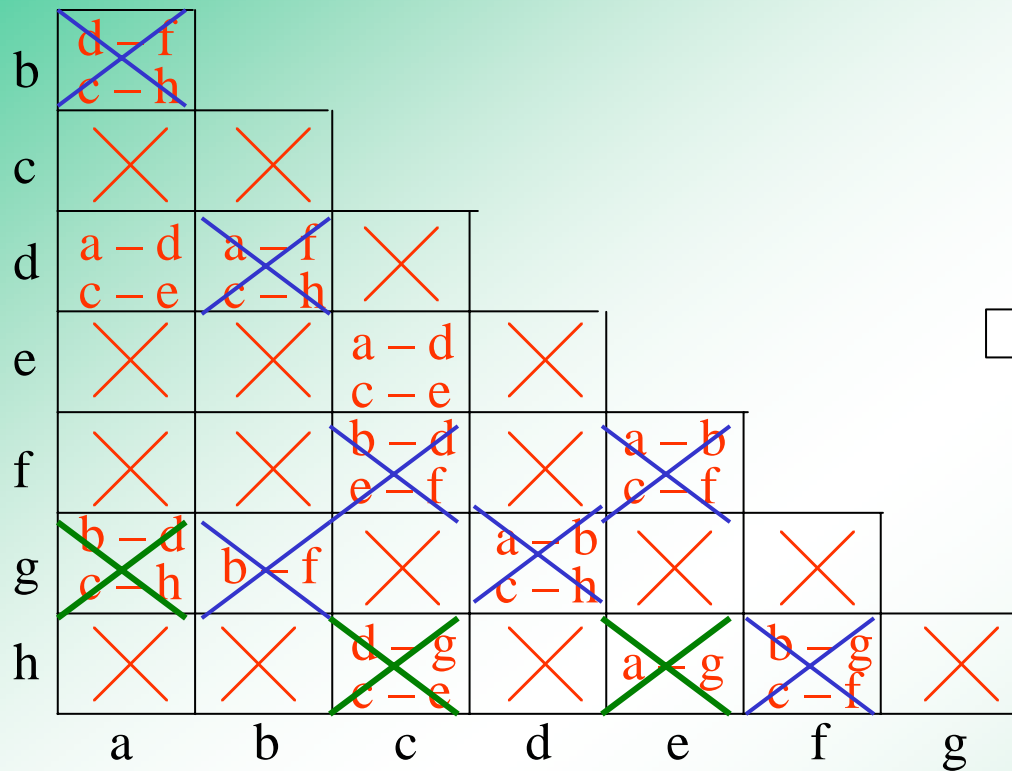

P.S.	N.S.		Z
	x = 0	x = 1	
a	a	c	0
b	f	h	0
c	c	a	1
f	f	b	1
g	b	h	0
h	c	g	1

$a \equiv d$   
 $c \equiv e$

# 15-4 Equivalent Sequential Circuits


*Definition* :  $N_1 \equiv N_2$  iff  $P$  in  $N_1 \equiv q$  in  $N_2$   
 $S$  in  $N_2 \equiv t$  in  $N_1$

*Ex:*


	$N_1$			
	x=0	x=1		
A	B	A	0	0
B	C	D	0	1
C	A	C	0	1
D	C	B	0	0

	$N_2$			
	x=0	x=1		
$S_0$	$S_3$	$S_1$	0	1
$S_1$	$S_3$	$S_0$	0	0
$S_2$	$S_0$	$S_2$	0	0
$S_3$	$S_2$	$S_3$	0	1

*Method 1. By observing*

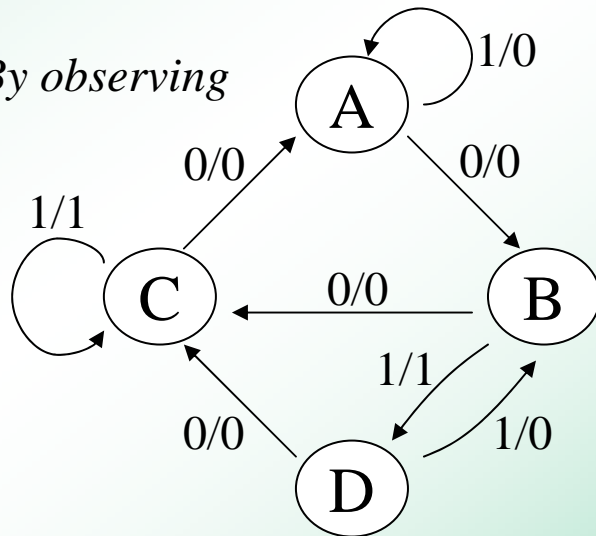

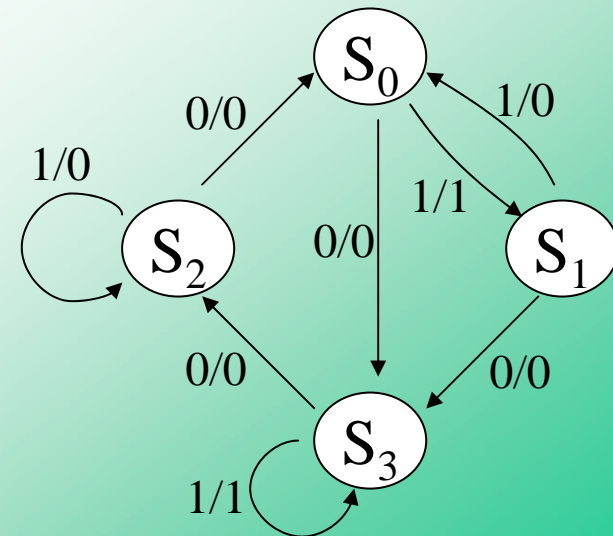$A \equiv S_2$   
 $B \equiv S_0$   
 $C \equiv S_3$   
 $D \equiv S_1$










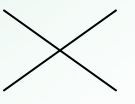
		$N_1$			
		$x=0$	$x=1$	$x=0$	$x=1$
A	B	A	0	0	
B	C	D	0	1	
C	A	C	0	1	
D	C	B	0	0	

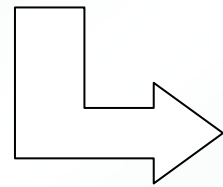
		$N_2$			
		$x=0$	$x=1$	$x=0$	$x=1$
$S_0$	$S_3$	$S_1$	0	1	
$S_1$	$S_3$	$S_0$	0	0	
$S_2$	$S_0$	$S_2$	0	0	
$S_3$	$S_2$	$S_3$	0	1	

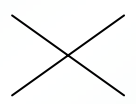







*Method 2. By implication table*

*1. Construct implication table by listing all state pair. X out pairs with different output*

$S_0$	<del> </del>	C - $S_3$ D - $S_1$	A - $S_3$ C - $S_1$	<del> </del>
$S_1$	B - $S_3$ A - $S_0$	<del> </del>	<del> </del>	C - $S_3$ B - $S_0$
$S_2$	B - $S_0$ A - $S_2$	<del> </del>	<del> </del>	C - $S_0$ B - $S_2$
$S_3$	<del> </del>	C - $S_2$ D - $S_3$	A - $S_2$ C - $S_3$	<del> </del>
	A	B	C	D

$S_0$		C - $S_3$ D - $S_1$	A - $S_3$ C - $S_1$	
$S_1$	B - $S_3$ A - $S_0$			C - $S_3$ B - $S_0$
$S_2$	B - $S_0$ A - $S_2$			C - $S_0$ B - $S_2$
$S_3$		C - $S_2$ D - $S_3$	A - $S_2$ C - $S_3$	
	A	B	C	D




$S_0$		C - $S_3$ D - $S_1$	<del>A - <math>S_3</math></del> <del>C - <math>S_1</math></del>	
$S_1$	<del>B - <math>S_3</math></del> <del>A - <math>S_0</math></del>			C - $S_3$ B - $S_0$
$S_2$	B - $S_0$ A - $S_2$			<del>C - <math>S_0</math></del> <del>B - <math>S_2</math></del>
$S_3$		<del>C - <math>S_2</math></del> <del>D - <math>S_3</math></del>	A - $S_2$ C - $S_3$	
	A	B	C	D

$$\Rightarrow A \equiv S_2 \quad B \equiv S_0 \quad C \equiv S_3 \quad D \equiv S_1$$

# 15-5 Incompletely Specified State Tables

*Ex:*

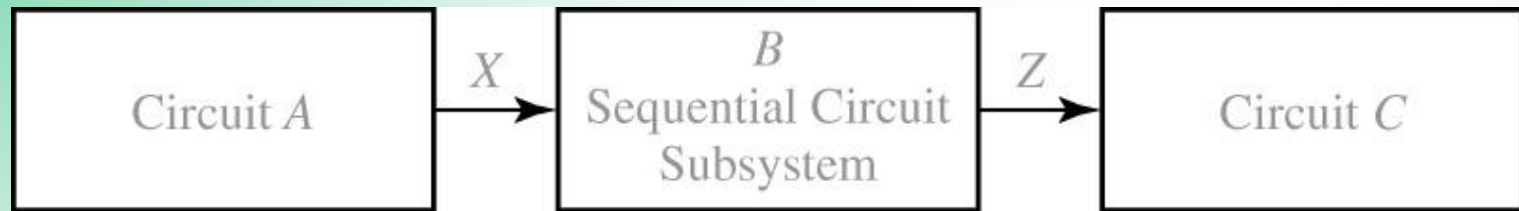

A can only give 100, 110


B gives  $\left\{ \begin{array}{l} \text{"0"} \\ \text{"1"} \end{array} \right.$  if  $\left\{ \begin{array}{l} 100 \text{ received} \\ 110 \text{ received} \end{array} \right.$  at 3rd bit

	$t_0$	$t_1$	$t_2$		$t_0$	$t_1$	$t_2$
$X =$	1	0	0	$Z =$	—	—	<b>0</b>
	1	1	0		—	—	<b>1</b>

*If don't cares are present, the state table is incompletely specified*




# State Graph for Network B:

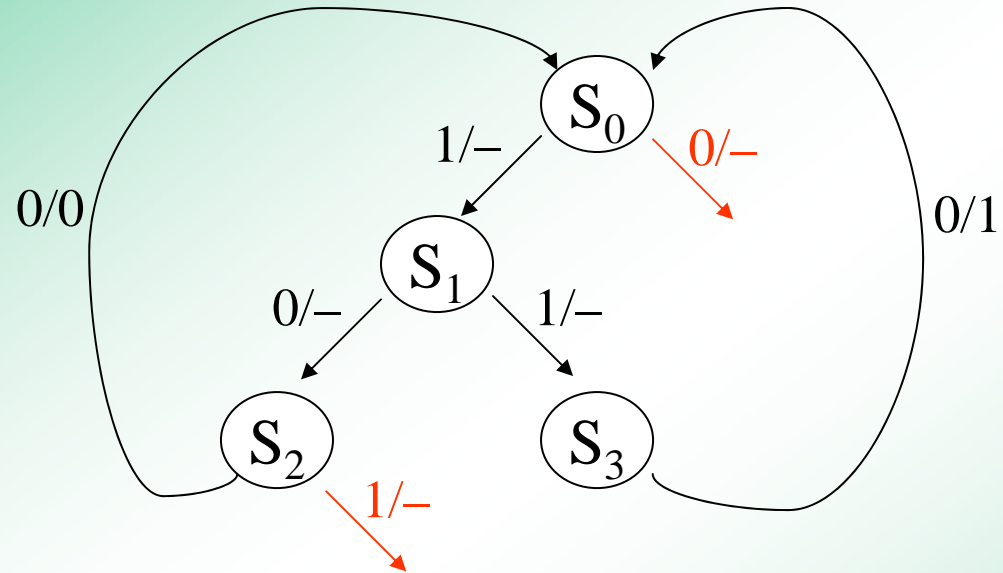

P.S.	N.S.		Z	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$S_0$	-	$S_1$	-	-
$S_1$	$S_2$	$S_3$	-	-
$S_2$	$S_0$	-	<b>0</b>	-
$S_3$	$S_0$	-	<b>1</b>	-

P.S.	N.S.		Z	
	x = 0	x = 1	x = 0	x = 1
S <sub>0</sub>	-(S <sub>0</sub> )	S <sub>1</sub>	-(0)	-
S <sub>1</sub>	<del>S<sub>2</sub></del> S <sub>0</sub>	-	-(1)	-
→ S <sub>2</sub>	S <sub>0</sub>	-(S <sub>1</sub> )	<b>0</b>	-
→ S <sub>3</sub>	S <sub>0</sub>	-	<b>1</b>	-

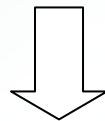

P.S.	N.S.		Z	
	x = 0	x = 1	x = 0	x = 1
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	<b>0</b>	-
S <sub>1</sub>	S <sub>0</sub>	-	<b>1</b>	-

Reduction of states !!

## 15-6 Derivation of F/F Input Equations

State Graph

⇒ State Table

⇒ State Assignment

⇒ State Transition Table

Choice of F/F!

⇒ K - map

⇒ F/F Input Equations

*Ex :*

P.S.	N.S.		Z	
	x = 0	x = 1	x = 0	x = 1
S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	0	0
S <sub>1</sub>	S <sub>3</sub>	S <sub>2</sub>	0	0
S <sub>2</sub>	S <sub>1</sub>	S <sub>4</sub>	0	0
S <sub>3</sub>	S <sub>5</sub>	S <sub>2</sub>	0	0
S <sub>4</sub>	S <sub>1</sub>	S <sub>6</sub>	0	0
S <sub>5</sub>	S <sub>5</sub>	S <sub>2</sub>	1	0
S <sub>6</sub>	S <sub>1</sub>	S <sub>6</sub>	0	1




7 states  $\Rightarrow$  3 F/F's A B C



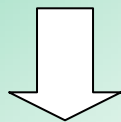Let S<sub>0</sub> = 000, S<sub>1</sub> = 110, S<sub>2</sub> = 001, S<sub>3</sub> = 111,  
S<sub>4</sub> = 011, S<sub>5</sub> = 101, S<sub>6</sub> = 010





## Transition Table

A	B	C	$A+B+C$		Z	
			x = 0	x = 1	x = 0	x = 1
0	0	0	110	001	0	0
1	1	0	111	001	0	0
0	0	1	110	011	0	0
1	1	1	101	001	0	0
0	1	1	110	010	0	0
1	0	1	101	001	1	0
0	1	0	110	010	0	1



(1) Choose D-F/F

$Q^+$	$D$
0	0
1	1

ABC	$D_A$		$D_B$		$D_C$	
	$X=0$	$X=1$	$X=0$	$X=1$	$X=0$	$X=1$
000	1	0	1	0	0	1
110	1	0	1	0	1	1
001	1	0	1	1	0	1
111	1	0	0	0	1	1
011	1	0	1	1	0	0
101	1	0	0	0	1	1
010	1	0	1	1	0	0



ABC	$D_A$		$D_B$		$D_C$	
	$X=0$	$X=1$	$X=0$	$X=1$	$X=0$	$X=1$
000	1	0	1	0	0	1
001	1	0	1	1	0	1
010	1	0	1	1	0	0
011	1	0	1	1	0	0
100	×	×	×	×	×	×
101	1	0	0	0	1	1
110	1	0	1	0	1	1
111	1	0	0	0	1	1



ABC	$D_A$		$D_B$		$D_C$	
	0	X=1	0	X=1	0	X=1
000	1	0	1	0	0	1
001	1	0	1	1	0	1
010	1	0	1	1	0	0
011	1	0	1	1	0	0
100	x	x	x	x	x	x
101	1	0	0	0	1	1
110	1	0	1	0	1	1
111	1	0	0	0	1	1

BC \ XA	00	01	11	10
	00	1	x	x
01	1	1	0	0
11	1	1	0	0
10	1	1	0	0

$$A^+ = D_A = X'$$

BC \ XA	00	01	11	10
	00	1	x	x
01	1	0	0	1
11	1	0	0	1
10	1	1	0	1

$$B^+ = D_B = X'C' + A'C + A'B$$

BC \ XA	00	01	11	10
	00	0	x	x
01	0	1	1	1
11	0	1	1	0
10	0	1	1	0

$$C^+ = D_C = A + XB'$$

Derivation of D F/F input equations

(2) Choose J-K F/F

Q	Q <sup>+</sup>	J	K
0	0	0	×
0	1	1	×
1	0	×	1
1	1	×	0

ABC	A <sup>+</sup> B <sup>+</sup> C <sup>+</sup> X=		J <sub>A</sub> K <sub>A</sub> X=		J <sub>B</sub> K <sub>B</sub> X=		J <sub>C</sub> K <sub>C</sub> X=	
	0	1	0	1	0	1	0	1
000	110	001	1×	0×	1×	0×	0×	1×
110	111	001	×	0	×	1	1×	1×
001	110	011	1×	1×	:	:	:	:
111	101	001	×	0	×	1	:	:
011	110	010	1×	×	0	:	:	:
101	101	001	×	0	0×	:	:	:
010	110	010	×	0	×	0	:	:





## Next State Map

		Q	
		0	1
AB	00	0	1
	01	1	0
	11	0	0
	10	1	x

$Q_+$

## D- F/F Input Map

		0	1
AB	00	0	1
	01	1	0
	11	0	0
	10	1	x

$$D = Q'A'B' + QB' + AB'$$

# Derivation of Flip-Flop Input Equations from Next State Maps

Type of F/F	Input	Q=0		Q=1		Rules for forming input map from next state map	
		Q+ =0	Q+=1	Q+ = 0	Q+ = 1	Q=0 Half of Map	Q=1 Half of Map
D-F/F	D	0	1	0	1	No change	No change
T-F/F	T	0	1	1	0	No change	Complement

Next State Map

		Q	
		0	1
AB			
00		0	1
01		1	0
11		0	0
10		1	x

$Q^+$

T – F/F Input Map

		Q	
		0	1
AB			
00		0	0
01		1	1
11		0	1
10		1	x

$$T = A'B + AB' + QB$$

## Derivation of Flip-Flop Input Equations from Next State Maps

Type of F/F	Input	Q=0		Q=1		Rules for forming input map from next state map	
		Q+ =0	Q+=1	Q+ = 0	Q+ = 1	Q=0 Half of Map	Q=1 Half of Map
D-F/F	D	0	1	0	1	No change	No change
T-F/F	T	0	1	1	0	No change	Complement
S-R F/F	S	0	1	0	x	No change	Replace 1's with x's
	R	x	0	1	0	*Replace 0's with x's *Replace 1's with 0's	Complement

## Next State Map

		Q	0	1
AB				
00			0	1
01			1	0
11			0	0
10			1	x

$Q_+$

## R-S F/F Input Maps

		0	1
AB			
00		0	x
01		1	0
11		0	0
10		1	x

		0	1
AB			
00		x	0
01		0	1
11		x	1
10		0	x

$$S = AB' + Q'A'B$$

$$R = QB$$

## Derivation of Flip-Flop Input Equations from Next State Maps

Type of F/F	Input	Q=0		Q=1		Rules for forming input map from next state map	
		Q+ =0	Q+ =1	Q+ = 0	Q+ = 1	Q=0 Half of Map	Q=1 Half of Map
D-F/F	D	0	1	0	1	No change	No change
T-F/F	T	0	1	1	0	No change	Complement
R-S F/F	S	0	1	0	x	No change	Replace 1's with x's
	R	x	0	1	0	*Replace 0's with x's *Replace 1's with 0's	Complement
J-K F/F	J	0	1	x	x	No change	Fill in with x's
	K	x	x	1	0	Fill in with x's	Complement

## Next State Map

		Q	
		0	1
AB	00	0	1
	01	1	0
	11	0	0
	10	1	x

$Q+$

## J-K F/F Input Maps

		0		1	
		0	1	0	1
AB	00	0	x	x	0
	01	1	x	x	1
	11	0	x	x	1
	10	1	x	x	x

$J = A'B + AB'$

$K = B$



# Next - State Maps


ABC	A+		B+		C+	
	0	X=1	0	X=1	0	X=1
000	1	0	1	0	0	1
001	1	0	1	1	0	1
010	1	0	1	1	0	0
011	1	0	1	1	0	0
100	×	×	×	×	×	×
101	1	0	0	0	1	1
110	1	0	1	0	1	1
111	1	0	0	0	1	1

BC	XA			
	00	01	11	10
00	1	×	×	0
01	1	1	0	0
11	1	1	0	0
10	1	1	0	0

BC	XA			
	00	01	11	10
00	1	×	×	0
01	1	0	0	1
11	1	0	0	1
10	1	1	0	1


BC	XA			
	00	01	11	10
00	0	×	×	1
01	0	1	1	1
11	0	1	1	0
10	0	1	1	0
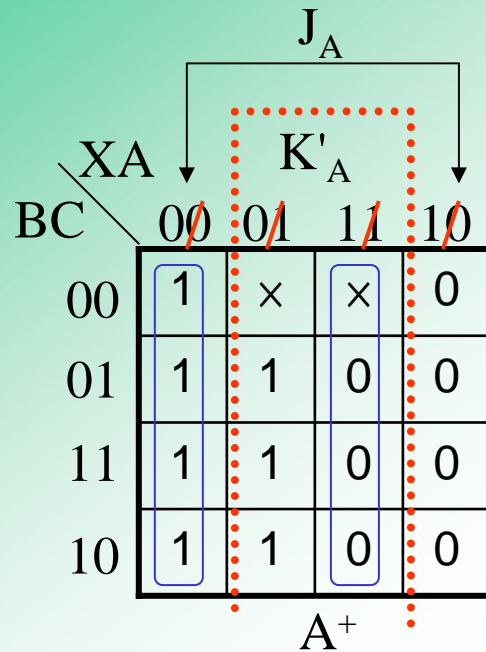
# Derivation of J-K Input Equations from Next State Maps




$$J_A = X'$$

$$K_A = X$$

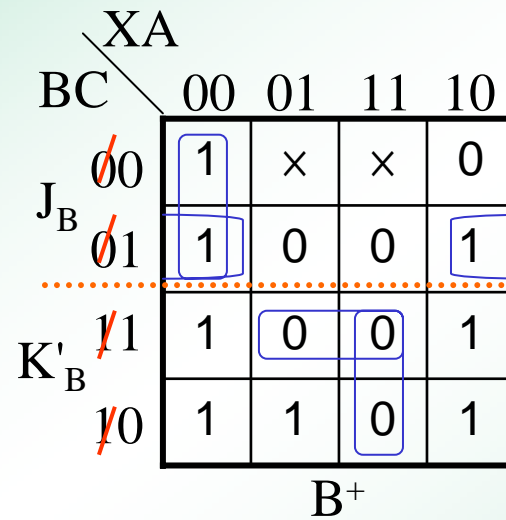

$$J_B = X'A' + A'C$$

$$K_B = AC + XA$$

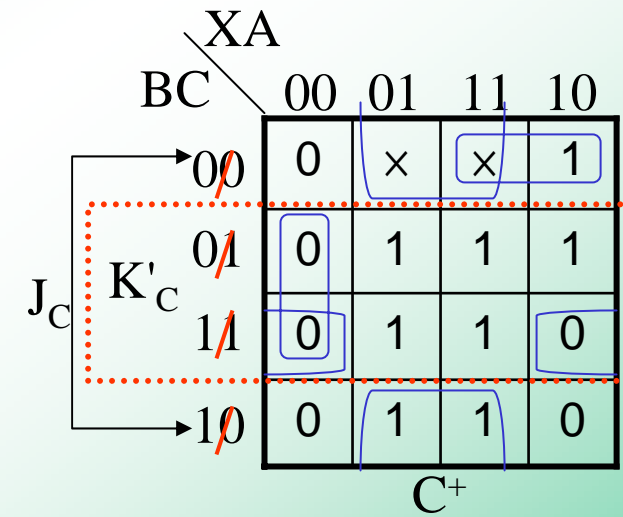

$$J_C = A + XB'$$

$$K_C = X'A' + A'B$$


Derivation of J-k F/F input equations

(3) Choose S-R F/F

Q	Q <sup>+</sup>	S	R
0	0	0	×
0	1	1	0
1	0	0	1
1	1	×	0

ABC	$A^+B^+C^+$ X=		$S_A R_A$ X=		$S_B R_B$ X=		$S_C R_C$ X=	
	0	1	0	1	0	1	0	1
000	110	001	1 0	0 x	:	:	:	:
110	111	001	x 0	0 1	:	:	:	:
001	110	011	1 0	0 x	:	:	:	:
111	101	001	x 0	0 1	:	:	:	:
011	110	010	1 0	0 x	:	:	:	:
101	101	001	x 0	0 1	:	:	:	:
010	110	010	1 0	0 x	:	:	:	:

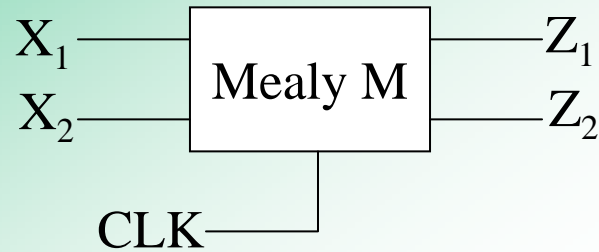*Ex:* Another example with 2 inputs  $X_1X_2$  , 2 outputs  $Z_1Z_2$



P.S.	N.S.				Z			
	$x_1x_2=$				$x_1x_2=$			
	00	01	11	10	00	01	11	10
$S_0$	$S_0$	$S_0$	$S_1$	$S_1$	00	00	01	01
$S_1$	$S_1$	$S_3$	$S_2$	$S_1$	00	10	10	00
$S_2$	$S_3$	$S_3$	$S_2$	$S_2$	11	11	00	00
$S_3$	$S_0$	$S_3$	$S_2$	$S_0$	00	00	00	00

4 states  $\Rightarrow$  2 F/F' s A , B

State Assignment :  $S_0 = 00$  ,  $S_1 = 01$  ,  $S_2 = 11$  ,  $S_3 = 10$

# State transition Table

P.S. AB	N.S.				Z			
	$x_1x_2=$ 00	01	11	10	$x_1x_2=$ 00	01	11	10
00	00	00	01	01	00	00	01	01
01	01	10	11	01	00	10	10	00
11	10	10	11	11	11	11	00	00
10	00	10	11	00	00	00	00	00

# D-F/F

		XA			
BC		00	01	11	10
00		0	0	0	0
01		0	1	1	0
11		1	1	1	1
10		0	1	1	0

$$D_A = A^+ = X_2 B + AB + X_2 A$$

		XA			
BC		00	01	11	10
00		0	0	1	1
01		1	0	1	1
11		0	0	1	1
10		0	0	1	0

$$D_B = B^+ = X_1 A + X_2' A' B + X_1 B + X_1 X_2$$

		XA			
BC		00	01	11	10
00		0	0	0	0
01		0	1	1	0
11		1	1	0	0
10		0	0	0	0

$$Z_1 = X_2 A' B + X_1' A B$$

		XA			
BC		00	01	11	10
00		0	0	1	1
01		0	0	0	0
11		1	1	0	0
10		0	0	0	0

$$Z_2 = X_1 A' B' + X_1' A B$$

# S-R F/F

Q	Q <sup>+</sup>	S	R
0	0	0	×
0	1	1	0
1	0	0	1
1	1	×	0

		XA			
		00	01	11	10
A=0	BC	00	0	0	0
	01	0	1	1	0
A=1	11	×	×	×	×
	10	0	×	×	0

$$S_A = X_2 B$$

		XA			
		00	01	11	10
A=0	BC	00	×	×	×
	01	×	0	0	×
A=1	11	0	0	0	0
	10	1	0	0	1

$$R_A = X_2 'B'$$

		XA			
		00	01	11	10
B=0	BC	00	0	0	1
	01	0	0	×	×
B=1	11	×	0	×	×
	10	0	0	1	0

$$S_B = X_1 X_2 + X_1 A'$$

		XA			
		00	01	11	10
B=0	BC	00	×	×	0
	01	0	1	0	0
B=1	11	1	1	0	0
	10	×	×	0	×

$$R_B = X_1 'X_2 + X_1 'A$$

# Derivation of F/F Input Equations

State Graph

⇒ State Table

⇒ State Assignment

⇒ State Transition Table

⇒ K - map ← (Choice of F/F)

⇒ F/F Input Equations

Different state assignment

⇒ different F/F Input Equations !



# 15-7 Equivalent State Assignments

§ Cost of logic strongly depends on state assignments.

*Ex:*

	Assign 1	Assign 2	P.S.	N.S.		Z	
	AB	AB		x = 0	x = 1	x = 0	x = 1
	11	00	S <sub>1</sub>	S <sub>1</sub>	S <sub>3</sub>	0	0
	10	01	S <sub>2</sub>	S <sub>2</sub>	S <sub>1</sub>	0	1
	01	10	S <sub>3</sub>	S <sub>2</sub>	S <sub>3</sub>	1	0


## \* Assignment 1

$$S_1 = 00, S_2 = 01, S_3 = 10$$

D - F/F : 2 F/F's A, B

$$D_A = XB' \quad D_B = X'(A + B)$$

## NOR implementation

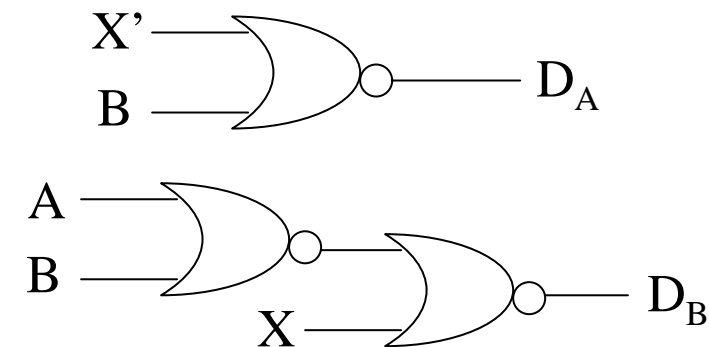



## \* Assignment 2

$$S_1 = 11, S_2 = 10, S_3 = 01$$

D - F/F : 2 F/F's A, B

$$D_A = X' + B' \quad D_B = X + A'B'$$

### NOR implementation

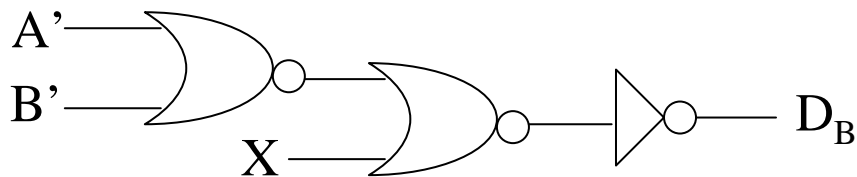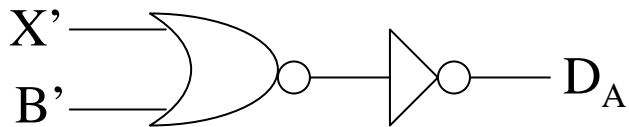

$\Rightarrow$  2 more gates for  
NOR implementation

# Adjacent states

2 states are adjacent

$S_1(010) \longleftrightarrow S_2(011)$

$(100) \longleftrightarrow (110)$

$S_1(010) \quad S_2(111)$

$(001) \quad (111)$

} adjacent

} not adjacent

## 15-8 Guidelines for State Assignment

work for D F/F , J - K F/F

not for T F/F , S - R F/F

1. States which have the same next state should be given adjacent assignment .
2. States which are next states of the same state should be given adjacent assignment .
3. States which have the same output  
⇒ adjacent states


In above order !!



To minimize  
output function


No guarantee a minimum solution

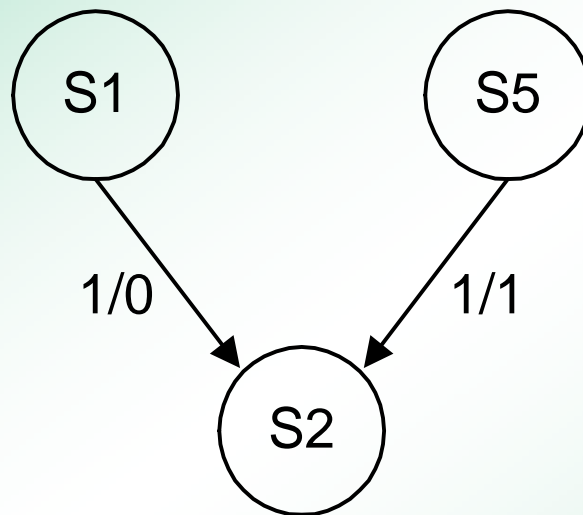**Guideline 1**：在相同的input條件下，會跳到同一個next state的states。  
state has the same n. s.




根據guideline 1，S1、S5需要相鄰。

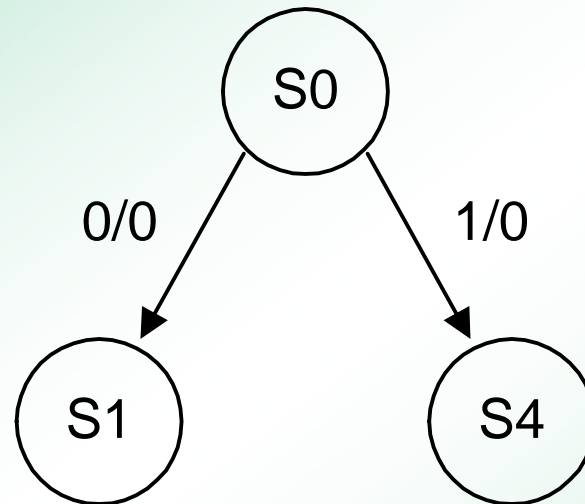**Guideline 2** : 同一個state跳出來的next states。  
states has the same p. s.



根據guideline 2，S1、S4需要相鄰。

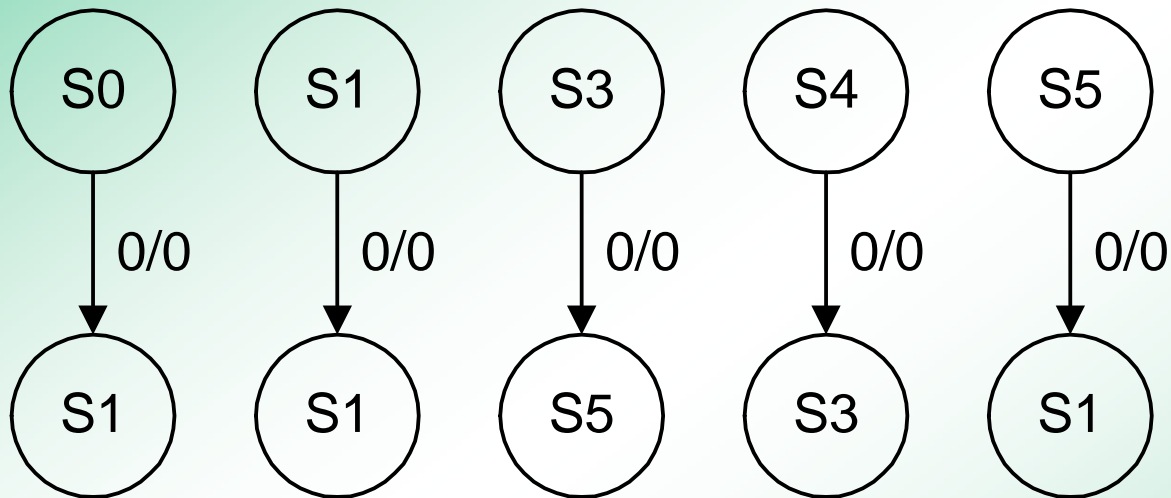**Guideline 3**：在相同的input條件下，會產生相同output的states。  
same output states



根據guideline 3，S0、S1、S3、S4、S5需要相鄰。

*Ex:*

P.S.	N.S.		Z	
	x = 0	x = 1	x = 0	x = 1
S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	0	0
S <sub>1</sub>	S <sub>3</sub>	S <sub>2</sub>	0	0
S <sub>2</sub>	S <sub>1</sub>	S <sub>4</sub>	0	0
S <sub>3</sub>	S <sub>5</sub>	S <sub>2</sub>	0	0
S <sub>4</sub>	S <sub>1</sub>	S <sub>6</sub>	0	0
S <sub>5</sub>	S <sub>5</sub>	S <sub>2</sub>	1	0
S <sub>6</sub>	S <sub>1</sub>	S <sub>6</sub>	0	1

3 F/F's A, B, C

### 1. list relationship

States having the same n.s.

Rule 1: (S<sub>0</sub>, S<sub>1</sub>, S<sub>3</sub>, S<sub>5</sub>) (S<sub>3</sub>, S<sub>5</sub>) (S<sub>4</sub>, S<sub>6</sub>) (S<sub>0</sub>, S<sub>2</sub>, S<sub>4</sub>, S<sub>6</sub>)

Rule 2: (S<sub>1</sub>, S<sub>2</sub>) (S<sub>2</sub>, S<sub>3</sub>) (S<sub>1</sub>, S<sub>4</sub>) (S<sub>2</sub>, S<sub>5</sub>) × 2 (S<sub>1</sub>, S<sub>6</sub>) × 2

States having the same p.s.



## 2. Use an assignment map

	A	0	1
BC			
00		$S_0$	
01		$S_2$	$S_5$
11		$S_4$	$S_3$
10		$S_6$	$S_1$

Assignment (a)

	A	0	1
BC			
00		$S_0$	
01		$S_1$	$S_6$
11		$S_3$	$S_4$
10		$S_5$	$S_2$

Assignment (b)

States having the same n.s.  
*Rule 1:*  $(S_0, S_1, S_3, S_5) (S_3, S_5) (S_4, S_6) (S_0, S_2, S_4, S_6)$

*Rule 2:*  $(S_1, S_2) (S_2, S_3) (S_1, S_4) (S_2, S_5) \times 2 (S_1, S_6) \times 2$

States having the same p.s.

High  
priority

# Assignment(a)

	P.S.	N.S.		Z	
		x = 0	x = 1	x = 0	x = 1
000	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	0	0
110	S <sub>1</sub>	S <sub>3</sub>	S <sub>2</sub>	0	0
001	S <sub>2</sub>	S <sub>1</sub>	S <sub>4</sub>	0	0
111	S <sub>3</sub>	S <sub>5</sub>	S <sub>2</sub>	0	0
011	S <sub>4</sub>	S <sub>1</sub>	S <sub>6</sub>	0	0
101	S <sub>5</sub>	S <sub>5</sub>	S <sub>2</sub>	1	0
010	S <sub>6</sub>	S <sub>1</sub>	S <sub>6</sub>	0	1

6 gates 13 literals

## Another straight forward assignment


	P.S.	N.S.		Z	
		x = 0	x = 1	x = 0	x = 1
000	S <sub>0</sub>	S <sub>1</sub>	S <sub>2</sub>	0	0
001	S <sub>1</sub>	S <sub>3</sub>	S <sub>2</sub>	0	0
010	S <sub>2</sub>	S <sub>1</sub>	S <sub>4</sub>	0	0
011	S <sub>3</sub>	S <sub>5</sub>	S <sub>2</sub>	0	0
100	S <sub>4</sub>	S <sub>1</sub>	S <sub>6</sub>	0	0
101	S <sub>5</sub>	S <sub>5</sub>	S <sub>2</sub>	1	0
110	S <sub>6</sub>	S <sub>1</sub>	S <sub>6</sub>	0	1

10 gates 39 literals

# Why guideline help ?

ABC		$A+B+C^+$				$Z$	
		$x=0$		$x=1$		$x=0$	$x=1$
000	$S_0$	110	$S_1$	001	$S_2$	0	0
110	$S_1$	111	$S_3$	001	$S_2$	0	0
001	$S_2$	110	$S_1$	011	$S_4$	0	0
111	$S_3$	101	$S_5$	001	$S_2$	0	0
011	$S_4$	110	$S_1$	010	$S_6$	0	0
101	$S_5$	101	$S_5$	001	$S_0$	1	0
010	$S_6$	110	$S_1$	010	$S_6$	0	1

Next state map

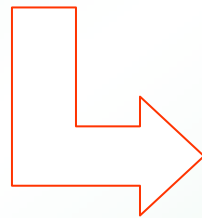

State transition graph

	ABC	$A+B+C^+$				$Z$	
		$x=0$		$x=1$		$x=0$	$x=1$
$S_0$	000	110	$S_1$	001	$S_2$	0	<b>0</b>
$S_2$	001	110	$S_1$	011	$S_4$	0	<b>0</b>
$S_6$	010	110	$S_1$	010	$S_6$	0	<b>1</b>
$S_4$	011	110	$S_1$	010	$S_6$	0	<b>0</b>
–	100	×××		×××		–	–
$S_5$	101	<b>101</b>	$S_5$	<b>001</b>	$S_2$	<b>1</b>	<b>0</b>
$S_1$	110	<b>111</b>	$S_3$	<b>001</b>	$S_2$	<b>0</b>	<b>0</b>
$S_3$	111	<b>101</b>	$S_5$	<b>001</b>	$S_2$	<b>0</b>	<b>0</b>

# Next state map

BC \ XA	00	01	11	10
00	$S_1$	×	×	$S_2$
01	$S_1$	$S_5$	$S_2$	$S_4$
11	$S_1$	$S_5$	$S_2$	$S_6$
10	$S_1$	$S_3$	$S_2$	$S_6$

$S_0$  (points to 00,00 and 00,10)  
 $S_2$  (points to 01,00 and 01,10)  
 $S_4$  (points to 11,00 and 11,10)  
 $S_6$  (points to 10,00 and 10,10)  
 $S_3$  (points to 01,01 and 10,01)  
 $S_5$  (points to 01,11 and 10,11)  
 $S_1$  (points to 11,01 and 10,11)  
 $S_3$  (points to 11,01 and 10,01)

BC \ XA	00	01	11	10
00	1	×	×	0
01	1	1	0	0
11	1	1	0	0
10	1	1	0	0

$$A^+ = X'$$

BC \ XA	00	01	11	10
00	1	×	×	1
01	1	0	0	1
11	1	0	0	1
10	1	1	0	1

BC \ XA	00	01	11	10
00	0	×	×	1
01	0	1	1	1
11	0	1	1	0
10	0	1	1	0

due to  $S_2$   $S_5$  assignment

Ex:

P.S.	N.S.		Z	
	x = 0	x = 1	x = 0	x = 1
a	a	c	0	0
b	d	f	0	1
c	c	a	0	0
d	d	b	0	1
e	b	f	1	0
f	c	e	1	0

## Guidelines

**1.** ( b,d ) ( c,f ) ( b,e )

**2.** ( a,c ) × 2 , ( d,f ) ( b,d )

( b,f ) ( c,e )

**3.** ( a,c ) ( b,d ) ( e,f )

## Assignment (a)

		$Q_1$		
		0	1	
$Q_2Q_3$	00	a	c	a = 000 b = 111
	01		e	c = 100
	11	b	d	d = 011
	10		f	e = 101 f = 110

## Assignment (b)

		$Q_1$		
		0	1	
$Q_2Q_3$	00	c	a	a = 100 b = 111
	01		e	c = 000
	11	d	b	d = 011
	10	f		e = 101 f = 010

1.  $(\underline{b,d}) (c,f) (b,e)$

2.  $(a,c) \times 2, (d,f) (\underline{b,d})$

$(b,f) (c,e)$

3.  $(a,c) (b,d) (e,f)$

## For Assignment (b)

	P.S.	N.S.		Z	
	$Q_1 Q_2 Q_3$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
$m_4$	100	100	000	0	0
$m_7$	111	011	010	0	1
$m_0$	000	000	100	0	0
$m_3$	011	011	111	0	1
$m_5$	101	111	010	1	0
$m_2$	010	000	101	1	0
$m_1$	001	---	---	-	-
$m_6$	110	---	---	-	-





# State Transition Table

	P.S. $Q_1 Q_2 Q_3$	N.S.		Z	
		$x = 0$	$x = 1$	$x = 0$	$x = 1$
$m_0$	000	000	100	0	0
$m_1$	001	---	---	-	1
$m_2$	010	000	101	1	0
$m_3$	011	011	111	0	1
$m_4$	100	100	000	0	0
$m_5$	101	111	010	1	0
$m_6$	110	---	---	-	-
$m_7$	111	<b>011</b>	<b>010</b>	<b>0</b>	<b>1</b>


next state map

		$xQ_1$			
		00	01	11	10
$Q_2 Q_3$	00	000	100	000	100
	01	×	111	010	×
	11	011	011	010	111
	10	000	×	×	101

# Next State Map

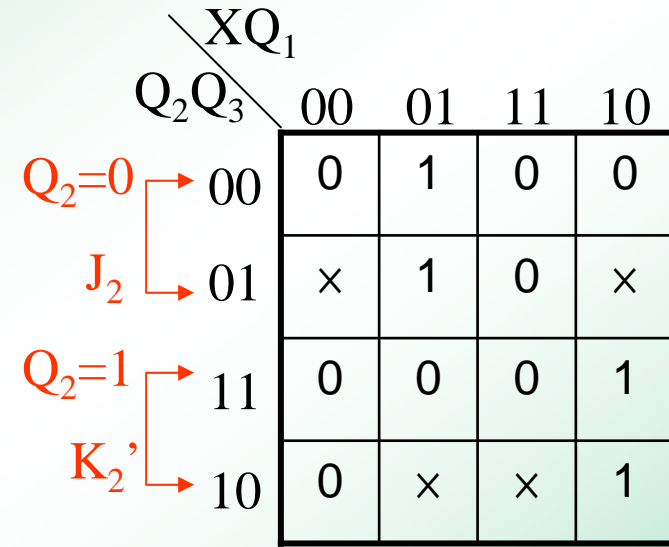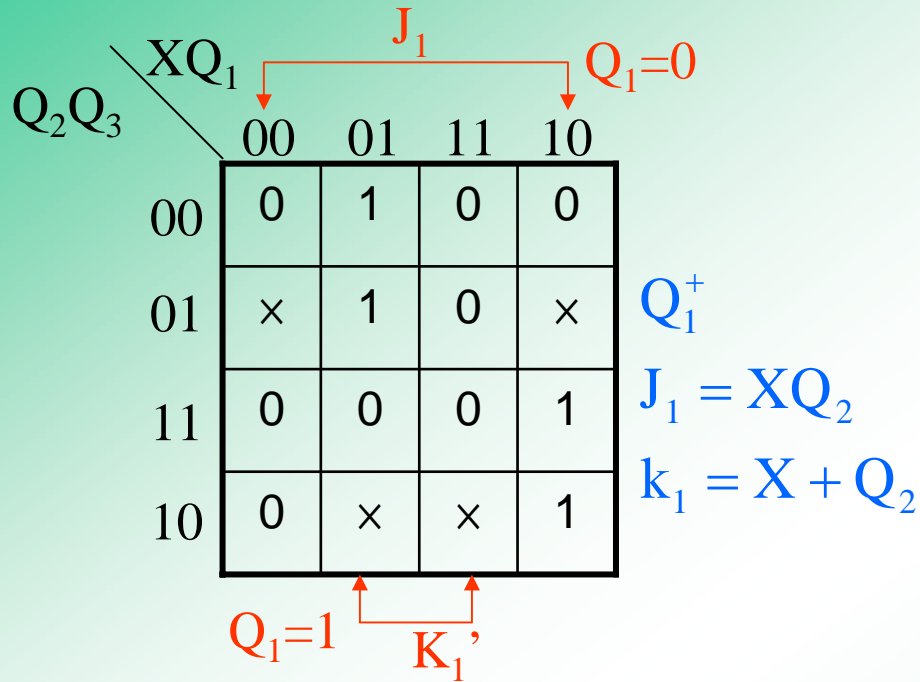

$Q_2^+$   
 $J_2 = Q_3$   
 $k_2 = Q_3'$

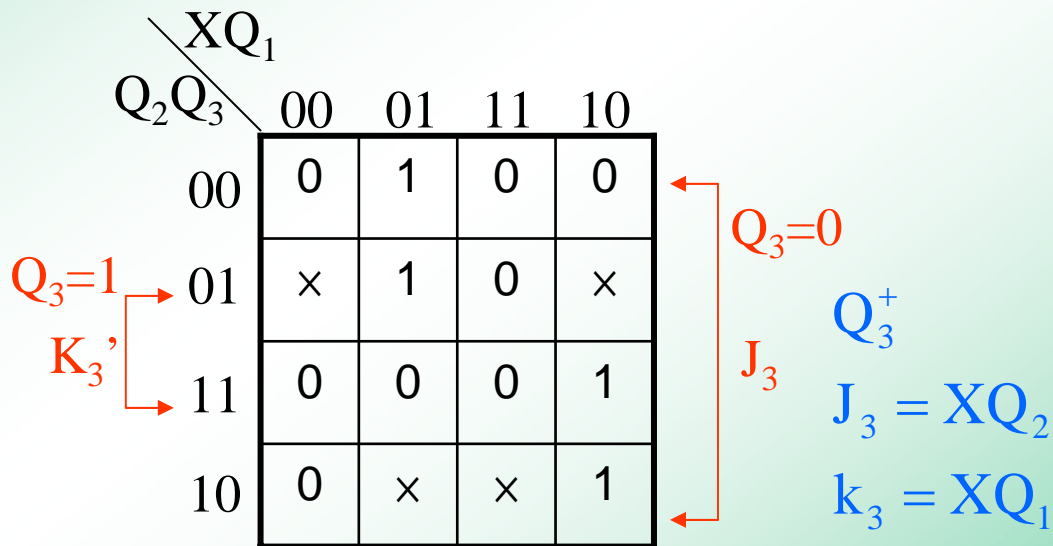

# D - F/F Implementation

		$XQ_1$			
$Q_2Q_3$		00	01	11	10
00			1		1
01		x	1		x
11					1
10			x	x	1

$$Q_1^+ = X'Q_1Q_2' + XQ_2'$$

		$XQ_1$			
$Q_2Q_3$		00	01	11	10
00					
01		x	1	1	x
11		1	1	1	1
10			x	x	

$$Q_2^+ = Q_3$$

		$XQ_1$			
$Q_2Q_3$		00	01	11	10
00					
01		x	1		x
11		1	1		1
10			x	x	1


$$Q_3^+ = XQ_1'Q_3 + X'Q_2Q_3'$$

		$XQ_1$			
$Q_2Q_3$		00	01	11	10
00					
01		x	1		x
11				1	1
10		1	x	x	

$$Z = XQ_2Q_3 + X'Q_2'Q_3 + X'Q_2Q_3'$$
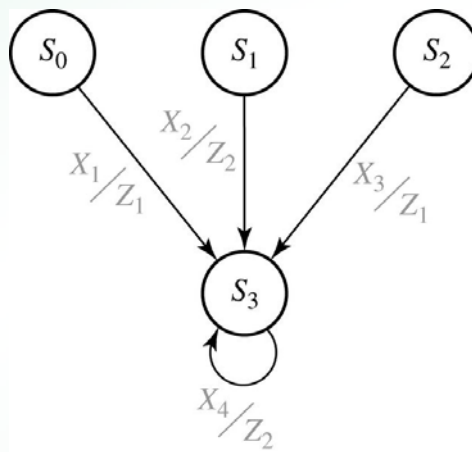
## 15-9 Using a One-Hot State Assignment


- When design with CPLD and FPGAs, it may not be important to minimize the number of F/F used in the design
- In order to design faster logic, the number of cells and interconnections between cells should be reduced
- **One-hot state assignment**
  - Using one F/F only for each state
  - 4 states use 4 F/F ( $Q_0, Q_1, Q_2, Q_3$ ) with following state assignment  
 $\mathbf{S_0: } Q_0Q_1Q_2Q_3=1000, \mathbf{S_1: } 0100, \mathbf{S_2: } 0010, \mathbf{S_3: } 0001$



Write next-state and output eq.  
directly by inspecting the state graph

$$Q_3^+ = X_1Q_0 + X_2Q_1 + X_3Q_2 + X_4Q_3$$

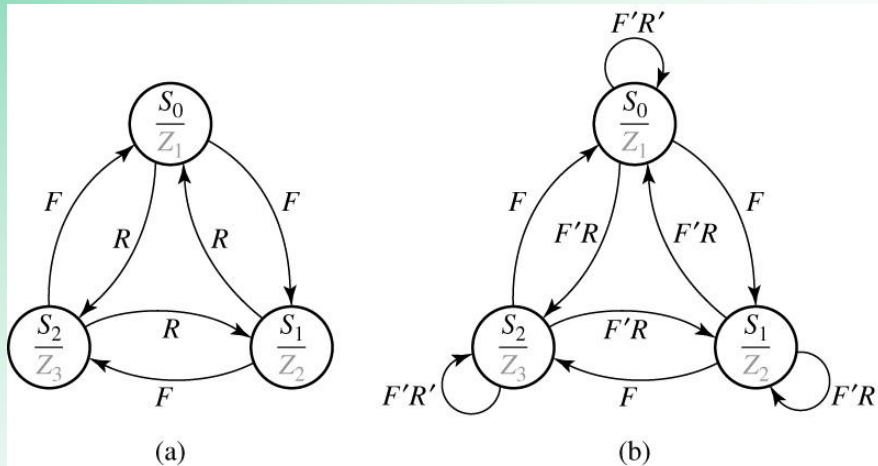- For Moore machine,  
 $S_0: Q_0Q_1Q_2=100$ ,  $S_1: 010$ ,  $S_2: 001$



$$Q_1^+ = F'R'Q_0 + FQ_2 + F'RQ_1$$

$$Q_2^+ = F'R'Q_1 + FQ_0 + F'RQ_2$$


$$Q_3^+ = F'R'Q_2 + FQ_1 + F'RQ_0$$

$$Z_1 = Q_0 \quad Z_2 = Q_1 \quad Z_3 = Q_2$$

- When design with CPLDs or FPGAs, try both an assignment with a minimum number of state variables and a one-hot assignment

# HOMEWORK -- Unit 15

- 15. 8
- 15. 20
- 15. 28

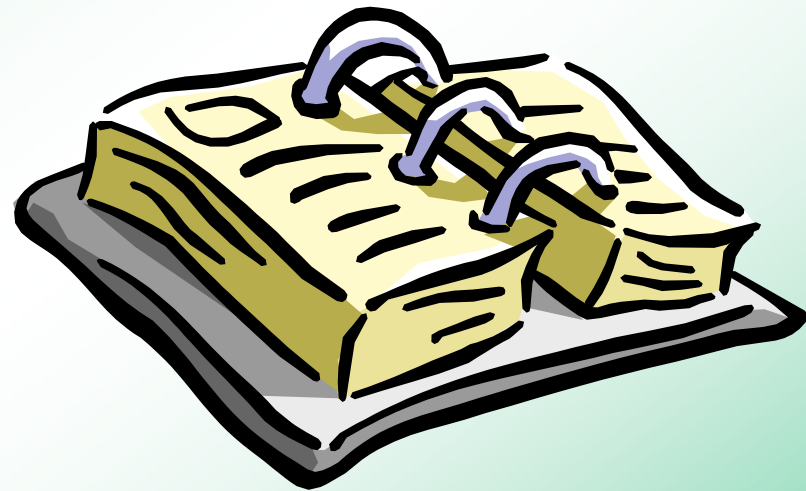

# A Short Cut Method to Find J-K Flip-Flop Input Equations

∴ For J-K F/F :  $J_A, K_A$  independent of  $Q_A$  又  $Q^+ = JQ' + K'Q$

⇒  $Q = 0$ 時  $Q^+ = J$        $Q = 1$ 時  $Q^+ = K'$

## Example

Next state map:  $Q_A^+ \quad Q_B^+ \quad Q_C^+$

Q	Q <sup>+</sup>	J	K
0	0	0	×
0	1	1	×
1	0	×	1
1	1	×	0

P.S. $Q_A Q_B Q_C$	N. S. $Q_A^+ Q_B^+ Q_C^+$	$Q_A$	
		0	1
000	111	1	1
001	xxx	×	×
010	000	0	0
011	000	0	0
100	111	0	×
101	xxx		
110	xxx		
111	000		

$Q_B Q_C$	$Q_A$		$Q_A^+$
	0	1	
00	1	1	
01	×	×	
11	0	0	
10	0	×	

$Q_B Q_C$	$Q_A$		$Q_B^+$
	0	1	
00	1	1	
01	×	×	
11	0	0	
10	0	×	

$Q_B Q_C$	$Q_A$		$Q_C^+$
	0	1	
00	1	1	
01	×	×	
11	0	0	
10	0	×	

∴ For J-K F/F :  $J_A, K_A$  independent of  $Q_A$  又  $Q^+ = JQ' + K'Q$

⇒  $Q=0$ 時  $Q^+ = J$        $Q=1$ 時  $Q^+ = K'$

Next state map:  $Q_A^+ \quad Q_B^+ \quad Q_C^+$

		$Q_A$	
		$0$	$1$
$Q_B$	$Q_C$	$0$	$1$
	$0$	$1$	$1$
$0$	$1$	$\times$	$\times$
$1$	$1$	$0$	$0$
$1$	$0$	$0$	$\times$

$J_A$  map |  $K'_A$  map

$Q_A^+$

$J_A = B' \quad K_A = B \text{ or } C$

		$Q_A$		$J_B$ map
		$0$	$1$	
$Q_B$	$Q_C$	$0$	$1$	} $B=0$
	$0$	$1$	$1$	
$0$	$1$	$\times$	$\times$	} $B=1$
$1$	$1$	$0$	$0$	
$1$	$0$	$0$	$\times$	

$Q_B^+ \quad K'_B$  map

$J_B=1 \quad K_B=1$

		$Q_A$		$J_C$ map
		$0$	$1$	
$Q_B$	$Q_C$	$0$	$1$	} $C=0$
	$0$	$1$	$1$	
$0$	$1$	$\times$	$\times$	} $C=1$
$1$	$1$	$0$	$0$	
$1$	$0$	$0$	$\times$	

$Q_C^+$

$J_C=B' \quad K_C=1$