
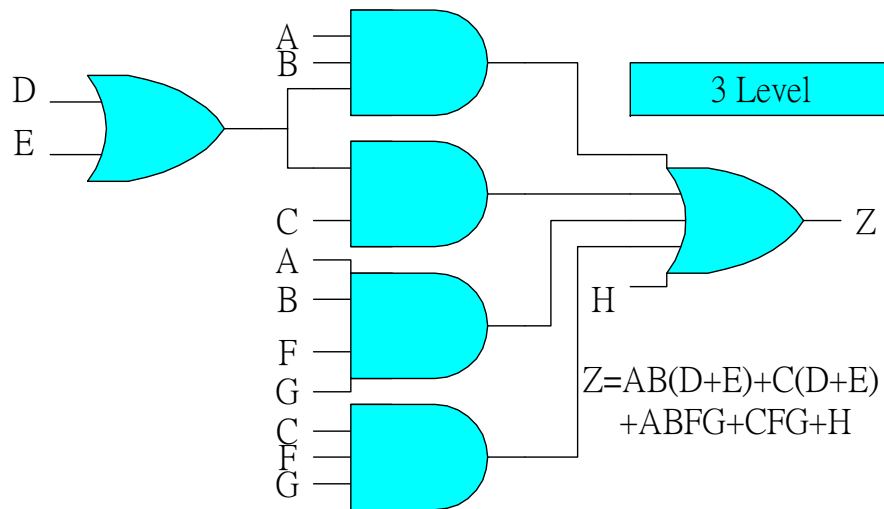


Unit 7.

Multi-Level Gate Networks NAND and NOR Gates

Multi Level Network

 


AND – OR : 2-level SOP
OR - AND : 2-level POS
OR - AND - OR : 3-level
 Network of AND and OR
 ⇒ no particular ordering

Gate Number & Delays determine level

Factoring to accomplish different level..

Ex : Multi - Level Designed by Using AND and OR
 
$$f(a, b, c, d) = \sum m(1,5,6,10,13,14)$$



Using K - map Method :

$$f = a'c'd + bc'd + bcd' + acd' \dots\dots (1)$$

2 - level AND - OR gate network

\Rightarrow 2 levels, 5 gates, 16 gate inputs

Factoring :

$$f = c'd(a'+b) + cd'(a+b) \dots\dots (2)$$

\Rightarrow 3 levels, 5 gates, 12 gate inputs

or Use POS :

$$f = (c+d)(a'+b+c)(c'+d')(a+b+c) \dots\dots (3)$$



\Rightarrow 2 levels, 5 gates, 14 gate inputs

or $f = [c + d(a'+b)][c'+d'(a+b)] \dots\dots (4)$


\Rightarrow 3 levels, 7 gates, 12 gate inputs

Other Types of Gates


NAND :

  



$$F = (ABC)' = A' + B' + C'$$

 


A	B	AB	\overline{AB}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

 


NOR :

  


$$F = (A+B+C)' = A'B'$$

 


A	B	A+B	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 

Majority Gate

 

Minority Gate

 

Majority of inputs = 1 $\Rightarrow F_M = 1$

Minority of inputs = 1 $\Rightarrow F_m = 1$

Odd number of inputs

<i>a</i>	<i>b</i>	<i>c</i>	F_M	F_m
<i>0</i>	<i>0</i>	<i>0</i>	<i>0</i>	<i>1</i>
<i>0</i>	<i>0</i>	<i>1</i>	<i>0</i>	<i>1</i>
<i>0</i>	<i>1</i>	<i>0</i>	<i>0</i>	<i>1</i>
<i>0</i>	<i>1</i>	<i>1</i>	<i>1</i>	<i>0</i>
<i>1</i>	<i>0</i>	<i>0</i>	<i>0</i>	<i>1</i>
<i>1</i>	<i>0</i>	<i>1</i>	<i>1</i>	<i>0</i>
<i>1</i>	<i>1</i>	<i>0</i>	<i>1</i>	<i>0</i>
<i>1</i>	<i>1</i>	<i>1</i>	<i>1</i>	<i>0</i>


Functionally Complete Sets of Gates

A set of logic operations is Functionally Complete, if any Boolean function can be expressed in terms of this set of operations.

$\{AND, OR, NOT\}$

$\{AND, NOT\} \because OR = X + Y = (X' Y)'$


can be reduced by AND, NOT

 

$\{OR, NOT\}$




A functionally complete set of operations must contains NOT

NOT: Realized by NAND or NOR

 

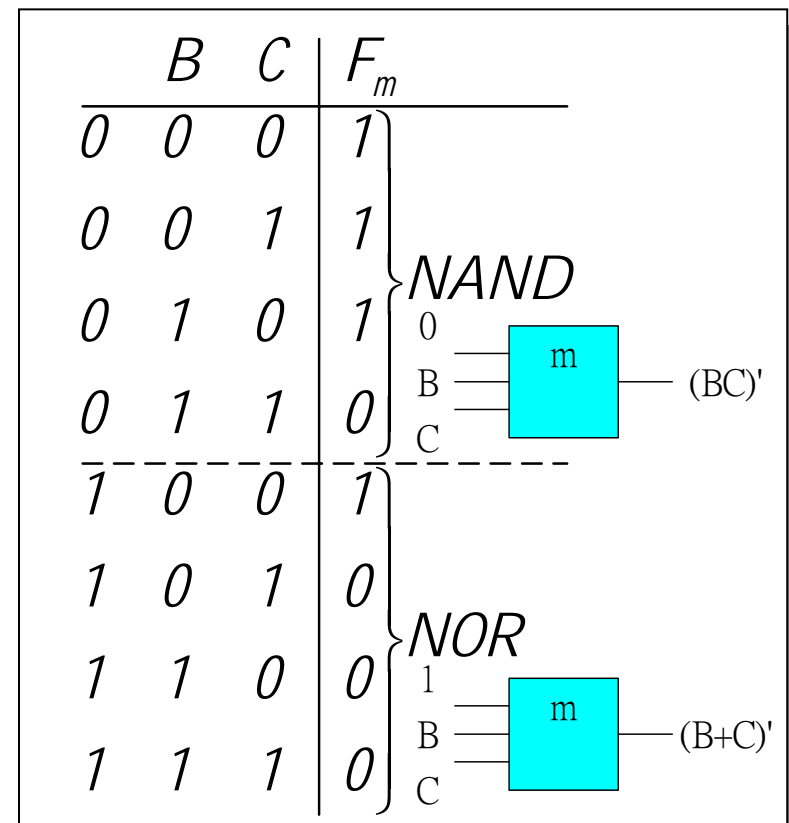 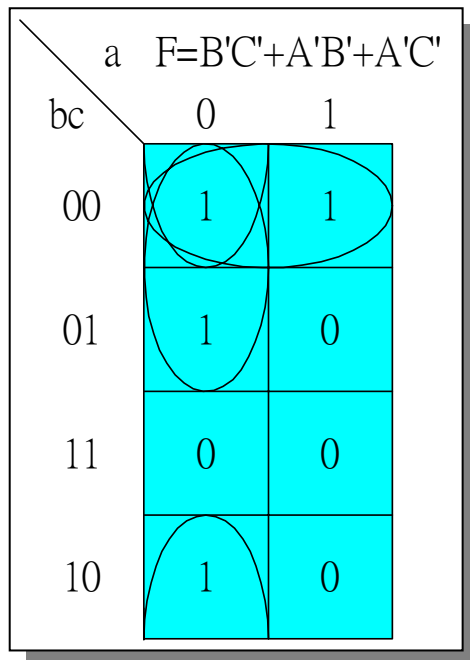
Example

3-input minority gates can realize any switching function




Example



1. Inverter : Let $C=B=A$

 

3. OR : $B+C = \left[(B+C)' \right]'$

 

  
2. AND : Let $A=1$ then $F_m = B'C'$
Must invert B & C in advance




Design of 2-Level NAND-and-NOR Gate Networks

NAND & NOR : Readily available in IC form

DeMorgan's Law

 


$$(A+B)' = A' B'$$

 


$$(A \cdot B)' = A'+B'$$

or

 

$$\text{OR} \quad (A+B) = (A' B')'$$

 


$$A \cdot B = (A'+ B)'$$


AND NOR with
complemented input

Sum of Product

Ex1 : AND / OR \Rightarrow NAND/NAND

 


Ex2 : AND / OR \Rightarrow NOR/NOR

 


故，前者較自然..

Product of Sum

Ex1 : OR / AND \Rightarrow NOR/NOR


 


Ex2 : OR / AND \Rightarrow NAND/NAND


 


故，前者較自然..

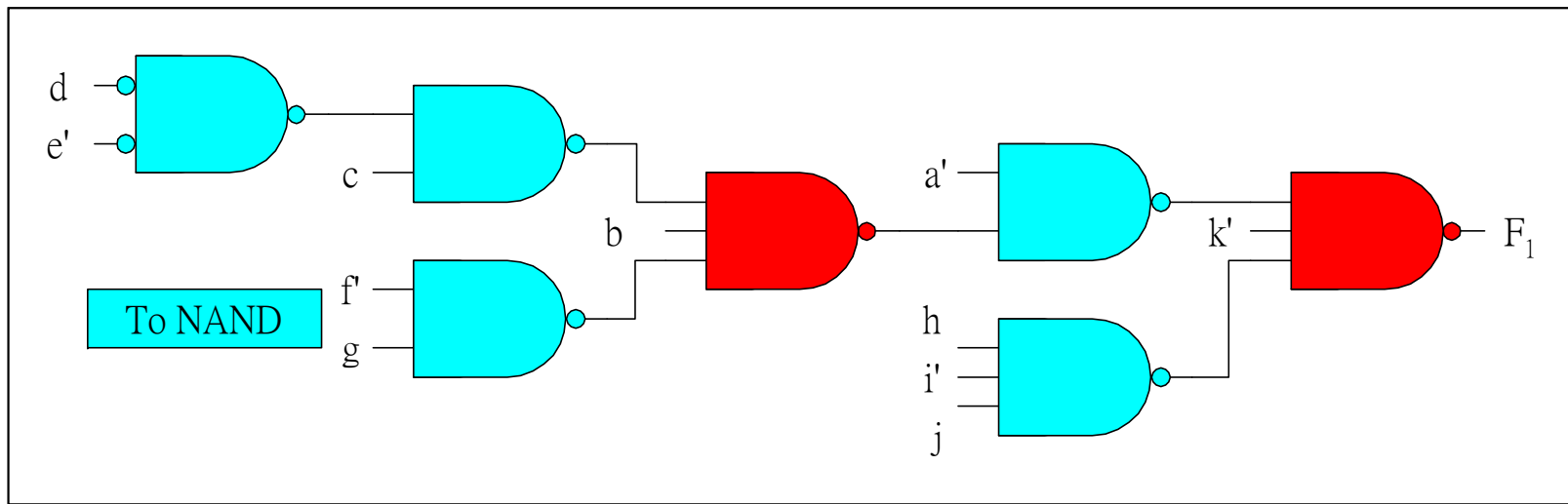 Multi-Level Network with NAND or NOR Gates



  Multi-Level Network with NAND or NOR Gates (Cont.)



§ Design of Two Level Multiple - Output Networks


$$\begin{aligned} \text{Ex: } F_1(A, B, C, D) &= \sum m(11, 12, 13, 14, 15) \\ F_2(A, B, C, D) &= \sum m(3, 7, 11, 12, 13, 15) \\ F_3(A, B, C, D) &= \sum m(3, 7, 12, 13, 14, 15) \end{aligned}$$

From K - Map


$$F_1 = AB + ACD$$

$$F_2 = ABC' + CD$$


$$F_3 = A'CD + AB$$

 

9 Gates, 21 Gate Inputs

 

7 Gates, 18 Gate Inputs

 

$$A'CD + ACD = CD$$

$$\rightarrow F_2 = (A'CD + ACD) + ABC'$$

$$= CD + ABC'$$

(1) 共用AB

(2) $A'CD + ACD$ 可得 CD ， CD covers $A'CD$ 與 ACD

Ex 1:

$$f_1 = \sum m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$



$$f_2 = \sum m(2, 3, 5, 6, 7, 10, 11, 14, 15)$$

$$f_3 = \sum m(6, 7, 8, 9, 13, 14, 15)$$


$$f_1 = {}_1bd + {}_2b'c + {}_3ab'$$

$$f_2 = {}_4a'bd + {}_5c$$
  
$$f_3 = {}_6bc + {}_7ab'c' + \begin{cases} {}_8ac'd \\ abd \end{cases}$$



10 Gates, 25 Gate Inputs

 


$$f_1 = {}_1a'bd + {}_2abd + {}_3ab'c' + {}_4b'c$$

$$f_2 = {}_1a'bd + c$$

$$f_3 = {}_3ab'c' + {}_2abd + bc$$



8 Gates, 22 Gate Inputs

 



Prime implicant 有時被拆開成 non prime implicants

假如其他 F's 有此 non prime implicants

Ex : a.

  





Better
Solution

  

Ex : b. (反例)

如圖所示，不用
common term 反而好

→ 故視情況而定

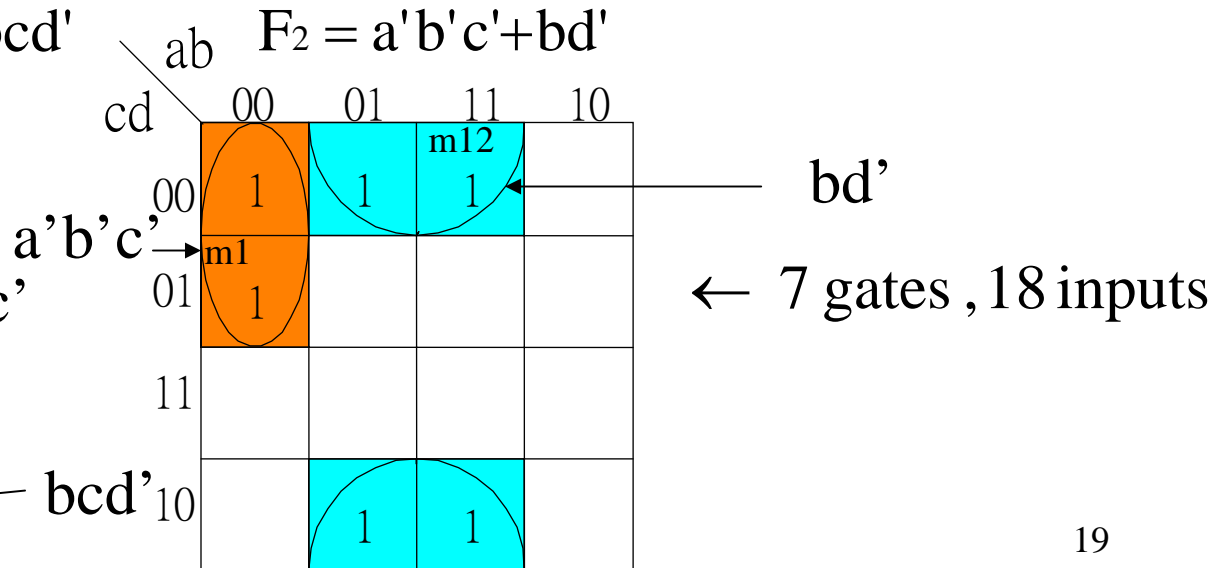   

§ Determination of Essential Prime Implicants , for M-Output Realization

Check essential prime implicants for every function

Ex. A term in only one prime implicant, but not in other functions

In Ex a : $C'D (m_1, m_5, m_9)$, $BD' (m_4, m_6, m_{12})$ are essential,
 ABD , ABC not essential.


$\because m_{15}$ is in ABD of F_1 , and in ABC of F_2

In Ex b : $a'd' (m_2)$, $a'bc (m_5)$, $a'b'c' (m_1)$, $bd' (m_{12})$ are essential.

Generally, essential terms 不適合部份拆開 ,
因其必定還是要包含此 term.

§ Design of Code Conversion Network:

 Convert 8 - 4 - 2 - 1 BCD to Excess - 3 Code



$$w = a + bc + bd$$

$$x = bc' d' + b' d + b' c$$

$$y = c' d' + cd$$

$$z = d'$$

<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>	
0	0	0	0	0	0	1	1	0
0	0	0	1	0	1	0	0	1
0	0	1	0	0	1	0	1	2
0	0	1	1	0	1	1	0	3
0	1	0	0	0	1	1	1	4
0	1	0	1	1	0	0	0	5
0	1	1	0	1	0	0	1	6
0	1	1	1	1	0	1	0	7
1	0	0	0	1	0	1	1	8
1	0	0	1	1	1	0	0	9
1	0	1	0	X	X	X	X	
1	0	1	1	X	X	X	X	
1	1	0	0	X	X	X	X	
1	1	0	1	X	X	X	X	
1	1	1	0	X	X	X	X	
1	1	1	1	X	X	X	X	

	ab	W			
cd		00	01	11	10
00		0	0	X	1
01		0	1	X	1
11		0	1	X	X
10		0	1	X	X

	ab	X			
cd		00	01	11	10
00		0	1	X	0
01		1	0	X	1
11		1	0	X	X
10		1	0	X	X

2-Level Network:

10 Gates

$$w = a + bc + bd$$

$$x = bc'd + b'd + b'c$$

$$y = c'd' + cd$$

$$z = d'$$

	ab	y			
cd		00	01	11	10
00		1	1	X	1
01		0	0	X	0
11		1	1	X	X
10		0	0	X	X

	ab	Z			
cd		00	01	11	10
00		1	1	X	1
01		0	0	X	0
11		0	0	X	X
10		1	1	X	X

3-Level Network:

$$w = a + b(c + d)$$



$$x = bc'd + b'(c + d)$$

$$y = c'd' + cd$$

$$z = d'$$

9 Gates

Multi-Output NAND NOR Networks

  

Home Work: Unit 7

- 7-2(b)
- 7-6
- 7-8
- 7-13(a)
- 7-17
- 7-24
- 7-32
- 7-39