

# **Unit 8.**

## **Combinational Circuit Design and Simulation Using Gates**

# Outline

- ✓ **Review of Combinational Circuit Design**
- ✓ **Design of Circuits with Limited Gate Fan-In**
- ✓ **Gate Delay and Timing Diagrams**
- ✓ **Hazards in Combinational Logic**
- ✓ **Simulation and Testing of Logic Circuits**

## 8-1 Review of Combinational Circuit Design


- ✓ **Design of a combinational switching circuit**
  - Setup a truth table which specifies the output(s) as a function of the input variables
  - Derive simplified algebraic expressions for the output functions using K-maps, the Q-M method, or other similar procedures.
- ✓ **Multi-level & Multi-output circuit**
- ✓ **Minimum SOP's starting point**
  - Minimum two-level AND-OR, NAND-NAND, OR-NAND, NOR-OR
- ✓ **Minimum POS's starting point**
  - Minimum two-level OR-AND, NOR-NOR, AND-NOR, NAND-AND

## 8-2 Circuit with Limited Gate Fan-In

### ✓ Example I


Realize  $f(a,b,c,d) = \sum m(0,3,4,5,8,9,10,14,15)$   
using 3-input NOR gates

		ab			
		00	01	11	10
cd	00	1	1	0	1
	01	0	1	0	1
	11	1	0	1	0
	10	0	0	1	1

 


$$\begin{aligned}
 f &= a'b'c'd + ab'cd + abc' + a'bc + a'cd' \\
 &= b'd(a'c' + ac) + a'c(b + d') + abc'
 \end{aligned}$$

 ✓ **Example II**  
**only using 2-input NAND gates and inverters**




$$f_1 = \Sigma m(0, 2, 3, 4, 5)$$

$$f_1 = b'c' + ab' + a'b$$

 

$$f_2 = \Sigma m(0, 2, 3, 4, 7)$$

$$f_2 = b'c' + bc + a'b$$

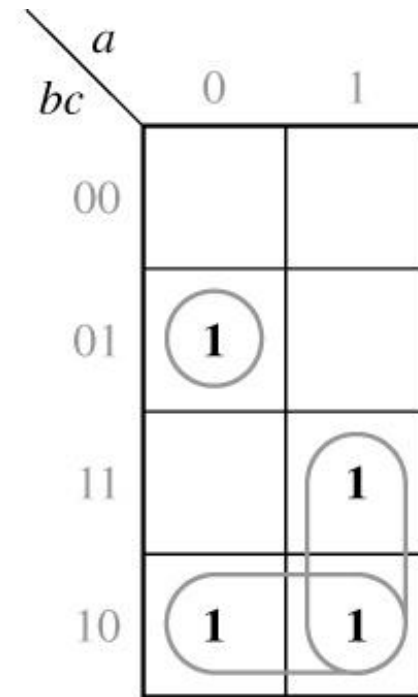


$$f_3 = \Sigma m(1, 2, 6, 7)$$

$$f_2 = a'b'c + ab + bc'$$


$$f_1 = b'(a + c') + a'b$$

$$f_2 = b(a' + c) + b'c' \quad \text{or} \quad f_2 = (b' + c)(b + c') + a'b$$

$$f_3 = a'b'c + b(a + c')$$






 


(a)

 

(b)

# 8-3 Gate Delay and Timing Diagrams

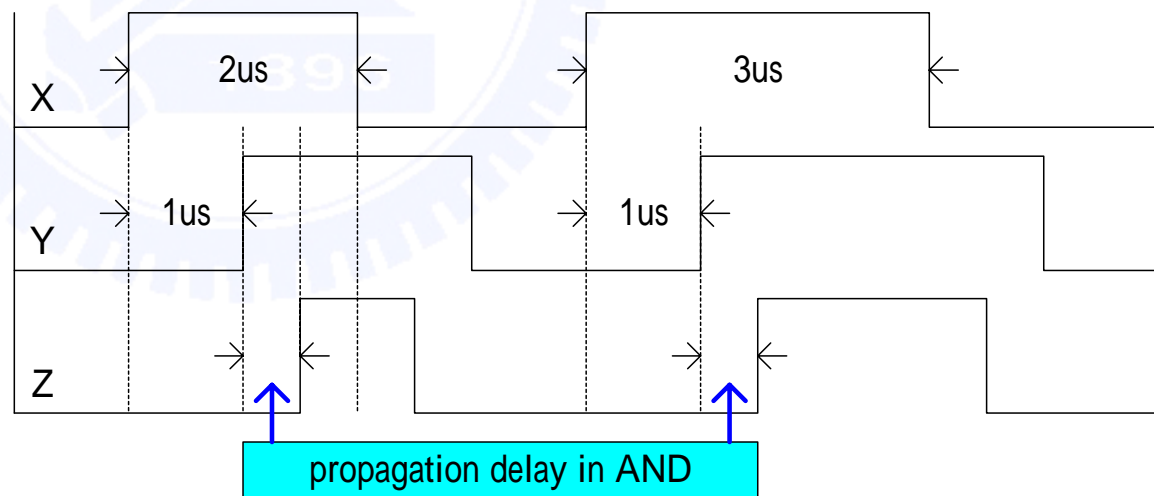     


## 8-4 Hazard in Combinational Logic

### ✓ What is hazard?

- **Unwanted** switching transients appearing in the output while the input to a combinational circuit changes

### ✓ Types of hazards

 



### ✓ In K-Map,

- If any two adjacent 1's are not covered by the same loop, a 1-hazard exists for the transition between the two 1's.





# Static 1-hazard

✓ Let  $A=1$  and  $C=1$

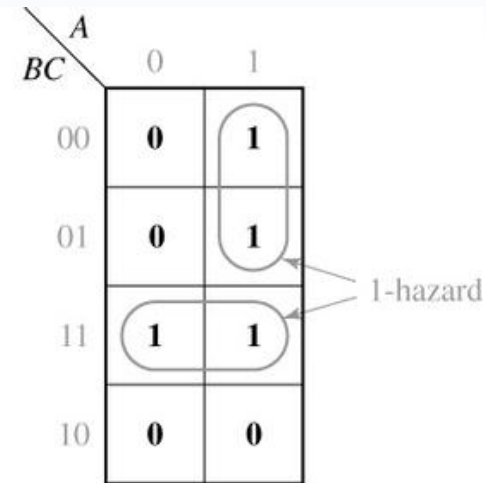
 


## Circuit with Hazard Removed

  

# Static 0-hazard

✓ Let  $A=0$ ,  $B=1$ , and  $D=0$

  

 
## Circuit with Hazard Removed

$$F = (A + C)(A' + D')(B' + C' + D)$$



$$F = (A + C)(A' + D')(B' + C' + D)(C + D')(A + B' + D)(A' + B' + C')$$



## 8-5 Simulation and Testing of Logic Circuits

### ✓ For simulation logic circuits

- Specify the circuit components and connections
- Determine the circuit inputs
- Observe the circuit outputs

### ✓ 4-valued logic simulator


- 0 (low), 1 (high), X (unknown), Z (high impedance)

#### AND & OR function for 4-valued simulation

●	0	1	X	Z	+	0	1	X	Z
0	0	0	0	0	0	0	1	X	X
1	0	1	X	X	1	1	1	1	1
X	0	X	X	X	X	X	1	X	X
Z	0	X	X	X	Z	X	1	X	X
 
# Testing of logic circuits

- ✓ In the logic circuit, a wrong output may be due to
  - Incorrect design
  - Gates connected wrong
  - Wrong input signals to the circuit
  - Defective gates
  - Defective connecting wires
- ✓ Logic circuit with incorrect output



# Homework

- ✓ 1、 3、 5、 7、 10
- ✓ Design Problems

